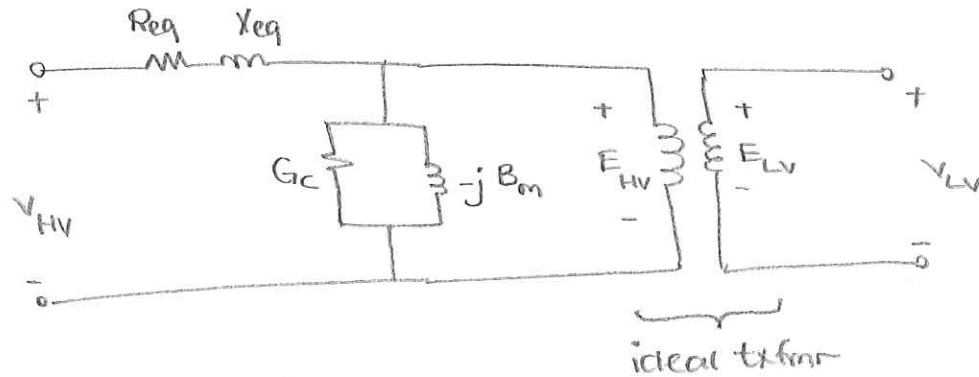


Name:

SOLUTION

ID:

**1a)** Draw the equivalent circuit for a non-ideal transformer with all the impedances referred to the high voltage side. Your circuit should contain  $R_{eq}$ ,  $X_{eq}$ ,  $B_m$ ,  $G_c$ , and an ideal transformer. Also, label the terminal voltages  $V_{HV}$  and  $V_{LV}$ , and winding voltages  $E_{HV}$  and  $E_{LV}$ . [3 marks]



**1b)** For a 200 MVA, 138 kV/13.8 kV single phase transformer, an open circuit test is performed to calculate the  $B_m$  and  $G_c$  parameters in the model from part a). With the high voltage side open, the following measurements were taken on the low voltage side:

Voltage = 13.8 kV, current = 1794 A, power = 952.2 kW.

What are the  $B_m$  and  $G_c$  parameters for this transformer in Siemens? [3 marks]

$$E_{HV} = 13.8 \text{ kV} \times \frac{138}{13.8} = 138 \text{ kV}$$


$$I_{HV} = 1794 \times \frac{13.8}{138} = 179.4 \text{ A}$$

$$P_{oc} = E_{HV}^2 \cdot G_c$$


$$\therefore G_c = \frac{P_{oc}}{E_{HV}^2} = \frac{952.2 \text{ kW}}{(138 \text{ kV})^2} = 5 \times 10^{-5} \text{ S}$$

$$Y_{eq} = \frac{I_{HV}}{E_{HV}} = \frac{179.4 \text{ A}}{138 \text{ kV}} = 13 \times 10^{-4} \text{ S}$$

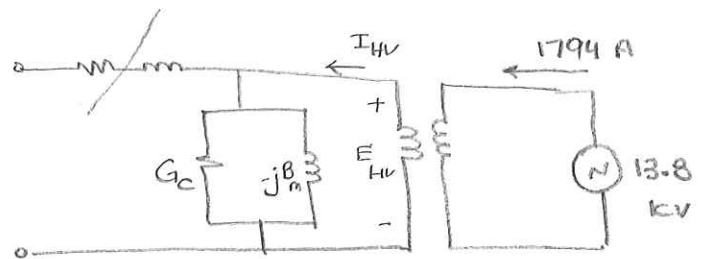
$$B_m = \sqrt{Y_{eq}^2 - G_c^2} \approx 13 \times 10^{-4} \text{ S}$$



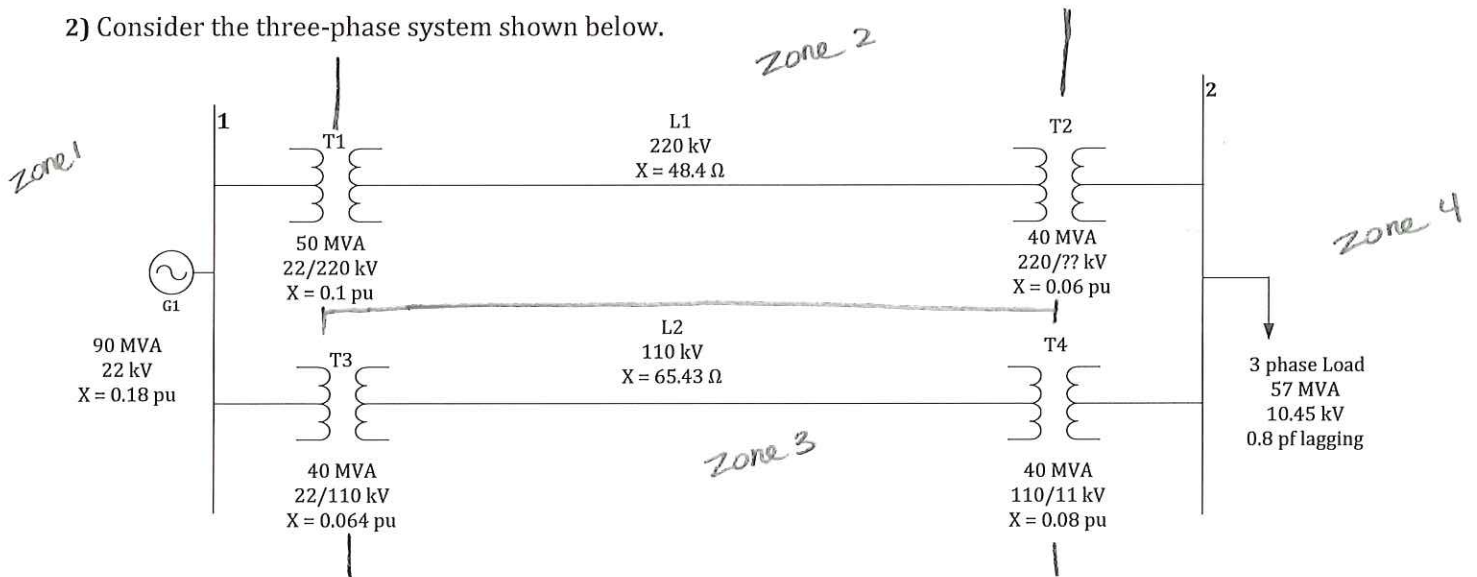2) Consider the three-phase system shown below.



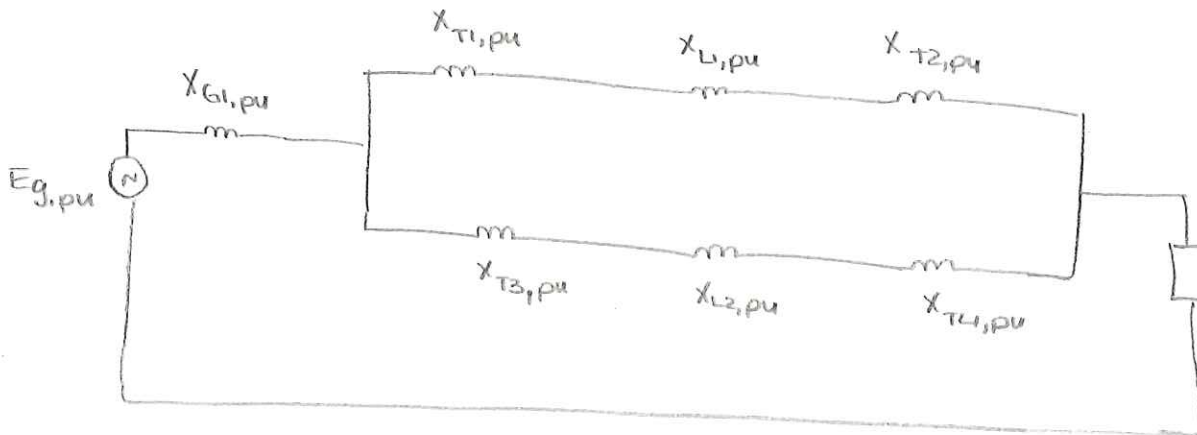a) Draw the per unit impedance diagram for this system. Label (but do not calculate) all impedances on the diagram. For example, the per unit impedance of T1 should be labelled as  $X_{T1,pu}$  on the diagram. [3 marks]



b) What should the voltage rating of T2 be? [2 marks]

To get the same  $V_{base}$  for load zone (zone 4 in diagram above), whether we calculate it from L1 side or L2 side, T2 should be  $220 / 11 \text{ kV}$

e.g. let's say  $V_{base_1} = 22 \text{ kV} \rightarrow V_{base_2} = 22 \times \frac{220}{22} = 220 \text{ kV}$

$V_{base_3} = 22 \times \frac{110}{11} = 110 \text{ kV}$

$V_{base_4} = V_{base_3} \times \frac{11}{110} = 11 \text{ kV}$ ,  $V_{base_4} = V_{base_2} \times \frac{??}{220} = 11 \text{ kV} \therefore ?? = 11 \text{ kV}$

- c) If a power base of 100 MVA and voltage base of 10kV on the load side is chosen, what is the per unit impedance of T4? [2 marks]

$$S_{\text{base}} = 100 \text{ mVA}$$

$$V_{\text{base}_4} = 10 \text{ kV}$$

$$\begin{aligned} X_{T4, \text{pu}, \text{new}} &= 0.08 \times \frac{100 \text{ mVA}}{40 \text{ mVA}} \times \left( \frac{11 \text{ kV}}{10 \text{ kV}} \right)^2 \\ &= 0.242 \text{ pu} \end{aligned}$$

- d) If the generator is operating at rated power and a line-to-line terminal voltage of 20 kV, calculate the magnitude of the line current entering bus 1 from the generator side. [2 marks]

in Amps

Let's use Gen rated values as base values:

$$S_{\text{gen, pu}} = 1 \text{ pu}$$

$$V_{\text{gen, pu}} = \frac{20 \text{ kV}}{22 \text{ kV}} = 0.91 \text{ pu}$$

$$|I_{\text{gen, pu}}| = \frac{S_{\text{gen, pu}}}{V_{\text{gen, pu}}} = \frac{1}{0.91} = 1.1 \text{ pu}$$

$$|I_{\text{gen}}| = 1.1 \text{ pu} \times I_{\text{rated}} = 1.1 \times \frac{90 \text{ mVA}}{\sqrt{3} \times 22 \text{ kV}} = 2598 \text{ A}$$

.If using base values from part c):

$$V_{\text{base}_1} = 20 \text{ kV}, \quad S_{\text{base}} = 100 \text{ mVA}$$

$$S_{\text{gen, pu}} = \frac{90 \text{ mVA}}{100 \text{ mVA}} = 0.9 \text{ pu}$$

$$V_{\text{gen, pu}} = \frac{20 \text{ kV}}{V_{\text{base}_1}} = 1 \text{ pu}$$

$$|I_{\text{gen, pu}}| = \frac{S_{\text{gen, pu}}}{V_{\text{gen, pu}}} = 0.9 \text{ pu}$$

$$|I_{\text{gen}}| = 0.9 \text{ pu} \times I_{\text{base}_1} = 0.9 \times \frac{100 \text{ mVA}}{\sqrt{3} \times 20 \text{ kV}} = 2598 \text{ A}$$

For Q2d, you could also simply re-arrange  $S_3\phi = \sqrt{3} V_{ll} I$  to solve for  $I$ !

in %

3) Consider a three phase, 100 MVA, 20kV/200 kV transformer with a per unit impedance of  $3+j4$ . You can ignore the excitation branch. If the transformer is drawing 80% of its rated current, calculate the total power losses in the transformer in p.u. and in Watts. [4 marks]

using rated values as base values :

$$I_{pu} = \frac{I_{actual}}{I_{base}} = \frac{0.8 \times I_{rated}}{I_{rated}}$$

$$= 0.8 \text{ pu}$$

$$P_{pu} = I_{pu}^2 \times R_{pu} = 0.8^2 \times 0.03 = 0.0192 \text{ pu}$$

$$P_{actual} = P_{pu} \times S_{base} = 0.0192 \times 100 \text{ MW} = 1.92 \text{ MW}$$

