

General

Single Phase \bar{S}:	$\bar{S} = \bar{V} \cdot \bar{I}^*$
Q for L and C:	$Q_L = \frac{V^2}{X_L} \quad Q_C = \frac{V^2}{X_C}$
Y Connection:	$\bar{V}_{ll} = \sqrt{3} \angle 30^\circ \cdot \bar{V}_\phi$
Δ Connection:	$\bar{I}_l = \sqrt{3} \angle -30^\circ \cdot \bar{I}_\phi$
3 Phase Power:	$\bar{S}_{3\phi} = 3 \cdot \bar{V}_\phi \cdot \bar{I}_\phi^*$ $S = \sqrt{3} \cdot V_{ll} \cdot I_l$ $P = S \cdot pf \quad S^2 = P^2 + Q^2$

Per Unit

Single Phase:	$S_{\text{base},1\phi} = P_{\text{base},1\phi} = Q_{\text{base},1\phi}$ $I_{\text{base}} = \frac{S_{\text{base},1\phi}}{V_{\text{base,L-N}}}$ $Z_{\text{base}} = R_{\text{base}} = X_{\text{base}}$ $Z_{\text{base}} = \frac{V_{\text{base,L-N}}}{I_{\text{base}}} = \frac{V_{\text{base,L-N}}^2}{S_{\text{base},1\phi}}$
Three Phase:	$S_{\text{base},3\phi} = 3 \cdot S_{\text{base},1\phi}$ $V_{\text{base,L-L}} = \sqrt{3} V_{\text{base,L-N}}$ $I_{\text{base}} = \frac{S_{\text{base},3\phi}}{\sqrt{3} V_{\text{base,L-L}}}$ $Z_{\text{base}} = \frac{V_{\text{base,L-L}}^2}{S_{\text{base},3\phi}}$
Change of Base:	$Z_{\text{pu,new}} = Z_{\text{pu,old}} \left(\frac{V_{\text{base,old}}}{V_{\text{base,new}}} \right)^2 \frac{S_{\text{base,new}}}{S_{\text{base,old}}}$