

**University of Calgary
Schulich School of Engineering
Department of Electrical and Computer Engineering**

ENEL 476 – Electromagnetic Waves and Applications

**Quiz #3
Winter Session 2016
Monday March 28, 2016
2:00-2:50 pm**

ICT 102

Student Name or ID number:

Dr. Fear

Question 1. (12 marks)

For a given transmission line, $R=100 \Omega/\text{m}$, $L=0.32 \mu\text{H}/\text{m}$, $G=0.03 \text{ S}/\text{m}$ and $C=96 \text{ pF}/\text{m}$. The frequency of operation is 100 MHz . Calculate:

a) The attenuation constant (α).

Approach 1:

$$\gamma = \alpha + j\beta$$

$$\textcircled{1} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\textcircled{1} = \sqrt{[100 + j(2\pi)(10^8)(0.32 \times 10^{-6})][0.03 + j(2\pi)(10^8)(96 \times 10^{-12})]}$$

$$R + j\omega L = 100 + j201.1$$

$$= 224.6 \angle 1.1 \text{ rad}$$

$$G + j\omega C = 0.03 + j0.06$$

$$= 0.0671 \angle 1.1 \text{ rad}$$

$$= 3.482 \angle 1.1$$

$$= 1.73 + j3.48$$

$\textcircled{1}$

\Rightarrow

$$\alpha = 1.73 \text{ Np/m}$$

b) The phase constant (β).

$$\textcircled{1} \quad \beta = 3.48 \text{ rad/m}$$

Approach 2: distortionless line $\left(R/L = G/C \text{ or } R/G = L/C \right)$

or $\textcircled{1} \alpha = \sqrt{RG} \text{ Np}$

$$\textcircled{1} = 1.73 \text{ Np/m}$$

$$\textcircled{1} \beta = \omega \sqrt{LC}$$

$$= (2\pi)(10^8) \sqrt{(0.32 \times 10^{-6})(96 \times 10^{-12})}$$

$$\textcircled{1} = 3.48 \text{ rad/m}$$

c) The impedance of the line (Z_0).

Approach 1:

$$\textcircled{1} Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$= \sqrt{\frac{224.6 \angle 1.1}{0.0671 \angle 1.1}}$$

$$\textcircled{1} Z_0 = 57.86 \Omega$$

Approach 2:

or $\textcircled{1} Z_0 = \sqrt{L/C}$

$$\textcircled{1} = 57.7 \Omega$$

d) The wavelength (λ)

$$\textcircled{1} \lambda = \frac{2\pi}{\beta}$$

$$\textcircled{1} \lambda = 1.81 \text{ m}$$

e) The phase velocity (v_p)

$$\textcircled{1} v_p = \frac{\omega}{\beta}$$

$$\textcircled{1} = 1.81 \times 10^8 \text{ m/s}$$

f) What is the distance that the forward-traveling voltage wave must travel for its amplitude to be reduced to 90% of the initial value?

$$\textcircled{1} V_0^+ e^{-\alpha z} = 0.9 V_0^+$$

$$e^{-\alpha z} = 0.9$$

$$-\alpha z = \ln(0.9)$$

$$\textcircled{1} \boxed{z = 0.061 \text{ m}}$$

Question 2. (20 marks)

Consider a $75\text{-}\Omega$ transmission line of length 0.25λ . The line is terminated with a load of $Z_L = 80 + j50\text{ }\Omega$. Find:

a) The reflection coefficient at the load (Γ_L)

$$\begin{aligned} \textcircled{1} \Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{(80 + j50) - 75}{80 + j50 + 75} \\ &= 0.31 \angle 1.16 \text{ rad.} \end{aligned}$$

(1) (1)

b) The standing wave ratio (s)

$$\begin{aligned} \textcircled{1} S &= \frac{1 + |\Gamma|}{1 - |\Gamma|} \\ \textcircled{1} &= 1.892 \end{aligned}$$

c) The input impedance or the impedance looking into the 0.25λ length of line terminated by the load (Z_{in}).

$$\begin{aligned} \textcircled{1} Z_{in} &= Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \end{aligned}$$

$$\begin{aligned} \beta l &= \left(\frac{2\pi}{\lambda}\right)(0.25\lambda) \\ &= \pi/2 \end{aligned}$$

$\tan(\beta l) \rightarrow \infty$

$Z_0 \tan \beta l \gg Z_L$

$$\therefore Z_{in} = Z_0 \left(\frac{jZ_0 \tan \beta l}{jZ_L \tan \beta l} \right)$$


$Z_L \tan \beta l \gg Z_0$

$$\begin{aligned} \textcircled{1} Z_{in} &= \frac{Z_0^2}{Z_L} \\ &= \frac{75^2}{80 + j50} \\ \boxed{Z_{in} = 50.56 - j31.6} \end{aligned}$$

(1) (1)

The transmission line in the first part of the question is connected to a generator that delivers 10V and has internal impedance of 75Ω .

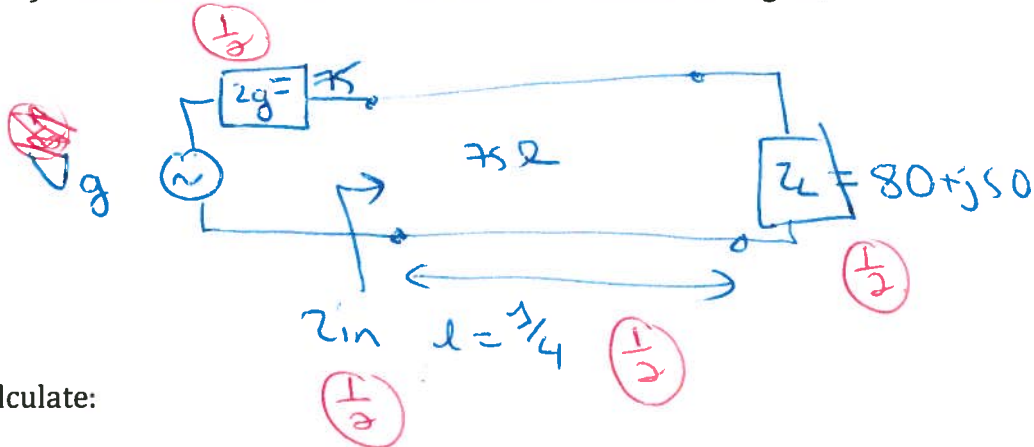d) Draw a sketch of the source, line and load, indicating Z_{in} .



Calculate:

e) The input current to the line (I_{in})

$$\begin{aligned} I_{in} &= \frac{V_g}{Z_{in} + 2g} \\ &= \frac{10}{75 + 50.56 - j31.62} \\ &= 0.077 \angle 0.247 \text{ rad} \end{aligned}$$

f) The power absorbed by the load (P_L)

$$\begin{aligned} P_L &= \frac{1}{2} |I_{in}|^2 \operatorname{Re}\{Z_{in}\} \\ &= \frac{1}{2} (0.077)^2 (50.56) \\ P_L &= 0.15 \text{ W} \end{aligned}$$

g) The amplitude of the forward traveling voltage wave (V_0^+).

$$\begin{aligned} V_{in} &= V_0^+ e^{j\beta l} + \rho V_0^+ e^{-j\beta l} \Rightarrow V_{in} = V_0^+ [e^{j\frac{\pi}{2}} + \rho e^{-j\frac{\pi}{2}}] \\ &= V_0^+ [j - j\rho] \\ V_{in} &= (V_g) \left(\frac{Z_{in}}{Z_{in} + 2g} \right) \\ &= 10 \left(\frac{50.56 - j31.6}{50.56 - j31.6 + 75} \right) \\ &= 4.38 - j1.41 \end{aligned}$$

$$V_0^+ = \frac{4.38 - j1.41}{j(1 - \rho)} \Rightarrow$$

$$V_0^+ = \frac{4.38 - j1.41}{j(1 - 0.31 \angle 1.16)}$$

$$= -j5$$

① $\therefore V_0^+ = -5$ ($V_0^+ = 5$ is also fine)

$$V(z, t) = -5 \cos(\omega t - \beta z + \phi) = 5 \cos(\omega t - \beta z + \phi + \phi_p)$$

Name	
Q1	
Q2	
Total	