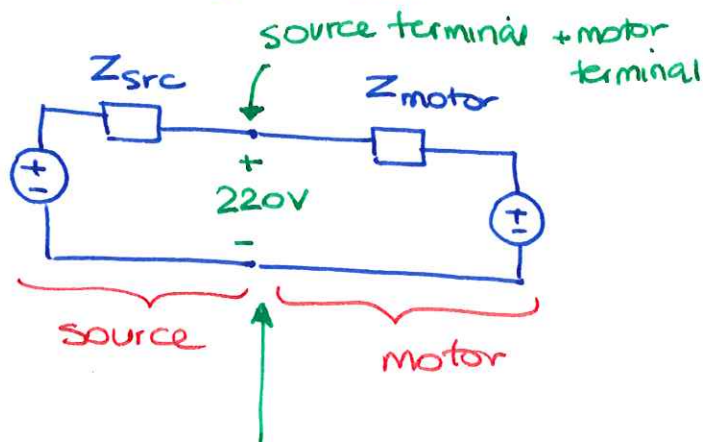


Tutorial 2

1) Let's draw the circuit:




Unless otherwise stated, voltage of a generator (or motor) refers to the terminal voltages

we can use the EMF behind an impedance model for motors & generators.


In this problem, we don't need to!

(We also don't know Z_{src} , Z_{motor} or internal EMF values).

Let's redraw:

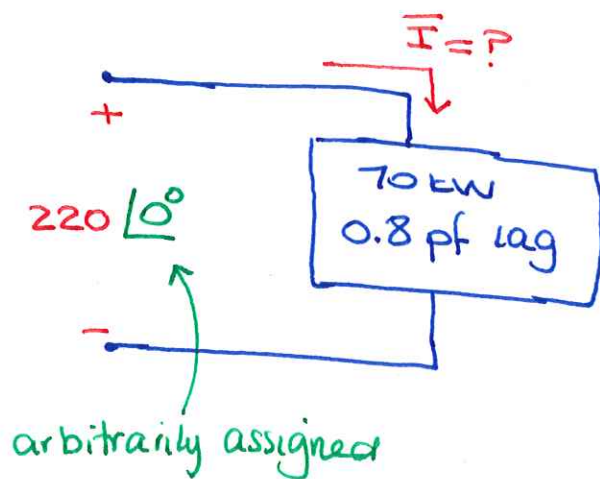

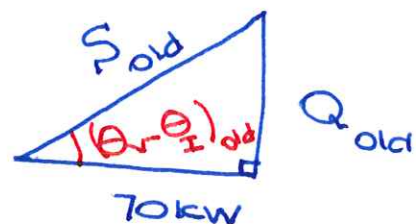power triangle for existing configuration:



$$(\theta_v - \theta_i)_{old} = \cos^{-1}(0.8) = \textcircled{+} 36.87^\circ \quad \leftarrow (\theta_v - \theta_i) > 0 \text{ for lagging PF}$$

$$Q_{old} = P_{old} \times \tan(\theta_v - \theta_i)_{old} = 52.5 \text{ kVar}$$

$$S_{old} = \frac{P_{old}}{\text{PF}} = \frac{70 \text{ kW}}{0.8} = 87.5 \text{ kVA}$$

can calculate mag & phase of \bar{I} separately:


$$S = V \cdot I \quad \therefore I = \frac{S}{V} = \frac{87.5 \text{ kVA}}{220 \text{ V}} = 397.7 \text{ A}$$

$$\theta_V - \theta_I = 36.87^\circ \quad \therefore \theta_I = 0 - 36.87^\circ = -36.87^\circ$$

$$\bar{I} = 397.7 \angle -36.87^\circ \text{ A}$$

could have also used $\bar{S} = \bar{V} \bar{I}^*$ to find \bar{I} in one shot

b.

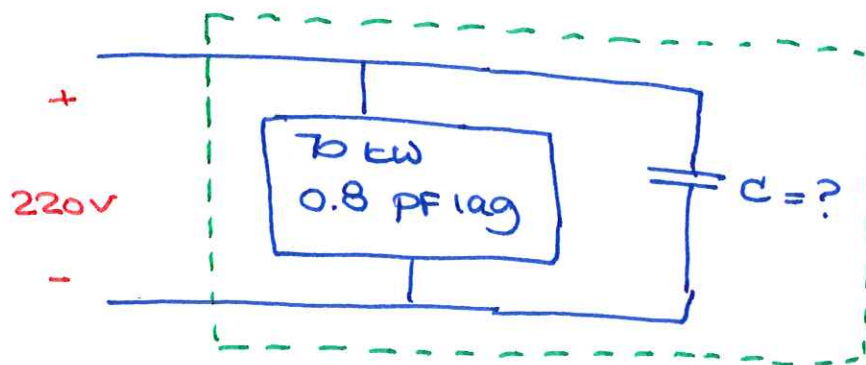

PF = 0.95 lagging

After adding cap:



$$(\theta_V - \theta_I)_{\text{new}} = \cos^{-1}(0.95) = \overset{\text{still lag}}{\text{+}} 18.19^\circ$$

$$Q_{\text{new}} = \underbrace{P_{\text{new}}}_{\text{still 70 kW}} \times \tan(\theta_V - \theta_I)_{\text{new}} = 23 \text{ kVAR}$$


$$Q_{\text{cap}} = Q_{\text{new}} - Q_{\text{old}} = -29.5 \text{ kVAR}$$

using the same procedure as tutorial 1, we can find

$$C = 1.62 \times 10^3 \text{ } \mu\text{F}$$

2)

line-to-line
voltage at
source
terminals

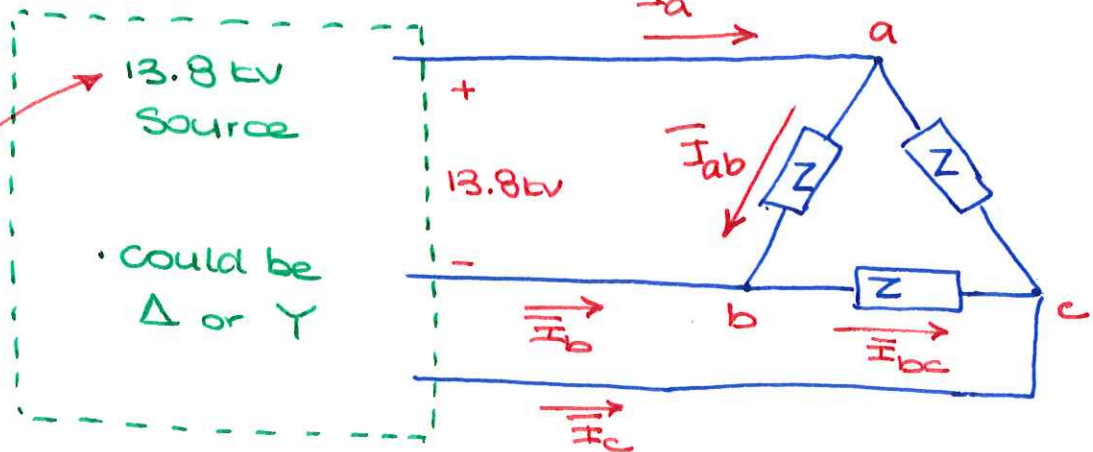

arbitrarily assigned since phase angle information about voltages or currents is provided

$$\overline{V}_{ab} = 13.8 \angle 0^\circ \text{ kV}$$

$$\overline{V}_{bc} = 13.8 \angle -120^\circ \text{ kV}$$

$$\overline{V}_{ca} = 13.8 \angle +120^\circ \text{ kV}$$

From Ohm's Law: $\overline{I}_{ab} = \frac{\overline{V}_{ab}}{Z_\Delta} = \frac{13.8 \angle 0^\circ \text{ kV}}{100 \angle 20^\circ \Omega} = 138 \angle -20^\circ \text{ A}$

To calculate power:

option 1) $\overline{S}_{3\phi} = 3 \cdot \overline{S}_{1\phi} = 3 \cdot \overbrace{\overline{V}_\phi} \cdot \overbrace{\overline{I}_\phi^*}$

$$= 3 (13.8 \angle 0^\circ \text{ kV}) (138 \angle +20^\circ \text{ A})$$

$$= 5.7 \angle 20^\circ \text{ MVA} = \underbrace{5.37}_{P_{3\phi} \text{ (MW)}} + j \underbrace{1.95}_{Q_{3\phi} \text{ (MVAR)}}$$

option 2) $\overline{S}_{3\phi} = \sqrt{3} V_{ll} \cdot \overline{I}_l = \sqrt{3} \cdot (13.8 \text{ kV}) (138 \times \sqrt{3})$

$$= 5.7 \text{ MVA}$$

$\overline{I}_l = \sqrt{3} \cdot \overline{I}_\phi \text{ for } \Delta$

$$\text{PF} = \cos(\theta_{V_\phi} - \theta_{I_\phi}) = \cos(\theta_Z) = \cos(20^\circ) = 0.94$$

$$P_{3\phi} = \overline{S}_{3\phi} \cdot \text{PF} = 5.37 \text{ MW}$$

$$Q_{3\phi} = \sqrt{\overline{S}_{3\phi}^2 - P_{3\phi}^2} = 1.95 \text{ MVAR}$$

Aside : $\overline{I}_{bc} = 138 \angle -20^\circ - 120^\circ$ A \overline{I}_{bc} lags \overline{I}_{ab} by 120°

$$\overline{I}_{ca} = 138 \angle -20^\circ + 120^\circ \quad A$$

$$\overline{I}_a = \sqrt{3} \times 138 \angle -20^\circ - 30^\circ = \sqrt{3} \times 138 \angle -50^\circ \quad A$$

$$\overline{I}_b = \sqrt{3} \times 138 \angle -50^\circ - 120^\circ$$

$$\overline{I}_c = \sqrt{3} \times 138 \angle -50^\circ + 120^\circ$$