

## ENEL 476 – Winter 2018

### Written Assignment #3

Due Friday April 13, 2018 (drop box on 2<sup>nd</sup> floor of ICT or via D2L)

A transmission line with  $Z_0 = 50 \Omega$  is connected to a load of  $Z_L = 20 - j20 \Omega$ . The frequency of operation is 1 GHz, and the velocity of propagation on the line is  $0.9c$  (where  $c$  is the speed of light in free space).

- Design a series stub tuner to match the load to the line. Select the stub location that is closest to the load. Specify the location of the stub and length of the open-circuited stub required to match the load. Use both wavelengths and physical distance.
- Design a shunt stub tuner to match the load to the line. Select the stub location that is closest to the load. Specify the location of the stub and length of the open-circuited stub required to match the load. Use wavelengths.
- Design a quarter-wavelength transformer to match the load to the line. Specify the location of the quarter-wavelength transformer relative to the load (in wavelengths), as well as the impedance of the quarter-wavelength line.

Submit the Smith chart that you used to design the tuners and transformer, as well as a summary of the locations and lengths (stub tuners) or location and impedance (quarter-wavelength transformer).

$$Z_L = 20 - j20$$
$$Z_0 = 50$$

$$Z_L = \frac{20 - j20}{50}$$

$$Z_L = 0.4 - j0.4$$

$$\lambda = \frac{0.9c}{f}$$
$$= \frac{0.9c}{1 \times 10^9}$$
$$= \frac{(0.9)(3 \times 10^8)}{1 \times 10^9}$$
$$= \frac{2.7}{10}$$
$$= 0.27 \text{ m}$$

$$\Rightarrow \lambda = 0.27 \text{ m}$$

a) Series stub tuning

↳ uplot  $z_L$

↳ draw constant- $s$  circle

↳ rotate towards generator to intersection with  $r=1$  circle


$$\rightarrow z_L @ 0.43\lambda$$

$$\rightarrow z_{i'} @ 0.166\lambda$$

$$\Rightarrow (0.5 - 0.43)\lambda = 0.07\lambda$$

$$0.07\lambda + 0.166\lambda = 0.236\lambda$$

$\Rightarrow$  this is stub location

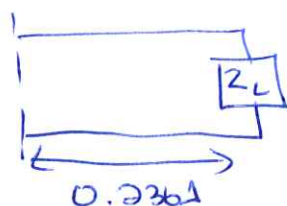

↳ at  $z_{i'}$ , the impedance  $z_{i'} = 1 + j1.1$

↳ need stub with  $z_{\text{stub}} = -j1.1$  to cancel imaginary component

↳ start at open & rotate around outside of chart to  $-j1.1$



$$\rightarrow \text{open @ } 0.25\lambda$$

$$\rightarrow -j1.1 @ 0.368\lambda$$

$$\Rightarrow (0.368 - 0.25)\lambda = 0.118\lambda$$

$\Rightarrow$  this is stub length

$$\Rightarrow \text{Stub location: } 0.236\lambda \text{ or } (0.236)(0.21) = 6.372\text{cm}$$

$$\text{stub length: } 0.118\lambda \text{ or } (0.118)(0.21) = 3.186\text{cm}$$




# Normalized Impedance Smith Chart

version 1.0  
2014-01-30



algernis

stub location

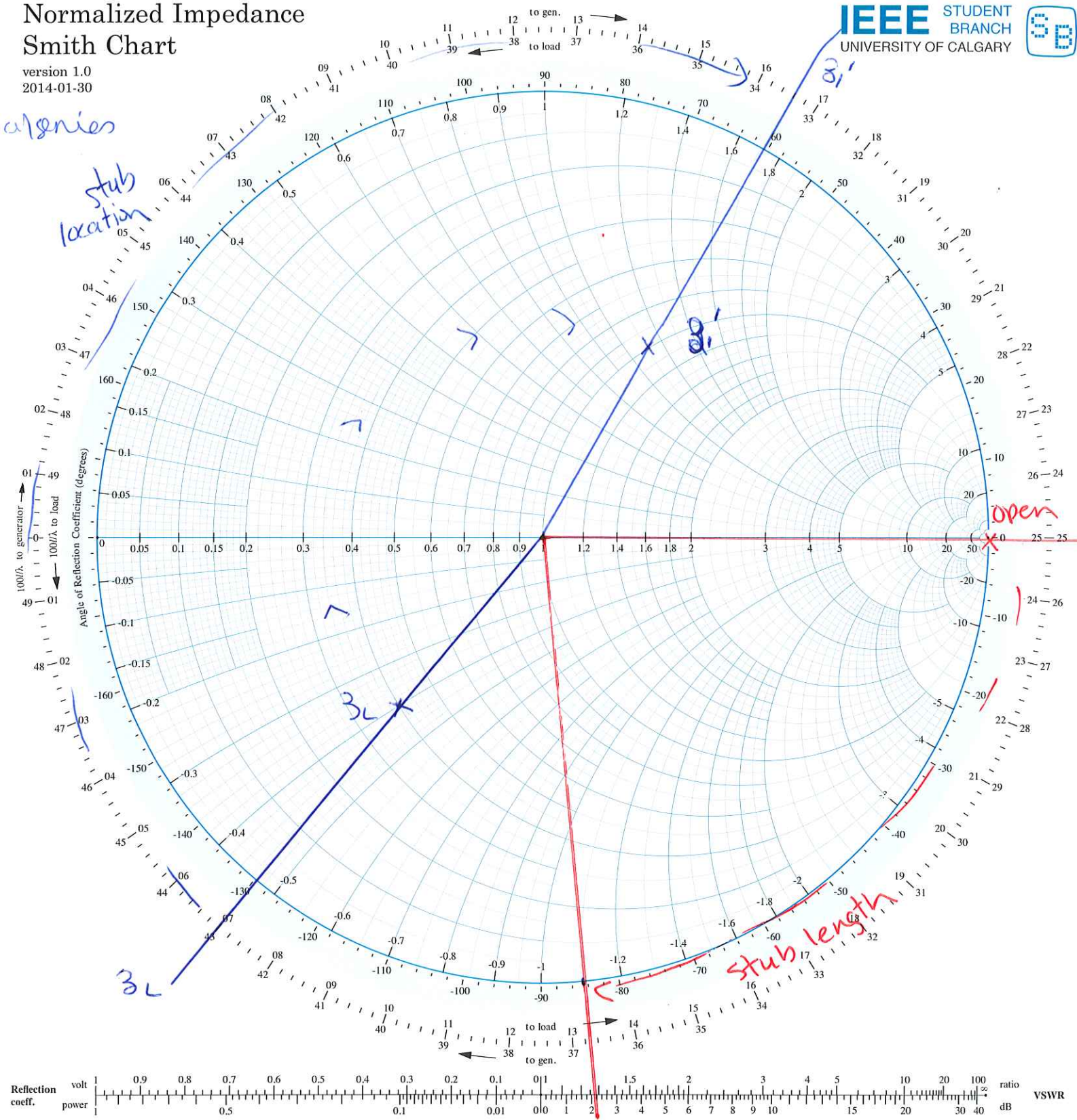

b) shunt stub tuning

↳ plot  $z_L$

↳ rotate  $180^\circ$  on chart to obtain  $y_L$   
(working in parallel  $\Rightarrow$  want to use admittance)

↳ draw constant  $s$ -circle

↳ rotate towards generator to intersection with  $g=1$  circle


$$\rightarrow y_L @ 0.182j$$

$$\rightarrow y_1' @ 0.334j$$

$$\rightarrow (0.334 - 0.182)j = 0.152j \Rightarrow \text{stub location}$$

$$\rightarrow @ y_1', \quad y_1' = 1 - j1.1$$

↳ need stub with  $y_{\text{stub}} = j1.1$  to cancel imaginary part

→  → start @ open & rotate around outside of chart to  $j1.1$ .

$$\rightarrow \text{open} @ 0$$

$$\rightarrow j1.1 @ 0.132j \Rightarrow \text{stub length: } 0.132j$$

$$\Rightarrow \text{Stub location: } 0.152j \text{ or } (0.152)(0.27) = 4.104\text{cm}$$

$$\text{Stub length: } 0.132j \text{ or } (0.132)(0.27) = 3.564\text{cm}$$





# Normalized Impedance Smith Chart

version 1.0  
2014-01-30



b) shunt

stub length

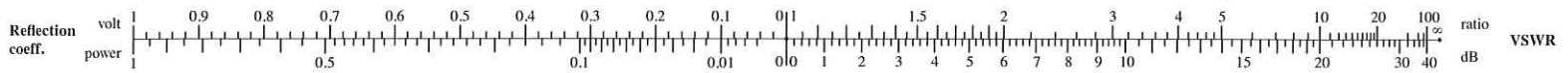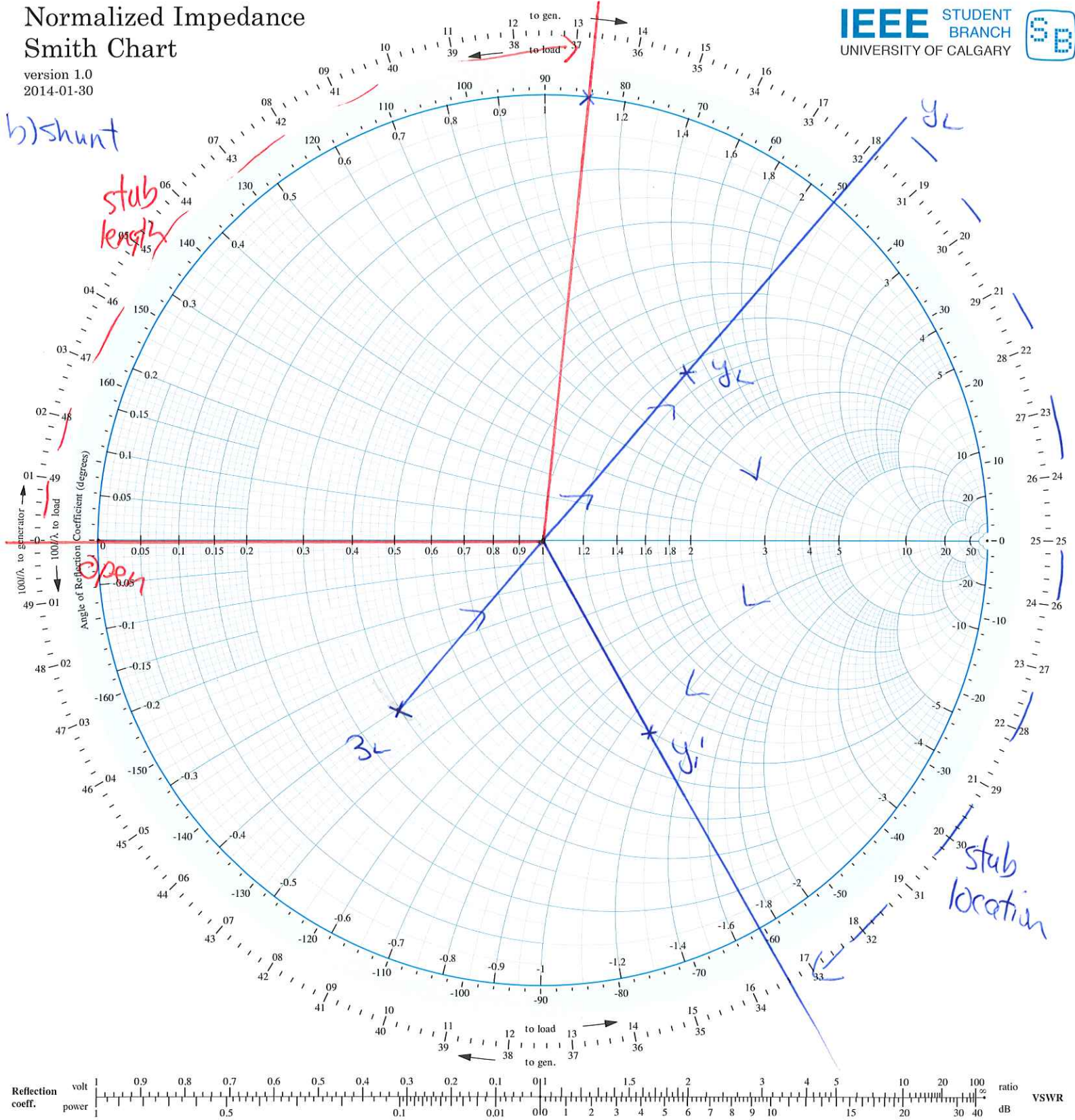

c)  $\rightarrow \frac{1}{4}$  transformer

$\rightarrow$  plot  $z_L$

$\rightarrow$  draw constant  $S$ -circle

$\rightarrow$  rotate from  $z_L$  to axis (i.e. want imaginary part of impedance to be zero)

$\hookrightarrow$  locations of  $V_{min}$  +  $V_{max}$

$V_{min}$

$z_L @ 0.43j$

$V_{min} @ 0.51$

$\Rightarrow$  move  $0.07j$  away from load

$\Rightarrow @ V_{min}, z_{in} = 0.33$

$$Z_{in} = (0.33)(50) \\ = 16.5 \Omega$$

$$Z_{\frac{1}{4}} = \sqrt{(16.5)(50)} \\ = 28.72 \Omega$$

$\Rightarrow$  move  $0.07j$  from load + attach  $\frac{1}{4}$  line with impedance  $28.72 \Omega$

check:  $\frac{16.5}{28.72} = 0.575$

$\hookrightarrow$  plot on chart + rotate  $\frac{1}{4}$

$\hookrightarrow z_{in} \sim 1.75$

$$Z_{in} = (1.75)(28.72)$$

$$= 50.26 \Omega \Rightarrow \text{close to } 50 \Omega \text{ target}$$

$V_{max}$

$z_L @ 0.43j$

$V_{max} @ 0.25j$

$\Rightarrow$  move  $0.32j$  from load

$\Rightarrow @ V_{max}, z_{in} = 3$

$$Z_{in} = 150$$

$$Z_{\frac{1}{4}} = \sqrt{(150)(50)} \\ = 86.6 \Omega$$

check:  $\frac{150}{86.6} = 1.73$

$\hookrightarrow$  plot  $1.73$  + rotate  $\frac{1}{4}$

$\Rightarrow 0.575$

$$Z_{in}' = (0.575)(86.6)$$

$$= 49.795 \Omega$$

$\hookrightarrow$  close to target



# Normalized Impedance Smith Chart

version 1.0  
2014-01-30



C) 3/4

