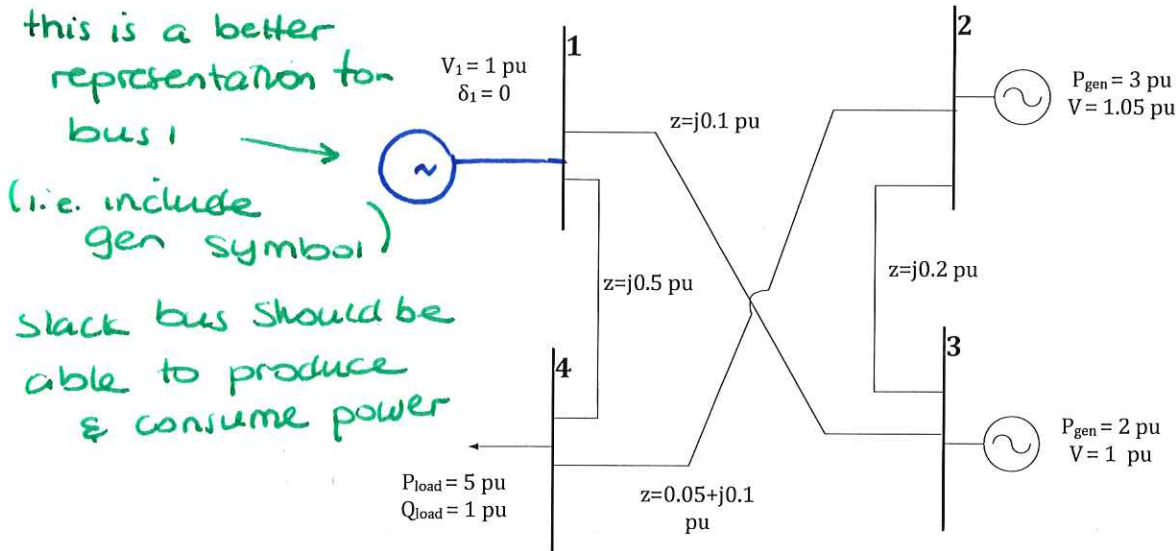


Tutorial 7

Consider the following system. The impedances (branches) between busses could represent lines or transformers in per unit.



- Identify bus types in this system
- Set up the X vector
- Set up Y_{bus}
- Write the equation f_1 (Real power flow equation at bus 1)

Power flow equations with Y_{bus} expressed in rectangular coordinates:

$$f_i = P_{\text{gen},i} - P_{\text{load},i} - \sum_{k=1}^N V_i V_k G[i, k] \cos(\delta_i - \delta_k) - \sum_{k=1}^N V_i V_k B[i, k] \sin(\delta_i - \delta_k)$$

$$f_{N+i} = Q_{\text{gen},i} - Q_{\text{load},i} - \sum_{k=1}^N V_i V_k G[i, k] \sin(\delta_i - \delta_k) + \sum_{k=1}^N V_i V_k B[i, k] \cos(\delta_i - \delta_k)$$

Tutorial 7

• We organize power flow equations as:

$$F(x) = \left[\begin{array}{c} f_i \\ \hline f_{N+i} \end{array} \right] \bigg\}^N = \left[\begin{array}{c} P_{\text{gen},i} \\ \hline Q_{\text{gen},i} \end{array} \right] \\ i = 1, \dots, N$$

• Bus type :

Bus #	type	unknown		
1	Slack	$P_{\text{gen},1}$	δ_1	$Q_{\text{gen},1}$
2	Gen/PV	δ_2	ϵ_2	$Q_{\text{gen},2}$
3	Gen/PV	δ_3	ϵ_3	$Q_{\text{gen},3}$
4	Non-gen	δ_4	ϵ_4	V_4

• $P_{\text{load},2} = Q_{\text{load},2} = 0$. Bus 2 would still be a gen bus even if $P_{\text{load},2}$ or $Q_{\text{load},2} \neq 0$. Same applies for bus 3.

• Bus 4 would still be a non-gen (load) bus even if $P_{\text{load},4} = Q_{\text{load},4} = 0$ (as long as there is no gen connected to it).

• The x vector is organized as follows:

$$x = \left[P_{\text{gen},1} \quad \delta_2 \quad \delta_3 \quad \delta_4 \quad | \quad Q_{\text{gen},1} \quad Q_{\text{gen},2} \quad Q_{\text{gen},3} \quad V_4 \right]^T$$

• Setting up Y_{bus} :

$$Y_{1,3} = \frac{1}{Z_{1,3}} = \frac{1}{j0.1} = -j10$$

$$Y_{1,4} = \frac{1}{Z_{1,4}} = \frac{1}{j0.5} = -j2$$

$$Y_{2,3} = \frac{1}{Z_{2,3}} = \frac{1}{j0.2} = -j5$$

$$Y_{2,4} = \frac{1}{Z_{2,4}} = \frac{1}{0.05 + j0.1} = 4 - j8$$

$$Y_{bus} = \begin{bmatrix} -j12 & 0 & +j10 & +j2 \\ 0 & 4-j13 & j5 & -4+j8 \\ j10 & j5 & -j15 & 0 \\ j2 & -4+j8 & 0 & 4-j10 \end{bmatrix}$$

↖ Σ of all admittances connected to bus 1

↖ $-Y_{1,4}$

therefore,

$$G_{bus} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 4 & 0 & -4 \\ 0 & 0 & 0 & 0 \\ 0 & -4 & 0 & 4 \end{bmatrix}$$

$$B_{bus} = \begin{bmatrix} -12 & 0 & 10 & 2 \\ 0 & -13 & 5 & 8 \\ 10 & 5 & -15 & 0 \\ 2 & 8 & 0 & -10 \end{bmatrix}$$

no j in the matrix!

$$Y = G + jB$$

f_1 : real power flow eq at bus 1

$$\begin{aligned} f_1 = P_{\text{eqn},1} &= P_{\text{gen},1} - P_{\text{load},1} - V_1 V_1 G[1,1] \cos(\delta_1 - \delta_1) \\ &\quad - V_1 V_2 G[1,2] \cos(\delta_1 - \delta_2) - V_1 V_3 G[1,3] \cos(\delta_1 - \delta_3) \\ &\quad - V_1 V_4 G[1,4] \cos(\delta_1 - \delta_4) - V_1 V_1 B[1,1] \sin(\delta_1 - \delta_1) \\ &\quad - V_1 V_2 B[1,2] \sin(\delta_1 - \delta_2) - V_1 V_3 B[1,3] \sin(\delta_1 - \delta_3) \\ &\quad - V_1 V_4 B[1,4] \sin(\delta_1 - \delta_4) \end{aligned}$$

unknowns in red

$$= P_{\text{gen},1} - (1)(1)(10) \sin(0 - \delta_3) - (1)V_4(2) \sin(0 - \delta_4)$$

$$= P_{\text{gen},1} - 10 \sin(-\delta_3) - 2V_4 \sin(-\delta_4)$$

To complete the mismatch vector, repeat this for bus 2-4
& also write Q_{eqn} for bus 1-4 (f_5 to f_8)

mismatch vector

$$F(x) = \begin{bmatrix} P_{\text{gen},1} - 10 \sin(-\delta_3) - 2V_4 \sin(-\delta_4) \\ \vdots \end{bmatrix}$$

we can not write this as $A \cdot x = B$ (linear sys of equations).

So, start with an initial guess/estimate for x :

$$x^0 = \begin{bmatrix} 0 & 0 & 0 & 0 & \vdots & 0 & 0 & 0 & 1 \end{bmatrix}^T$$

flat start : Set unknown $V = 1$ pu

" $\delta = 0^\circ$

" $P_{\text{gen}}, Q_{\text{gen}} = 0$ pu

- then,
- Calculate $F(x^0)$. Likely $\|F(x^0)\| \neq 0$
 - improve x^0 by using the update term from NR
come up with new vector x^1 .
 - Repeat until we find optimal solution x^* .