

### **ENEL 476 – Assignment #3**

**Due on Thurs April 6 at 4 pm**

**Drop boxes on 2<sup>nd</sup> floor of ICT**

An antenna with impedance  $Z_L = 72 - j43 \, \Omega$  is connected to a lossless transmission line with impedance  $Z_0 = 75 \, \Omega$ . Use the Smith Chart to solve the following problems.

- a) Plot the normalized impedance,  $z_L$
- b) Find the reflection coefficient,  $\Gamma$ .
- c) Find the standing wave ratio (VSWR, SWR or s).
- d) Find the shortest distances from the antenna to the location of the voltage maximum ( $V_{\max}$ ) and voltage minimum ( $V_{\min}$ ) on the transmission line.
- e) Indicate the locations of the short and open on the Smith Chart.
- f) The antenna is connected to transmission line of length of  $0.625\lambda$ . What is  $Z_{\text{in}}$  at this location?
- g) A generator supplies 20 V and has internal impedance of  $Z_g = 75 \, \Omega$ . How much power is absorbed by the load connected to the generator and the  $0.625\lambda$  line?