

## Assignment 1 Solution

**2.1** (a)  $\bar{A}_1 = 5\angle 30^\circ = 5[\cos 30^\circ + j \sin 30^\circ] = 4.33 + j 2.5$

(b)  $\bar{A}_2 = -3 + j4 = \sqrt{9+16} \angle \tan^{-1} \frac{4}{-3} = 5\angle 126.87^\circ = 5e^{j126.87^\circ}$

(c)  $\bar{A}_3 = (4.33 + j2.5) + (-3 + j4) = 1.33 + j6.5 = 6.635\angle 78.44^\circ$

(d)  $\bar{A}_4 = (5\angle 30^\circ)(5\angle 126.87^\circ) = 25\angle 156.87^\circ = -22.99 + j9.821$

(e)  $\bar{A}_5 = (5\angle 30^\circ)/(5\angle -126.87^\circ) = 1\angle 156.87^\circ = 1e^{j156.87^\circ}$

**2.2** (a)  $\bar{I} = 400\angle -30^\circ = 346.4 - j200$

(b)  $i(t) = 5\sin(\omega t + 15^\circ) = 5\cos(\omega t + 15^\circ - 90^\circ) = 5\cos(\omega t - 75^\circ)$

$$\bar{I} = (5/\sqrt{2})\angle -75^\circ = 3.536\angle -75^\circ = 0.9151 - j3.415$$

(c)  $\bar{I} = (4/\sqrt{2})\angle -30^\circ + 5\angle -75^\circ = (2.449 - j1.414) + (1.294 - j4.83)$   
 $= 3.743 - j6.244 = 7.28\angle -59.06^\circ$


**2.4** (a)  $\bar{I}_1 = 10\angle 0^\circ \frac{-j6}{8 + j6 - j6} = 10 \frac{6\angle -90^\circ}{8} = 7.5\angle -90^\circ \text{ A}$

From Current division

$\bar{I}_2 = \bar{I} - \bar{I}_1 = 10\angle 0^\circ - 7.5\angle -90^\circ = 10 + j7.5 = 12.5\angle 36.87^\circ \text{ A}$

$\bar{V} = \bar{I}_2(-j6) = (12.5\angle 36.87^\circ)(6\angle -90^\circ) = 75\angle -53.13^\circ \text{ V}$

(b)

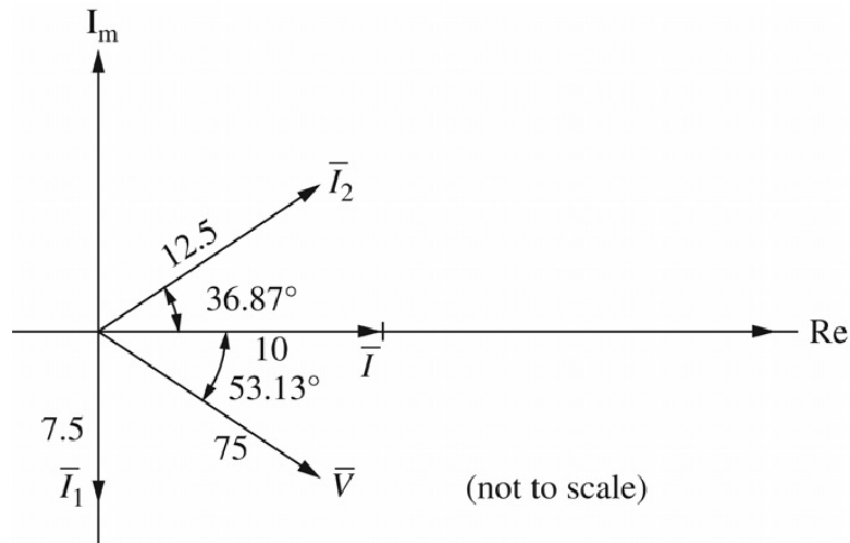


**2.15** (a)  $\bar{I} = \left[ \left( 4/\sqrt{2} \right) \angle 60^\circ \right] / (2 \angle 30^\circ) = \sqrt{2} \angle 30^\circ \text{ A}$

$$i(t) = 2 \cos(\omega t + 30^\circ) \text{ A with } \omega = 377 \text{ rad/s}$$


$$\begin{aligned} p(t) &= v(t)i(t) = 4 \left[ \cos 30^\circ + \cos(2\omega t + 90^\circ) \right] \\ &= 3.46 + 4 \cos(2\omega t + 90^\circ) \text{ W} \end{aligned}$$

(b)  $v(t)$ ,  $i(t)$ , and  $p(t)$  are plotted below: (See next page)

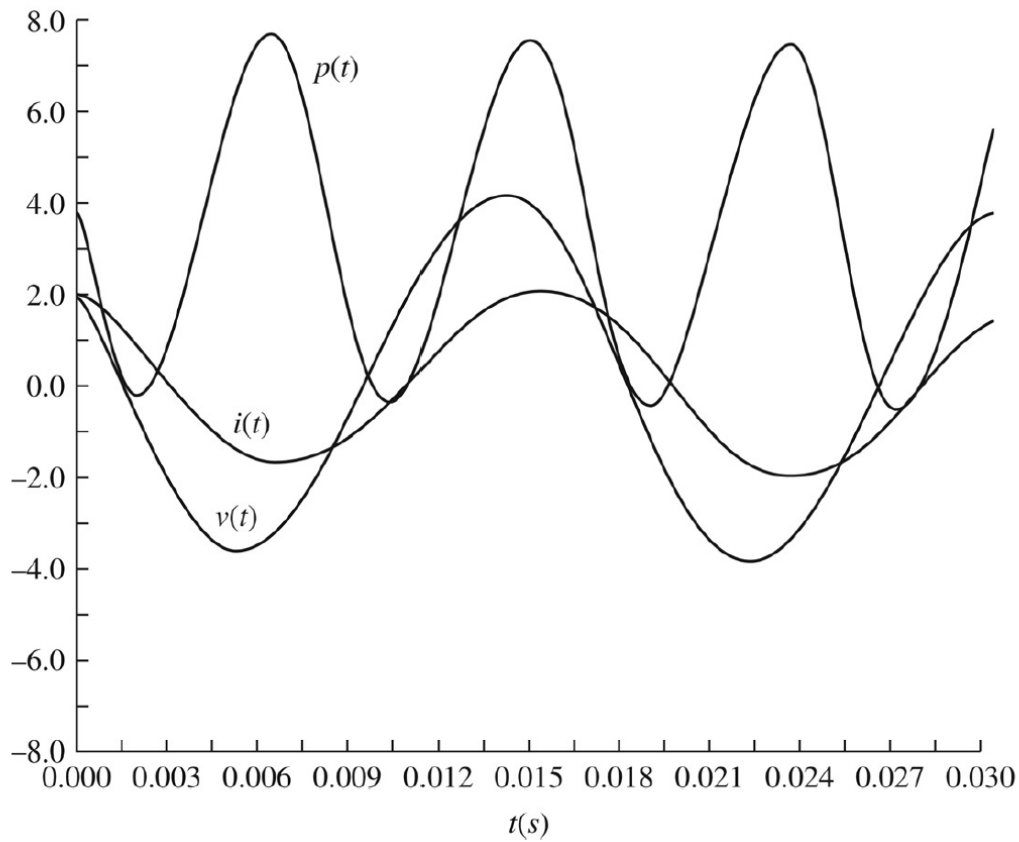(c) The instantaneous power has an average value of 3.46 W, and the frequency is twice that of the voltage or current.



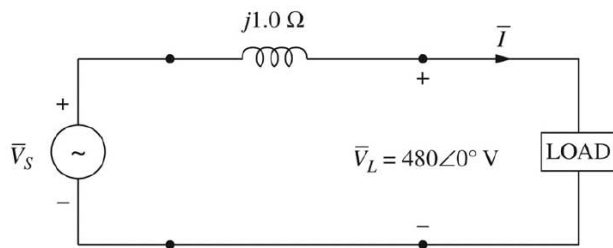**2.26** (a) The problem is modeled as shown in figure below:



$$P_L = 120 \text{ kW}$$


$$pf_L = 0.85 \text{ Lagging}$$

$$\theta_L = \cos^{-1} 0.85 = 31.79^\circ$$

Power triangle for the load:

$$\bar{S}_L = P_L + jQ_L = 141.18 \angle 31.79^\circ \text{ kVA}$$
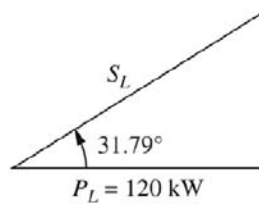
$$I = S_L / V = 141,180 / 480 = 294.13 \text{ A}$$



$$Q_L = P_L \tan(31.79^\circ)$$

$$= 74.364 \text{ kVAR}$$

Real power loss in the line is zero.

$$\text{Reactive power loss in the line is } Q_{LINE} = I^2 X_{LINE} = (294.13)^2 1 \\ = 86.512 \text{ kVAR}$$

$$\therefore \bar{S}_s = P_s + jQ_s = 120 + j(74.364 + 86.512) = 200.7 \angle 53.28^\circ \text{ kVA}$$

The input voltage is given by  $V_s = S_s / I = 682.4 \text{ V (rms)}$

The power factor at the input is  $\cos 53.28^\circ = 0.6$  Lagging

$$(b) \text{ Applying KVL, } \bar{V}_s = 480 \angle 0^\circ + j1.0(294.13 \angle -31.79^\circ)$$

$$= 635 + j250 = 682.4 \angle 21.5^\circ \text{ V (rms)}$$

$$(pf)_s = \cos(21.5^\circ + 31.79^\circ) = 0.6 \text{ Lagging}$$

$$\text{Pf} = \cos(\text{voltage angle} - \text{current angle})$$

**2.30** (a) For load 1:  $\theta_1 = \cos^{-1}(0.28) = 73.74^\circ$  Lagging

$$\bar{S}_1 = 125 \angle 73.74^\circ = 35 + j120$$

$$\bar{S}_2 = 10 - j40$$

$$\bar{S}_3 = 15 + j0$$

$$\bar{S}_{TOTAL} = \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = 60 + j80 = 100 \angle 53.13^\circ \text{ kVA} = P + jQ$$

$$\therefore P_{TOTAL} = 60 \text{ kW}; Q_{TOTAL} = 80 \text{ kVAR}; \text{ kVA}_{TOTAL} = S_{TOTAL} = 100 \text{ kVA.} \leftarrow$$

$$\text{Supply } pf = \cos(53.13^\circ) = 0.6 \text{ Lagging} \leftarrow$$

$$(b) \bar{I}_{TOTAL} = \frac{\bar{S}^*}{\bar{V}^*} = \frac{100 \times 10^3 \angle -53.13^\circ}{1000 \angle 0^\circ} = 100 \angle -53.13^\circ \text{ A}$$

At the new  $pf$  of 0.8 lagging,  $P_{TOTAL}$  of 60kW results in the new reactive power  $Q'$ , such that

$$\theta' = \cos^{-1}(0.8) = 36.87^\circ$$

and  $Q' = 60 \tan(36.87^\circ) = 45 \text{ kVAR}$

$\therefore$  The required capacitor's kVAR is  $Q_C = 80 - 45 = 35 \text{ kVAR} \leftarrow$

It follows then  $X_C = \frac{V^2}{\bar{S}_C^*} = \frac{(1000)^2}{j35000} = -j28.57 \Omega$

and  $C = \frac{10^6}{2\pi(60)(28.57)} = 92.85 \mu\text{F} \leftarrow$

The new current is  $I' = \frac{\bar{S}^*}{\bar{V}^*} = \frac{60,000 - j45,000}{1000 \angle 0^\circ} = 60 - j45 = 75 \angle -36.87^\circ \text{ A}$

The supply current, in magnitude, is reduced from 100A to 75A  $\leftarrow$

Addition of capacitor bank and “correction of power factor” closer to unity resulted in lower current through the transmission lines, which translates to lower losses in the lines.

**2.40** (a)  $\bar{V}_{AN} = \frac{208}{\sqrt{3}} \angle 0^\circ = 120.1 \angle 0^\circ \text{ V}$  (Assumed as Reference)

$$\bar{V}_{AB} = 208 \angle 30^\circ \text{ V}; \bar{V}_{BC} = 208 \angle -90^\circ \text{ V}; \bar{I}_A = 10 \angle -90^\circ \text{ A}$$


$$\bar{Z}_Y = \frac{\bar{V}_{AN}}{\bar{I}_A} = \frac{120.1 \angle 0^\circ}{10 \angle -90^\circ} = 12.01 \angle +90^\circ = (0 + j12.01) \Omega$$

(b)  $\bar{I}_{AB} = \frac{\bar{I}_A}{\sqrt{3}} \angle 30^\circ = \frac{10}{\sqrt{3}} \angle -90^\circ + 30^\circ = 5.774 \angle -60^\circ \text{ A}$

$$\bar{Z}_\Delta = \frac{\bar{V}_{AB}}{\bar{I}_{AB}} = \frac{208 \angle 30^\circ}{5.774 \angle -60^\circ} = 36.02 \angle 90^\circ = (0 + j36.02) \Omega$$

Note:  $\bar{Z}_Y = \bar{Z}_\Delta / 3$

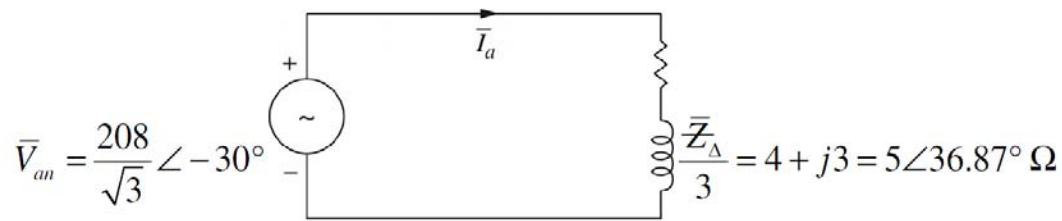**2.42** (a) With  $\bar{V}_{ab}$  as reference




$$\bar{I}_a = \frac{\bar{V}_{an}}{(\bar{Z}_\Delta / 3)} = \frac{120.1 \angle -30^\circ}{5 \angle 36.87^\circ} = 24.02 \angle -66.87^\circ \text{ A}$$

$$\begin{aligned} \bar{S}_{3\phi} &= 3\bar{V}_{an}\bar{I}_a^* = 3(120.1 \angle -30^\circ)(24.02 \angle +66.87^\circ) \\ &= 8654 \angle 36.87^\circ = 6923 + j5192 \end{aligned}$$

$P_{3\phi} = 6923 \text{ W}$ ;  $Q_{3\phi} = 5192 \text{ VAR}$ ; both absorbed by the load


$$pf = \cos(36.87^\circ) = 0.8 \text{ Lagging}; S_{3\phi} = |\bar{S}_{3\phi}| = 8654 \text{ VA}$$

(b)

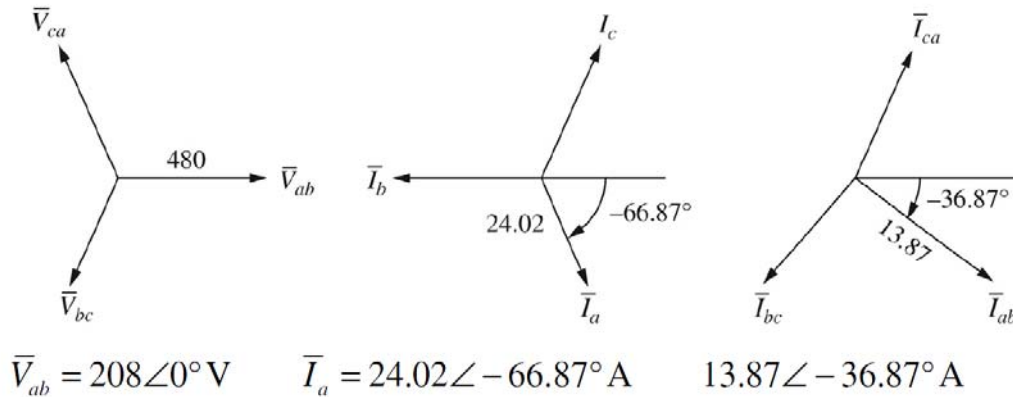

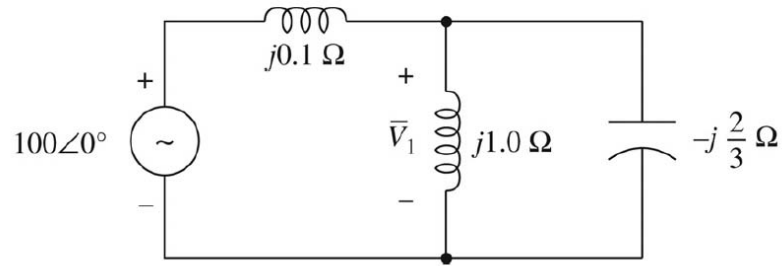**2.50** Replace delta by the equivalent WYE:  $\bar{Z}_Y = -j\frac{2}{3}\Omega$

Per-phase equivalent circuit is shown below:



Noting that  $\left(j1.0 \parallel -j\frac{2}{3}\right) = -j2$ , by voltage-divider law,

$$\bar{V}_1 = \frac{-j2}{-j2 + j0.1}(100\angle 0^\circ) = 105\angle 0^\circ$$

$$\therefore v_1(t) = 105\sqrt{2} \cos(\omega t + 0^\circ) = 148.5 \cos \omega t \text{ V} \quad \leftarrow$$

In order to find  $i_2(t)$  in the original circuit, let us calculate  $\bar{V}_{A'B'}$

$$\bar{V}_{A'B'} = \bar{V}_{A'N'} - \bar{V}_{B'N'} = \sqrt{3} e^{j30^\circ} \bar{V}_{A'N'} = 181.8 \angle 30^\circ$$

Then

$$\bar{I}_{A'B'} = \frac{181.8 \angle 30^\circ}{-j2} = 90.9 \angle 120^\circ$$

$$\begin{aligned} \therefore i_2(t) &= 90.9 \sqrt{2} \cos(\omega t + 120^\circ) \\ &= 128.6 \cos(\omega t + 120^\circ) \text{ A} \quad \leftarrow \end{aligned}$$