

Tutorial 3

A transmission line with impedance of $0.6+j3\ \Omega$ per phase connects a Y-connected generator to 3 loads in parallel:

- Load 1 draws 165 kW and 117 kVAr (or 202.3 kVA and 0.81 lagging power factor)
- Load 2: delta-connected, $Z = 144-j42\ \Omega$
- Load 3: Y-connected, $Z = j26\ \Omega$

Line-to-neutral voltage at the load end is 2600 V. Find:

- a) Phase current of the source
- b) Line-to-line voltage at the source
- c) $V_{an}(t)$ in Load 3
- d) Instantaneous phase current in Load 2
- e) Power absorbed by Load 3