

Then,

$$C_{an} = \frac{2\pi\epsilon}{\ln \frac{D}{D_{sc}}}$$

for symm alignment

$$C_{an} = \frac{2\pi\epsilon}{\ln \frac{D_{eq}}{D_{sc}}}$$


for asymm alignment with transposition

where  $D$  is the distance between bundle centers

charging current was the last concept in Topic 5, Part 1. We didn't get to cover it in Week 7

• Current supplied to line capacitance is charging current
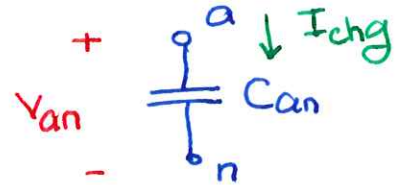
$$\bar{I}_{chg} = \frac{\bar{V}_{an}}{Z_c} = \frac{\bar{V}_{an}}{\frac{1}{j\omega C_{an}}} = j\omega \cdot C_{an} \cdot \bar{V}_{an}$$




$$Q_{chg} = \frac{V_{an}^2}{X_{cap}} = \frac{V_{an}^2}{\frac{-1}{\omega \cdot C_{an}}} = -\omega \cdot C_{an} \cdot V_{an}^2$$

reactive power from  $C_{an}$
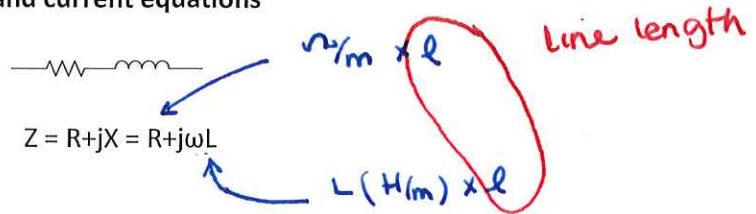
## Transmission line voltage and current equations

Transmission line models used in previous topics looked like:




We ignored the line capacitance in these models.

In part 1 of topic 5, we came up with equations to calculate the distributed inductance (H/m) and distributed capacitance (F/m)

Objective of part 2: Determine how to model (lump) this all together.

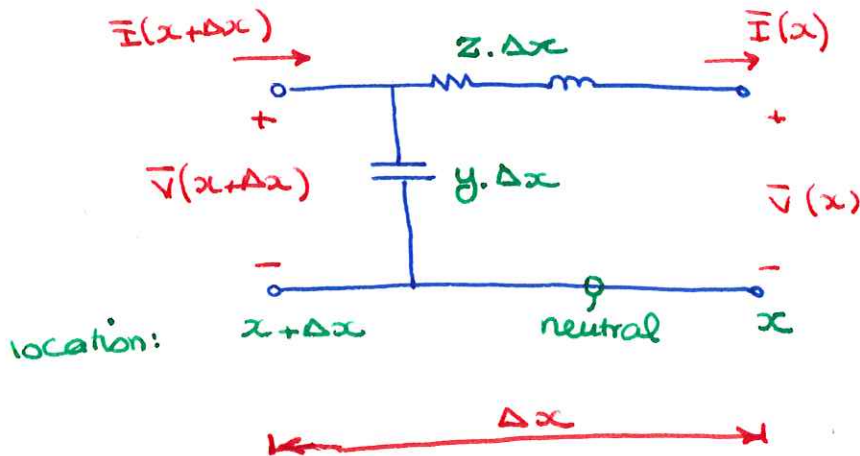Consider a small portion of the line with length  $\Delta x$ :



lower case  
 $z = R + j\omega L$  where:  
 $R$  is in  $\Omega/m$  &  
 $L$  is in  $H/m$

lower case  
 $y = j\omega C$  where  
 $C$  is in  $F/m$

From KVL:  $V(x + \Delta x) = V(x) + z \cdot \Delta x \cdot I(x)$

Therefore:  $\lim_{\Delta x \rightarrow 0} \frac{V(x + \Delta x) - V(x)}{\Delta x} = z \cdot I(x)$

$$\frac{dV(x)}{dx} = z \cdot I(x) \quad (i)$$

From KCL:  $I(x + \Delta x) = I(x) + V(x + \Delta x) y \cdot \Delta x$

Therefore:  $\lim_{\Delta x \rightarrow 0} \frac{I(x + \Delta x) - I(x)}{\Delta x} = y \cdot V(x + \Delta x)$

$$\frac{dI(x)}{dx} = y \cdot V(x) \quad (ii)$$

Solve DEQ from

combining (i) & (ii) to get:  $V(x) = K_1 \cdot \cosh(\gamma x) + K_2 \cdot \sinh(\gamma x)$  where  $\gamma = \sqrt{y \cdot z}$  propagation constant (1/m)

If we know  $\bar{V}$  and  $\bar{I}$  at one end, e.g. receiving end ( $x=0$ ):  $V_R = V(0)$  and  $I_R = I(0)$ , we can find  $K_1$  and  $K_2$ :

$$V(x) = V_R \cdot \cosh(\gamma x) + I_R Z_c \cdot \sinh(\gamma x) \quad (1)$$

where  $Z_c = \sqrt{z/y}$  characteristic impedance ( $\Omega$ )

Similar derivation for  $I(x)$  gives:  $I(x) = I_R \cdot \cosh(\gamma x) + \frac{V_R}{Z_c} \cdot \sinh(\gamma x) \quad (2)$

Eq (1) and (2) give us voltage and current at any point  $x$  along the line ( $x$  is the distance from the receiving end)

Note: voltage and current in above expressions are phasors.

• addition to the "Transmission Line Eq" handout:

combining (i) & (ii) gives us 2<sup>nd</sup> order DEQ:  $\frac{d^2 \bar{V}(x)}{dx^2} - Z \cdot Y \cdot \bar{V}(x) = 0$


## Transmission Line Models

• we are often interested in terminal characteristics of the line:

$$\bar{V}_R, \bar{I}_R, \bar{V}_S, \bar{I}_S$$

↑  
↑  
Sending end

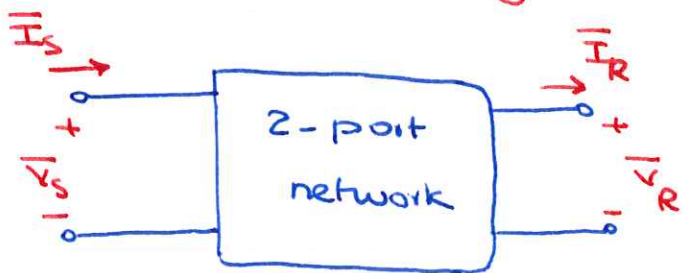• don't care about  $\bar{V}(x)$  &  $\bar{I}(x)$   
for  $x$  between two terminals




where:

$$\begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \bar{V}_R \\ \bar{I}_R \end{bmatrix}$$

$$\begin{cases} \bar{V}_S = A \cdot \bar{V}_R + B \cdot \bar{I}_R \\ \bar{I}_S = C \cdot \bar{V}_R + D \cdot \bar{I}_R \end{cases}$$

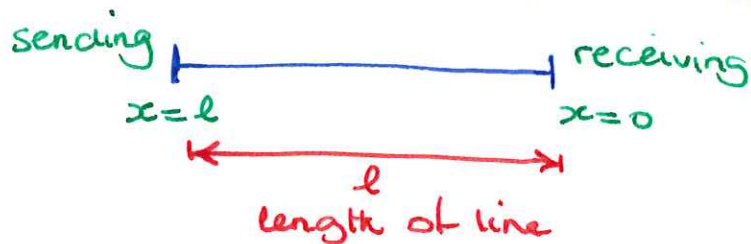need to find ABCD parameters for transmission lines! Let's use  $\bar{V}(x)$  and  $\bar{I}(x)$  equations



$$\bar{V}_S = \bar{V}(x) \Big|_{x=l} \stackrel{\text{eq(1)}}{=} \underbrace{\cosh(\gamma l)}_A \cdot \bar{V}_R + \underbrace{Z_c \sinh(\gamma l)}_B \cdot \bar{I}_R$$

$$\bar{I}_S = \bar{I}(x) \Big|_{x=l} \stackrel{\text{eq(2)}}{=} \underbrace{\cosh(\gamma l)}_D \cdot \bar{I}_R + \underbrace{\frac{1}{Z_c} \sinh(\gamma l)}_C \cdot \bar{V}_R$$


$$\therefore \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_c \sinh(\gamma l) \\ \frac{1}{Z_c} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

• These are the exact ABCD parameters for two-port network representation of a line.



- For modelling lines in simulations/circuit analysis, need to model the line using circuit elements. Common representation is

Equivalent  $\pi$  Model:

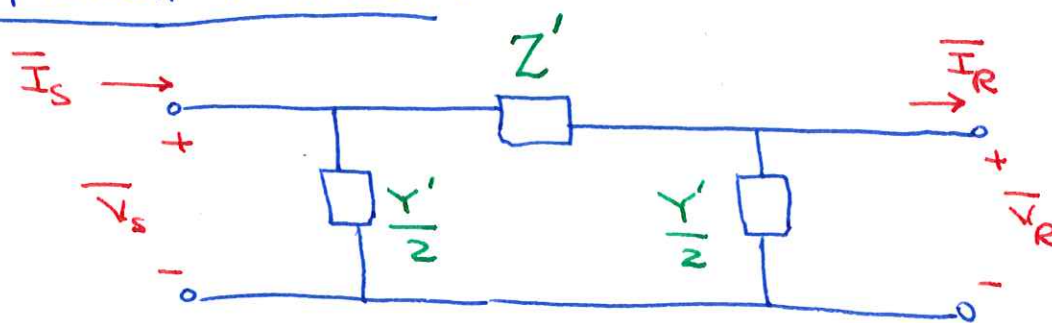

notice upper case  $Z$  &  $Y$ .

objective: find  $Z'$  &  $Y'$  such that this model has the same behaviour as the 2-port network?

- skipping the derivation (writing KCL & KVL for eq  $\pi$  model and equating  $V_s$  &  $I_s$  equations with 2-port network)

$$Z' = Z \cdot \frac{\sinh(\gamma l)}{\gamma l}$$

where  $Z = z \cdot l$

↑  
total impedance


↑  
distributed impedance  
( $\Omega/m$ )

$$\frac{Y'}{2} = \frac{Y}{2} \frac{\tanh(\frac{\gamma l}{2})}{\frac{\gamma l}{2}}$$

where  $Y = y \cdot l$

↑  
distributed admittance

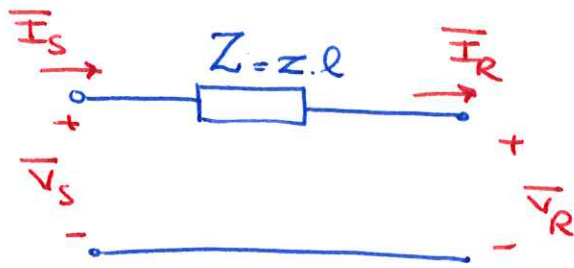
• For short lines ( $l < 80 \text{ km}$ ), use  $Z' = Z$  &  $\frac{Y'}{2} = 0$



$$\begin{cases} \bar{V}_S = Z \cdot \bar{I}_R + \bar{V}_R \\ \bar{I}_S = \bar{I}_R \end{cases} \quad \text{from KVL} \quad \therefore \begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \bar{V}_R \\ \bar{I}_R \end{bmatrix}$$

ABCD parameters for short lines

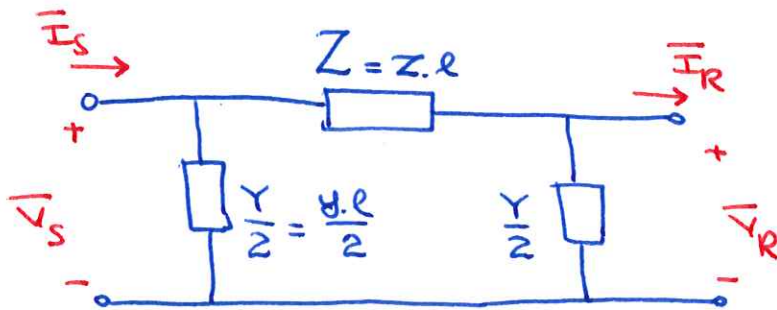• For medium lines ( $80 < l < 250 \text{ km}$ ) use  $Z' = Z$  &  $\frac{Y'}{2} = \frac{Y}{2}$




Nominal  $\pi$  Circuit

by using KVL & KCL, we can arrive at ABCD parameters for this model

$$\begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix} = \begin{bmatrix} 1 + \frac{YZ}{2} & Z \\ Y(1 + \frac{YZ}{4}) & 1 + \frac{YZ}{2} \end{bmatrix} \begin{bmatrix} \bar{V}_R \\ \bar{I}_R \end{bmatrix}$$

ABCD parameters for medium lines

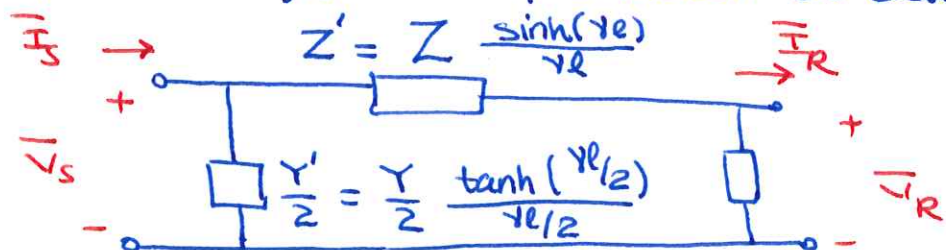
• For long lines ( $l > 250 \text{ km}$ ), use Eq.  $\pi$  model as defined previously.




## Tutorial 6

### Problems 1-2 are from Topic 5 - Part 1 (Transmission line parameters)

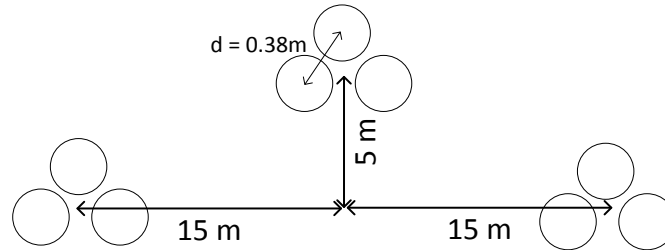**Problem 1:** Find resistance per phase, inductance per phase and current carrying capacity (ampacity) per phase for 275km long Conдор conductor in the following configuration. R is  $0.072 \Omega/\text{km}$ .



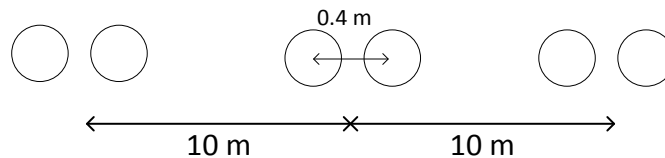**Problem 2:** Figure below shows the conductor configuration of a completely transposed, three phase, 345 kV, 60 Hz transmission line with a two conductor bundle of 795 kcmil conductors. Bundle spacing is 0.4 m. Flat horizontal spacing is retained, with 10 m between adjacent bundle centers. Length of line is 200 km. (GMR of a 795 kcmil conductor is 0.0114 m, and radius of conductor is 0.0141m.)



- a) Calculate the total capacitance-to-neutral of one phase in F and the admittance-to-neutral in S.
- b) If the line voltage is 345 kV, determine the charging current in kA per phase and the total (three phase) reactive power in MVar supplied by the line capacitance.

### The following problems are from Topic 5 - Part 2 (Transmission line models).

**Problem 3:** 765 kV rated line.  $V_R = 765 \text{ kV}$  (line to line).  $S_R = 2000 + j1000 \text{ MVA}$ .  $z = 0.0201 + j0.535 \Omega/\text{km}$ ,  $y = j7.75 \times 10^{-6} \text{ S/km}$ . Write the expression for  $V(x)$ .

**Problem 4:** 500 kV rated line.  $R = 0.02 \Omega/\text{km}$ ,  $x = 0.335 \Omega/\text{km}$ ,  $y = j4.807 \times 10^{-6} \text{ S/km}$ , length = 300 km. Find  $Z_c$ ,  $\gamma l$ , exact ABCD parameters, equivalent  $\pi$  model.

## Tutorial 6

1) From table A.4,  $D_s = 0.0368$  ft, ampacity = 900 A  
 $= 0.912$  m

R : 3 conductors per phase connected in parallel.

$$\therefore R_{eq} = \frac{1}{\frac{1}{0.072} + \frac{1}{0.072} + \frac{1}{0.072}} = \frac{0.072}{3} = 0.024 \text{ } \Omega/\text{km}$$


$$R_{total} = R_{eq} \times 275 \text{ km} = 6.6 \text{ } \Omega$$

L :  $L = 2 \times 10^{-7} \ln \frac{D_{eq}}{D_{SL}}$

where  $D_{eq} = \sqrt[3]{D_{xy} \cdot D_{yz} \cdot D_{xz}}$

$\uparrow \quad \quad \uparrow \quad \quad \uparrow$   
 $\sqrt{15^2 + 5^2} \quad 30 \text{ m}$

$= 19.57 \text{ m}$

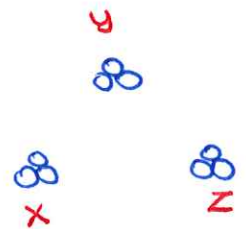

$$D_{SL} = \sqrt[3]{D_s \cdot d^2} = \sqrt[3]{0.912 \times (0.38)^2} = 0.1174 \text{ m}$$

$$\therefore L = 2 \times 10^{-7} \ln \frac{19.57}{0.1174} = 1.02 \times 10^{-6} \text{ H/m}$$

total inductance  $L_{total} = L \times 275 \text{ 000} = 0.28 \text{ H}$

total reactance  $X_{total} = \omega \cdot L = (2\pi \times 60) \times L = 106.08 \text{ } \Omega$   
(not needed) ↑  
assumed N. American

ampacity : 3 conductors per bundle  $\therefore$  total ampacity per phase  
 $= 2700 \text{ A}$



$$2) \quad C_{an} = \frac{2\pi\epsilon}{\ln \frac{D_{eq}}{D_{sc}}} \quad (F/m)$$

$$\text{where } D_{eq} = \sqrt[3]{10 \times 10 \times 20}$$


$$D_{sc} = \sqrt{r \cdot d} = \sqrt{0.0141 \times 0.4} = 0.075 \text{ m}$$

$$C_{an\_total} = C_{an} \times 200\,000 = \frac{2\pi \times 8.85 \times 10^{-12}}{\ln \frac{12.6}{0.075}} \times 200\,000$$

$$= 2.17 \times 10^{-6} \text{ F}$$

$$Y_{an\_total} = j \omega C_{an\_total} = j (2\pi \times 60) (2.17 \times 10^{-6}) = j 8.19 \times 10^{-4} \text{ S}$$

part b).

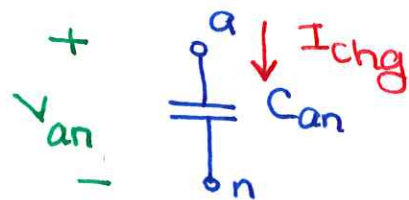

$$I_{chg} = \frac{V_{an}}{Z_{cap}} = V_{an} \cdot Y_{cap}$$

$$= \frac{345 \text{ kV}}{\sqrt{3}} \cdot (8.19 \times 10^{-4}) = 0.163 \text{ kA}$$

$$Q_{chg, 3\phi} = 3 \times Q_{chg, 1\phi} = 3 \left( V_{an}^2 \cdot B_{an\_total} \right)$$

$$= 3 \left( \frac{345 \text{ kV}}{\sqrt{3}} \right)^2 \cdot (8.19 \times 10^{-4}) = 97.5 \text{ mVar}$$

$$\frac{1}{j\omega C} \quad Z_c = \frac{1}{j\omega C} = \cancel{R + jX}$$

$$Y_c = j\omega C = \cancel{G + jB}$$

$$Q = I^2 \cdot X = \frac{V^2}{X}$$

$$= \frac{I^2}{B} = V^2 \cdot B$$

Since  $R=G=0$   
 $X = \frac{1}{B}$



$$3) \quad \bar{V}(x) = \bar{V}_R \cdot \cosh(\gamma x) + \bar{I}_R \cdot Z_c \cdot \sinh(\gamma x)$$

$\uparrow$  given       $\uparrow$  need to calculate       $\uparrow$  need to calculate based on  $\bar{V}_R$  &  $\bar{S}_R$        $\nwarrow$  need to calculate

$$\gamma = \sqrt{Z \cdot y} = \sqrt{4.15 \times 10^{-6} \angle 177.8^\circ} = 2.036 \times 10^{-3} \angle 88.9^\circ \quad 1/\text{km}$$

$\swarrow$  of magnitude       $\searrow$  divide phase by 2

$$Z_c = \sqrt{\frac{Z}{y}} = 262.7 \angle -1.1^\circ \quad \Omega$$

$$V_R = \frac{765 \text{ kV}}{\sqrt{3}} = 441.7 \text{ kV}$$

$\leftarrow \bar{V}_R, \bar{V}_S, \bar{V}(x)$  are line-to-neutral quantities in line models

$$\bar{V}_R = 441.7 \angle 0^\circ \text{ kV}$$

$\uparrow$  arbitrarily assigned

$$\bar{S}_{R_{10}} = \bar{V}_{R_{l-n}} \cdot \bar{I}_R^* \quad \therefore \bar{I}_R = \frac{\bar{S}_{R_{10}}^*}{\bar{V}_{R_{l-n}}^*} = \frac{\frac{1}{3} (2000 + j1000)^*}{441.7 \angle 0^\circ} = 1688 \angle -26.6^\circ$$

Finally, 
$$\bar{V}(x) = 441.7 \angle 0^\circ \cosh(2.036 \times 10^{-3} \angle 88.9^\circ \cdot x) + 443.44 \angle -27.7^\circ \sinh(2.036 \times 10^{-3} \angle 88.9^\circ \cdot x)$$

this is the line-to-neutral voltage in kV at any point  $x$  measured from receiving end.

$$4) Z = R + jX = 0.02 + j 0.335 = 0.336 \angle 86.6^\circ \quad \Omega/\text{km}$$

$$Y = j 4.807 \times 10^{-6} \text{ S/km} = 4.807 \times 10^{-6} \angle 90^\circ \text{ S/km}$$

$$Z_c = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{0.336 \angle 86.6^\circ}{4.807 \times 10^{-6} \angle 90^\circ}} = 264.4 \angle -1.7^\circ \quad \Omega$$

$$\gamma \cdot l = \sqrt{Z \cdot Y} \cdot l = 0.0113 + j 0.381$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_c \sinh(\gamma l) \\ \frac{1}{Z_c} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

$$A = D = \cosh(\gamma l) = \cosh(0.0113 + j 0.381)$$

$$\text{using } \cosh(\alpha + j\beta) = \cosh(\alpha) \cdot \cos(\beta) + j \sinh(\alpha) \cdot \sin(\beta),$$

$$\begin{aligned} A = D &= \cosh(0.0113) \cdot \cos(0.381) + j \sinh(0.0113) \cdot \sin(0.381) \\ &= 0.9285 + j 0.00418 \\ &= 0.9285 \angle 0.26^\circ \end{aligned}$$


$$B = Z_c \sinh(\gamma l) = 264.4 \angle -1.7^\circ \sinh(0.0113 + j 0.381)$$

$$\text{using } \sinh(\alpha + j\beta) = \sinh(\alpha) \cdot \cos(\beta) + j \cosh(\alpha) \cdot \sin(\beta),$$

$$\begin{aligned} B &= 264.4 \angle -1.7^\circ (0.3716 \angle 88.39^\circ) \\ &= 98.25 \angle 86.69^\circ \quad \Omega \end{aligned}$$

$$C = \frac{1}{Z_c} \sinh(\gamma l) = 1.405 \times 10^{-3} \angle 90.09^\circ \text{ S}$$

Eq  $\pi$  model :

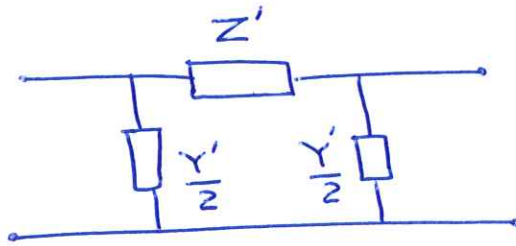

$$Z' = Z \cdot \frac{\sinh(\gamma l)}{\gamma l} = 98.26 \angle 86.69^\circ$$

$$Z \cdot l = (0.336 \angle 86.6^\circ) \times 300$$

$$\frac{Y'}{2} = \left( \frac{Y}{2} \right) \frac{\tanh\left(\frac{\gamma l}{2}\right)}{\frac{\gamma l}{2}} = 6.37 \times 10^{-7} + j 7.3 \times 10^{-4} \text{ S}$$

$$Y \cdot l = (j 4.807 \times 10^{-6}) \times 300$$