

Set 1 - extra problems

Solutions to the following problem from the text book are provided here:

**Topic 1:** 2.13, 2.22, 2.24, 2.28,

**Topic 2:** 2.44, 2.46, 2.52

$$\mathbf{2.13} \quad \bar{Z} = R - jX_c = 10 - j25 = 26.93 \angle -68.2^\circ \Omega$$

$$\begin{aligned} i(t) &= (359.3/26.93) \cos(\omega t + 68.2^\circ) \\ &= 13.34 \cos(\omega t + 68.2^\circ) \text{ A} \end{aligned}$$

$$\begin{aligned} \text{(a)} \quad p_R(t) &= [13.34 \cos(\omega t + 68.2^\circ)] [133.4 \cos(\omega t + 68.2^\circ)] \\ &= 889.8 + 889.8 \cos[2(\omega t + 68.2^\circ)] \text{ W} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad p_x(t) &= [13.34 \cos(\omega t + 68.2^\circ)] [333.5 \cos(\omega t + 68.2^\circ - 90^\circ)] \\ &= 2224 \sin[2(\omega t + 68.2^\circ)] \text{ W} \end{aligned}$$

$$\text{(c)} \quad P = I^2 R = (13.34/\sqrt{2})^2 10 = 889.8 \text{ W}$$

$$\text{(d)} \quad Q = I^2 X = (13.34/\sqrt{2})^2 25 = 2224 \text{ VAR S}$$

$$\begin{aligned} \text{(e)} \quad pf &= \cos[\tan^{-1}(Q/P)] = \cos[\tan^{-1}(2224/889.8)] \\ &= 0.3714 \text{ Leading} \end{aligned}$$

$$\begin{aligned} 2.22 \quad (a) \quad \bar{Y}_1 &= \frac{1}{\bar{Z}_1} = \frac{1}{(4 + j5)} = \frac{1}{6.4 \angle 51.34^\circ} = 0.16 \angle -51.34^\circ \\ &= (0.1 - j0.12) \text{ S} \end{aligned}$$

$$\bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{10} = 0.1 \text{ S}$$

$$P = V^2 (G_1 + G_2) \Rightarrow V = \sqrt{\frac{P}{G_1 + G_2}} = \sqrt{\frac{1000}{(0.1 + 0.1)}} = 70.71 \text{ V}$$

$$P_1 = V^2 G_1 = (70.71)^2 0.1 = 500 \text{ W}$$

$$P_2 = V^2 G_2 = (70.71)^2 0.1 = 500 \text{ W}$$

$$\begin{aligned} (b) \quad \bar{Y}_{eq} &= \bar{Y}_1 + \bar{Y}_2 = (0.1 - j0.12) + 0.1 = 0.2 - j0.12 \\ &= 0.233 \angle -30.96^\circ \text{ S} \end{aligned}$$

$$I_S = V Y_{eq} = 70.71(0.233) = 16.48 \text{ A}$$

$$2.24 \quad \bar{S}_1 = P_1 + jQ_1 = 10 + j0; \bar{S}_2 = 10 \angle \cos^{-1} 0.9 = 9 + j4.359$$


$$\bar{S}_3 = \frac{10 \times 0.746}{0.85 \times 0.95} \angle -\cos^{-1} 0.95 = 9.238 \angle -18.19^\circ = 8.776 - j2.885$$

$$\bar{S}_S = \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = 27.78 + j1.474 = 27.82 \angle 3.04^\circ$$

$$P_S = \text{Re}(\bar{S}_S) = 27.78 \text{ kW}$$

$$Q_S = \text{Im}(\bar{S}_S) = 1.474 \text{ kVAR}$$

$$S_S = |\bar{S}_S| = 27.82 \text{ kVA}$$

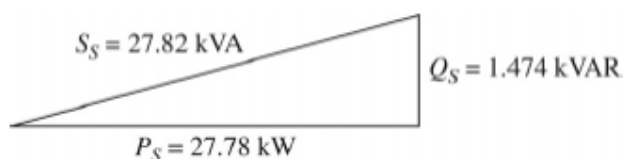

2.28

$$\bar{S}_1 = 15 + j6.667$$

$$\bar{S}_2 = 3(0.96) - j3[\sin(\cos^{-1} 0.96)] = 2.88 - j0.84$$

$$\bar{S}_3 = 15 + j0$$

$$\bar{S}_{TOTAL} = \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = (32.88 + j5.827) \text{ kVA}$$

(i) Let  $\bar{Z}$  be the impedance of a series combination of  $R$  and  $X$

$$\text{Since } \bar{S} = \bar{V} \bar{I}^* = \bar{V} \left( \frac{\bar{V}}{\bar{Z}} \right)^* = \frac{V^2}{\bar{Z}^*}, \text{ it follows that}$$

$$\bar{Z}^* = \frac{V^2}{\bar{S}} = \frac{(240)^2}{(32.88 + j5.827)10^3} = (1.698 - j0.301) \Omega$$

$$\therefore \bar{Z} = (1.698 + j0.301) \Omega \leftarrow$$


(ii) Let  $\bar{Z}$  be the impedance of a parallel combination of  $R$  and  $X$

$$\text{Then } R = \frac{(240)^2}{(32.88)10^3} = 1.7518 \Omega$$

$$X = \frac{(240)^2}{(5.827)10^3} = 9.885 \Omega$$

$$\therefore \bar{Z} = (1.7518 \parallel j9.885) \Omega \leftarrow$$

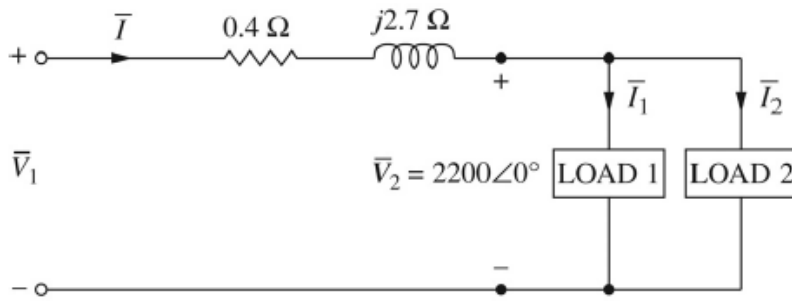**2.44** (a) The per-phase equivalent circuit for the problem is shown below:



Phase voltage at the load terminals is  $V_2 = \frac{2200\sqrt{3}}{\sqrt{3}} = 2200 \text{ V}$  taken as Ref.

Total complex power at the load end or receiving end is

$$\bar{S}_{R(3\phi)} = 560.1(0.707 + j0.707) + 132 = 528 + j396 = 660\angle 36.87^\circ \text{ kVA}$$

With phase voltage  $\bar{V}_2$  as reference,

$$\bar{I} = \frac{\bar{S}_{R(3\phi)}^*}{3\bar{V}_2^*} = \frac{660,000\angle -36.87^\circ}{3(2200\angle 0^\circ)} = 100\angle -36.87^\circ \text{ A}$$

Phase voltage at sending end is given by

$$\bar{V}_1 = 2200\angle 0^\circ + (0.4 + j2.7)(100\angle -36.87^\circ) = 2401.7\angle 4.58^\circ \text{ V}$$

The magnitude of the line to line voltage at the sending end of the line is

$$(V_1)_{L-L} = \sqrt{3}V_1 = \sqrt{3}(2401.7) = 4160 \text{ V}$$

(b) The three-phase complex-power loss in the line is given by


$$\begin{aligned}\bar{S}_{L(3\phi)} &= 3RI^2 + j3\times I^2 = 3(0.4)(100^2) + j3(2.7)(100)^2 \\ &= 12 \text{ kW} + j81 \text{ kVAR}\end{aligned}$$

(c) The three-phase sending power is

$$\begin{aligned}\bar{S}_{S(3\phi)} &= 3\bar{V}_1\bar{I}^* = 3(2401.7\angle 4.58^\circ)(100\angle 36.87^\circ) \\ &= 540 \text{ kW} + j477 \text{ kVAR}\end{aligned}$$

Note that  $\bar{S}_{S(3\phi)} = \bar{S}_{R(3\phi)} + \bar{S}_{L(3\phi)}$

**2.46 (a)**

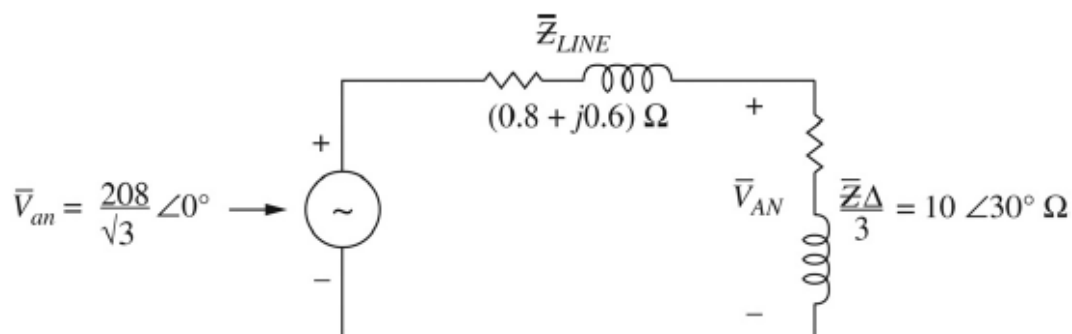

Using voltage division: 
$$\bar{V}_{AN} = \bar{V}_{an} \frac{\bar{Z}_\Delta / 3}{(\bar{Z}_\Delta / 3) + \bar{Z}_{LINE}}$$


$$= \frac{208}{\sqrt{3}} \angle 0^\circ \frac{10 \angle 30^\circ}{10 \angle 30^\circ + (0.8 + j0.6)}$$

$$= \frac{(120.09)(10 \angle 30^\circ)}{9.46 + j5.6} = \frac{1200.9 \angle 30^\circ}{10.99 \angle 30.62^\circ}$$

$$= 109.3 \angle -0.62^\circ \text{ V}$$

Load voltage =  $V_{AB} = \sqrt{3} (109.3) = 189.3 \text{ V Line-to-Line}$

(b)

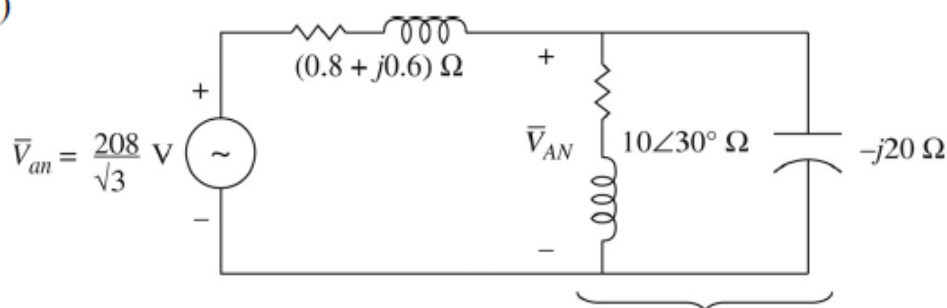

$$\bar{Z}_{eq} = 10 \angle 30^\circ \parallel (-j20)$$

$$= 11.547 \angle 0^\circ \Omega$$

$$\begin{aligned}
\bar{V}_{AN} &= \bar{V}_{an} \frac{\bar{Z}_{eq}}{\bar{Z}_{eq} + \bar{Z}_{LINE}} \\
&= (208/\sqrt{3}) \frac{11.547}{(11.547 + 0.8 + j0.6)} \\
&= \frac{1386.7}{12.362 \angle 2.78^\circ} = 112.2 \angle -2.78^\circ \text{ V}
\end{aligned}$$

Load voltage Line-to-Line  $V_{AB} = \sqrt{3} (112.2) = 194.3 \text{ V}$

**2.52** (a) Let  $\bar{V}_{AN}$  be the reference:  $\bar{V}_{AN} = \frac{2160}{\sqrt{3}} \angle 0^\circ = 2400 \angle 0^\circ \text{ V}$

Total impedance per phase  $\bar{Z} = (4.7 + j9) + (0.3 + j1) = (5 + j10) \Omega$

$\therefore$  Line Current  $= \frac{2400 \angle 0^\circ}{5 + j10} = 214.7 \angle -63.4^\circ \text{ A} = \bar{I}_A \leftarrow$

With positive A-B-C phase sequence,

$$\bar{I}_B = 214.7 \angle -183.4^\circ \text{ A}; \bar{I}_C = 214.7 \angle -303.4^\circ = 214.7 \angle 56.6^\circ \text{ A} \leftarrow$$

$$\begin{aligned}
(b) \left( \bar{V}_{A'N} \right)_{LOAD} &= 2400 \angle 0^\circ - [(214.7 \angle -63.4^\circ)(0.3 + j1)] \\
&= 2400 \angle 0^\circ - 224.15 \angle 9.9^\circ = 2179.2 - j38.54 \\
&= 2179.5 \angle -1.01^\circ \text{ V} \leftarrow
\end{aligned}$$

$$\left( \bar{V}_{B'N} \right)_{LOAD} = 2179.5 \angle -121.01^\circ \text{ V}; \left( \bar{V}_{C'N} \right)_{LOAD} = 2179.5 \angle -241.01^\circ \text{ V} \square$$

(c)  $S/\text{Phase} = \left( \bar{V}_{A'N} \right)_{LOAD} \bar{I}_A = (2179.5)(214.7) = 467.94 \text{ kVA} \leftarrow$

Total apparent power dissipated in all three phases in the load

$$\left[ S_{3\phi} \right]_{LOAD} = 3(467.94) = 1403.82 \text{ kVA} \leftarrow$$

Active power dissipated per phase in load =  $(P_{1\phi})_{LOAD}$

$$= (2179.5)(214.7)\cos(62.39^\circ) = 216.87\text{kW} \leftarrow$$

$$\therefore [P_{3\phi}]_{LOAD} = 3(216.87) = 650.61\text{kW} \leftarrow$$

Reactive power dissipated per phase in load =  $(Q_{1\phi})_{LOAD}$

$$= (2179.5)(214.7)\sin(62.39^\circ) = 414.65\text{kVAR} \leftarrow$$

$$\therefore [Q_{3\phi}]_{LOAD} = 3(414.65) = 1243.95\text{kVAR} \leftarrow$$

$$\text{(d) Line losses per phase } (P_{1\phi})_{LOSS} = (214.7)^2 0.3 = 13.83\text{kW} \leftarrow$$

$$\text{Total line loss } (P_{3\phi})_{LOSS} = 13.83 \times 3 = 41.49\text{kW} \leftarrow$$