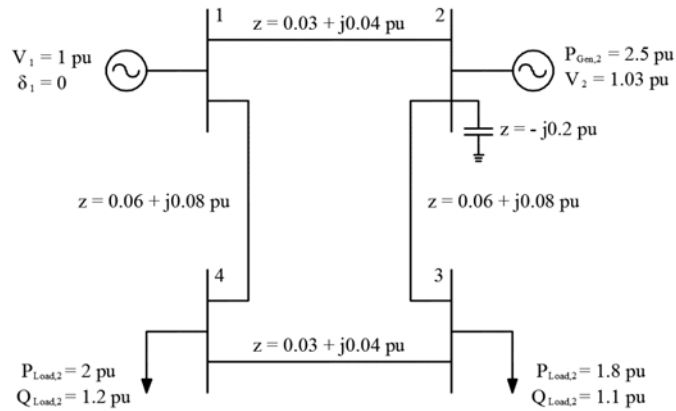


Name: _____

ID: _____

1) Consider the system below:



a. Fill out the following table for this system. The answer(s) should be selected from terms in the brackets. [3 marks]

| Bus Number | Bus Type (Load, Gen, Slack) | Known Variable (Pgen, Qgen, V, δ , Pload, Qload) | Unknown Variable (Pgen, Qgen, V, δ , Pload, Qload) |
|------------|--------------------------------|--|--|
| 1 | Slack | V, δ , Pload, Qload | Pgen, Qgen |
| 2 | Gen | Pgen, V, Pload, Qload | Qgen, δ |
| 3 | Load | Pgen, Qgen, Pload, Qload | V, δ |
| 4 | Load | Pgen, Qgen, Pload, Qload | V, δ |

b. Create the X vector for this system (in the form of $X = [-----]^T$). [4 marks]

$$X = [P_{gen,1} \quad \delta_2 \quad \delta_3 \quad \delta_4 \quad Q_{gen,1} \quad Q_{gen,2} \quad V_3 \quad V_4]^T$$

c. Create the admittance matrix Y_{bus} for system. Also, provide the B_{bus} and G_{bus} matrices. [4 marks]

$$Y_{bus} = \begin{bmatrix} 18-j24 & -12+j16 & 0 & -6+j8 \\ -12+j16 & 18-j19 & -6+j8 & 0 \\ 0 & -6+j8 & 18-j24 & -12+j16 \\ -6+j8 & 0 & -12+j16 & 18-j24 \end{bmatrix}$$


$$B_{bus} = \begin{bmatrix} -24 & 16 & 0 & 8 \\ 16 & -19 & 8 & 0 \\ 0 & 8 & -24 & 16 \\ 8 & 0 & 16 & -24 \end{bmatrix}$$

$$G_{bus} = \begin{bmatrix} 18 & -12 & 0 & -6 \\ -12 & 18 & -6 & 0 \\ 0 & -6 & 18 & -12 \\ -6 & 0 & -12 & 18 \end{bmatrix}$$

d. If all the branches in the system were lossless, how much real power is injected by the slack bus? [1 mark]

$$\text{If there are no losses in the branches, } \sum P_{gen} = \sum P_{load} \rightarrow P_{gen,1} = P_{load,3} + P_{load,4} - P_{gen,2} = 2 + 1.8 - 2.5 = 1.3 \text{ pu}$$

2) Consider the two bus system below:

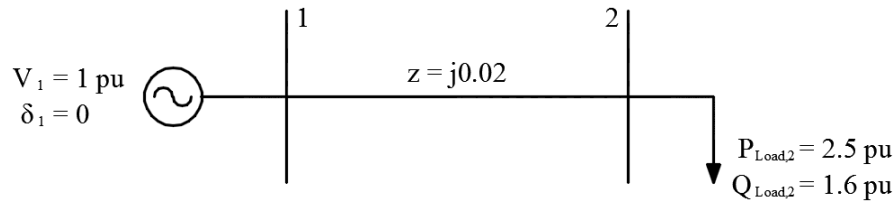

a. Create the Ybus for this system. [1 mark]

$$Y_{\text{bus}} = \begin{bmatrix} -j50 & j50 \\ j50 & -j50 \end{bmatrix}$$

b. Create the X vector for this system. [1 mark]

$$X = [P_{\text{gen},1} \quad \delta_2 \quad Q_{\text{gen},1} \quad V_2]^T$$

c. Write the real and reactive power flow equations for bus 2. Plug in all the known values and simplify as much as possible. [3 marks]

$$\begin{aligned} f_2 &= P_{\text{gen},2} - P_{\text{load},2} - \sum_{k=1}^2 V_2 V_k G[2,k] \cos(\delta_2 - \delta_k) - \sum_{k=1}^2 V_2 V_k B[2,k] \sin(\delta_2 - \delta_k) \\ &= 0 - 2.5 - V_2 V_1 G[2,1] \cos(\delta_2 - \delta_1) - V_2 V_2 G[2,2] \cos(\delta_2 - \delta_2) - V_2 V_1 B[2,1] \sin(\delta_2 - \delta_1) - V_2 V_2 B[2,2] \sin(\delta_2 - \delta_2) \\ &= -2.5 - 50 V_2 \sin(\delta_2) \end{aligned}$$

$$\begin{aligned} f_4 &= Q_{\text{gen},2} - Q_{\text{load},2} - \sum_{k=1}^2 V_2 V_k G[2,k] \sin(\delta_2 - \delta_k) + \sum_{k=1}^2 V_2 V_k B[2,k] \cos(\delta_2 - \delta_k) \\ &= 0 - 1.6 - V_2 V_1 G[2,1] \sin(\delta_2 - \delta_1) - V_2 V_2 G[2,2] \sin(\delta_2 - \delta_2) + V_2 V_1 B[2,1] \cos(\delta_2 - \delta_1) + V_2 V_2 B[2,2] \cos(\delta_2 - \delta_2) \\ &= -1.6 + 50 V_2 \cos(\delta_2) - 50 (V_2)^2 \end{aligned}$$

d. If the optimal value of $\delta_2 = -0.05211$ radians, what is the optimal voltage at bus 2? [3 marks]

Need to find the value of V_2 that "solves" the power flow equation.

If using f_2 , solve for V_2 such that: $-2.5 - 50 V_2 \sin(-0.05211) = 0$

This gives $V_2 = 0.96 \text{ pu}$

If using f_4 , solve for V_2 such that: $-1.6 + 50 V_2 \cos(-0.05211) - 50 (V_2)^2 = 0$

Solving this quadratic equation gives:

$V_2 = 0.965 \text{ pu}$ or 0.03 pu (Voltage of 0.03 pu , however, is not acceptable as it indicates the load has gone "dark"!)

Using either of the above equations is acceptable for this problem!