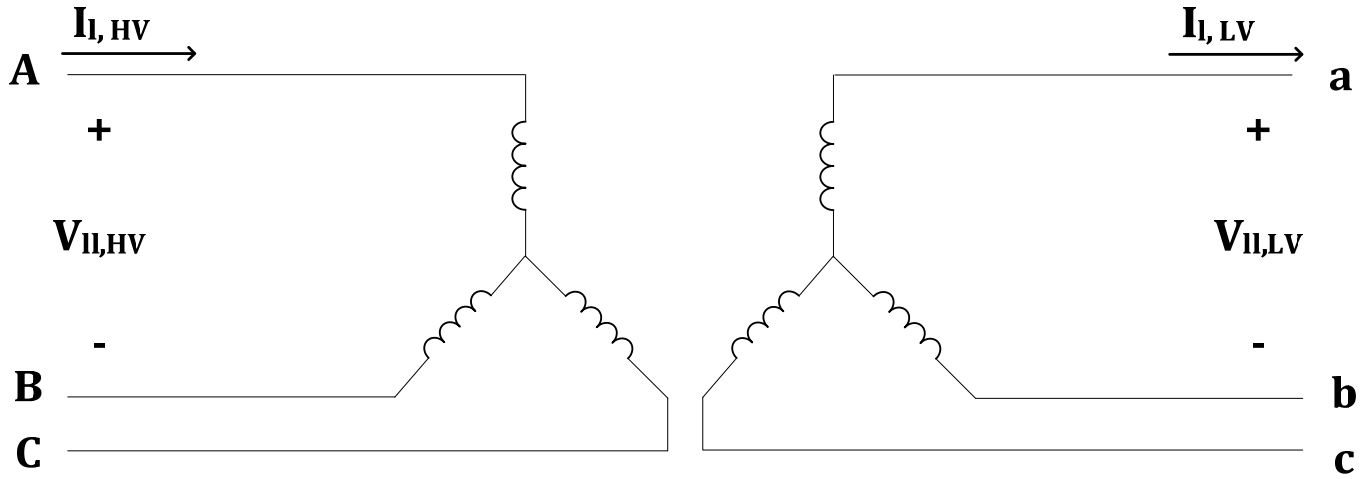


Voltage and current relationships for three phase transformers

Relationships between line-to-line voltage on either side of the transformer and line current on either side of the transformer are dependent on the winding connection type.


1) Y-Y connection



Magnetic coupling between the two winding gives: $\frac{\bar{V}_{\phi, HV}}{\bar{V}_{\phi, LV}} = \frac{N_1}{N_2}$ & $\frac{\bar{I}_{\phi, HV}}{\bar{I}_{\phi, LV}} = \frac{N_2}{N_1}$


Also know that, in both sides, $\bar{V}_{ll} = \sqrt{3} \angle 30^\circ \cdot \bar{V}_{ln}$ therefore, $\frac{\bar{V}_{ll, HV}}{\bar{V}_{ll, LV}} = \frac{N_1}{N_2}$

2) Δ-Δ connection

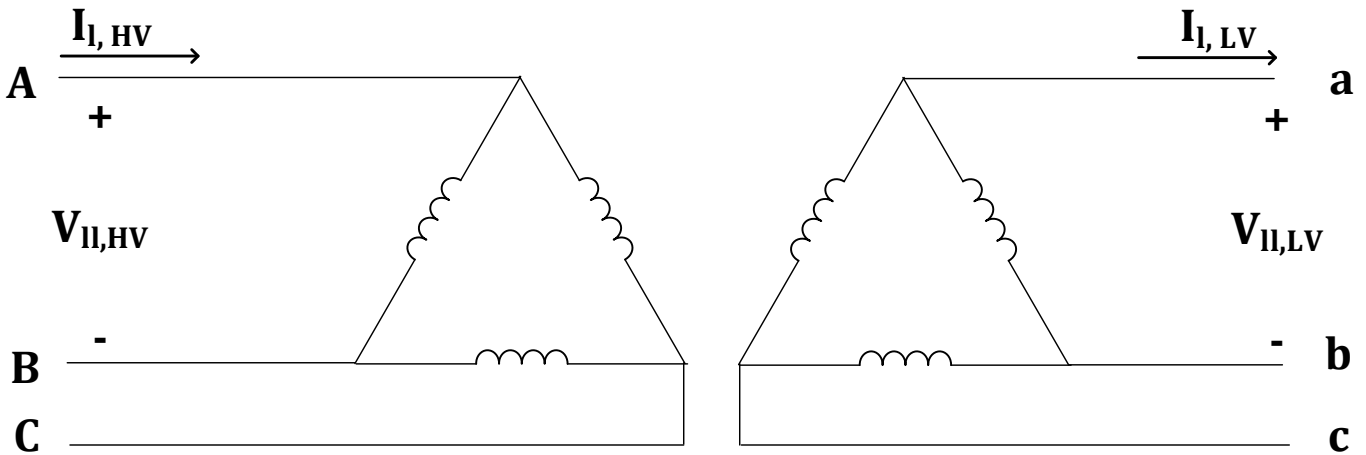

Similar to Y-Y, $\frac{\bar{V}_{ll, HV}}{\bar{V}_{ll, LV}} = \frac{N_1}{N_2}$ & $\frac{\bar{I}_{l, HV}}{\bar{I}_{l, LV}} = \frac{N_2}{N_1}$

3) Δ-Y Connection

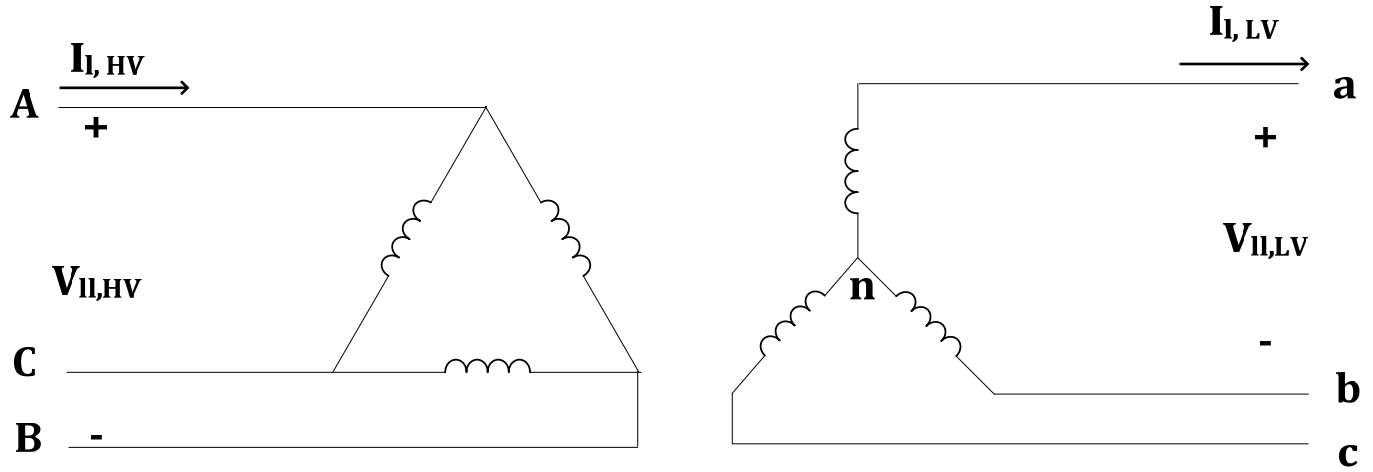

Magnetic coupling between the two winding gives: $\frac{\bar{V}_{\phi,HV}}{\bar{V}_{\phi,LV}} = \frac{N_1}{N_2}$ & $\frac{\bar{I}_{\phi,HV}}{\bar{I}_{\phi,LV}} = \frac{N_2}{N_1}$

Also, from Δ and Y connection properties: $\bar{V}_{ll,LV} = \sqrt{3} \angle 30^\circ \cdot \bar{V}_{\phi,LV}$ & $\bar{V}_{ll,HV} = \bar{V}_{\phi,HV}$

Therefore, $\frac{\bar{V}_{ll,HV}}{\bar{V}_{ll,LV}} = \frac{\bar{V}_{\phi,HV}}{\sqrt{3} \angle 30^\circ \cdot \bar{V}_{\phi,LV}} = \frac{N_1}{N_2 \cdot \sqrt{3}} \cdot \angle -30^\circ$

- The ratio of line-to-line voltage magnitudes is $\frac{N_1}{N_2 \cdot \sqrt{3}}$
- Line-to-line voltage on the Δ side lags line-to-line voltage on the Y side by 30°

Similarly, $\frac{\bar{I}_{l,HV}}{\bar{I}_{l,LV}} = \frac{N_2 \cdot \sqrt{3}}{N_1} \angle -30^\circ$

4) Y-Δ Connection

We can show that:

$$\frac{\bar{V}_{ll,HV}}{\bar{V}_{ll,LV}} = \frac{\sqrt{3} \cdot N_1}{N_2} \cdot \angle 30^\circ$$

$$\frac{\bar{I}_{l,HV}}{\bar{I}_{l,LV}} = \frac{N_2}{\sqrt{3} \cdot N_1} \angle 30^\circ$$