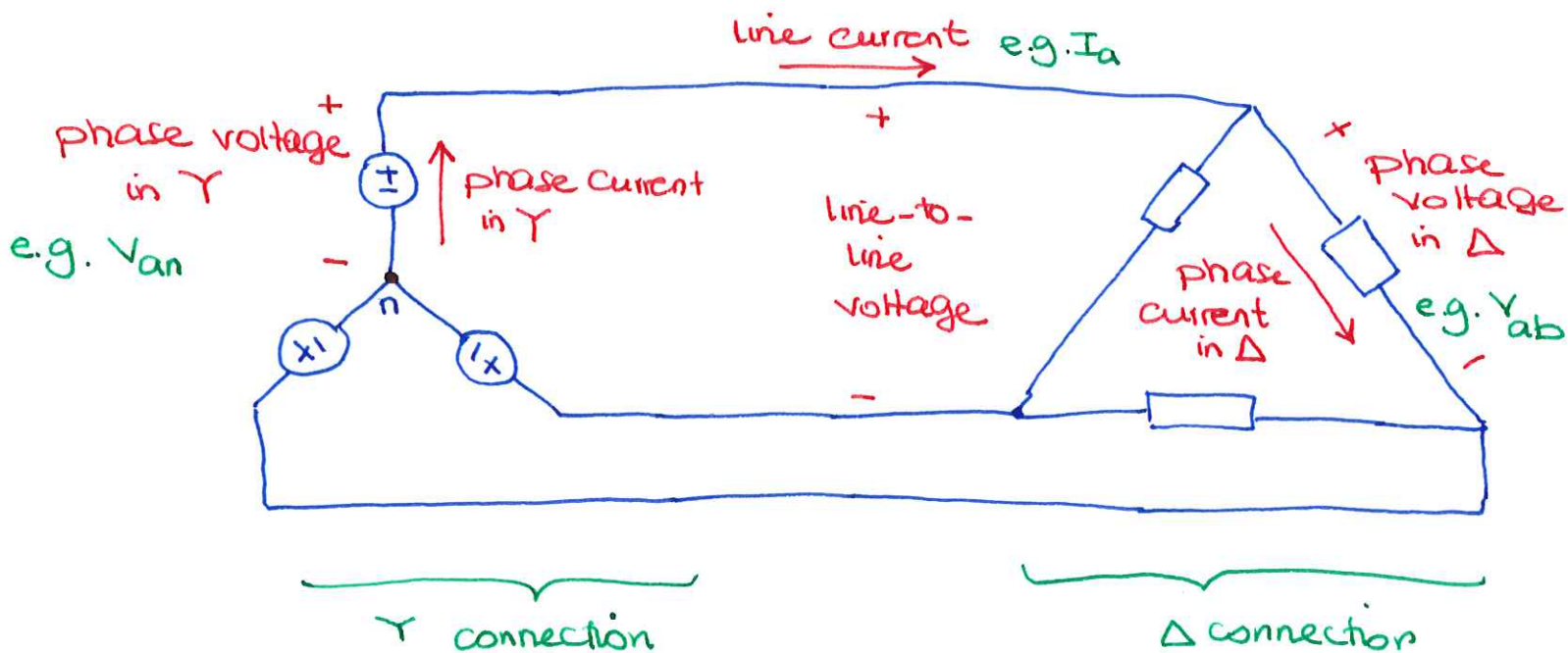


## Important: Voltages & Currents in 3 $\phi$ Systems


- Voltage in each phase of a device (gen, load) is phase voltage
- Current in each phase of a device (gen, load) is phase current
- Voltages between phases (lines) is line-to-line (phase-to-phase) voltage
- Current in a line is line current.


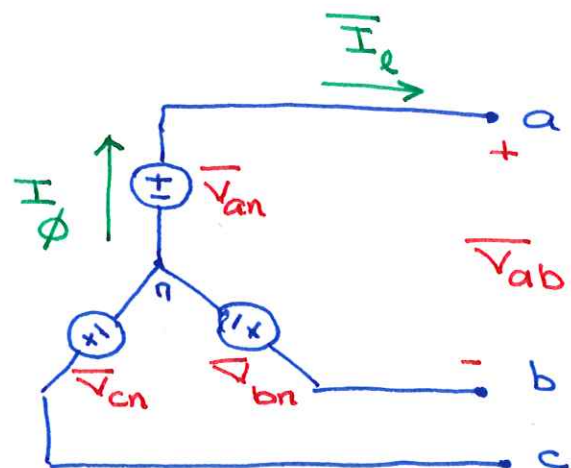
### Y-connected Source/Load

- Phase <sup>current</sup> = line current


$$\boxed{\overline{I}_l = \overline{I}_\phi}$$



- Y-connected source shown here.  
Same relationships for Y load.

• Phase voltages & line-to-line voltages are related by:
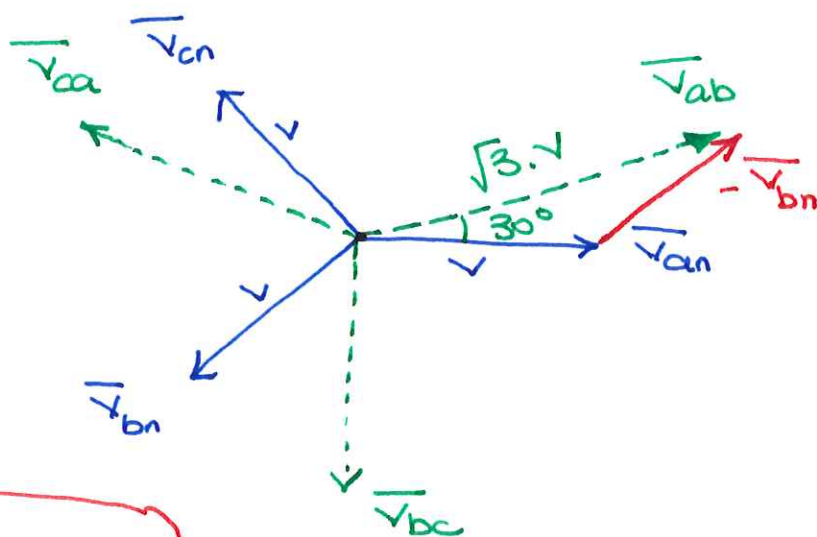
$$\begin{aligned}\overline{V}_{ab} &= \overline{V}_{an} - \overline{V}_{bn} \\ &= V \angle \alpha - V \angle \alpha - 120^\circ \\ &= \sqrt{3} \cdot V \angle \alpha + 30^\circ\end{aligned}$$



i.e.

mag:

$$V_{l-l} = \sqrt{3} \cdot V_\phi$$

phase:

$$\theta_{V_{l-l}} = \theta_{V_\phi} + 30^\circ$$

OR

$$\overline{V}_{l-l} = \overline{V}_\phi \cdot \sqrt{3} \angle 30^\circ$$

• Line-to-line voltages lead corresponding phase (line-to-neutral) voltages by  $30^\circ$ .  $\overline{V}_{ab}$  leads  $\overline{V}_{an}$ ,  $\overline{V}_{bc}$  leads  $\overline{V}_{bn}$ ,  $\overline{V}_{ca}$  leads  $\overline{V}_{cn}$  by  $30^\circ$

• Line-to-line voltages are also balanced:  $\overline{V}_{ab} + \overline{V}_{bc} + \overline{V}_{ca} = 0$

• Power in  $3\phi = 3 \times$  power in one phase

$$\begin{aligned}\overline{S}_{3\phi} &= 3 \cdot \overline{S}_{1\phi} \\ &= 3 \cdot \overline{V}_\phi \cdot \overline{I}_\phi^* \end{aligned} \quad \left. \vphantom{\begin{aligned}\overline{S}_{3\phi} &= 3 \cdot \overline{S}_{1\phi} \\ &= 3 \cdot \overline{V}_\phi \cdot \overline{I}_\phi^* \end{aligned}} \right\} \text{true for Y or } \Delta$$

therefore,

$$P_{3\phi} = 3 \cdot V_\phi \cdot I_\phi \cdot \underbrace{\cos(\theta_{V_\phi} - \theta_{I_\phi})}_{\text{PF}}$$

$$S_{3\phi} = |\overline{S}_{3\phi}| = 3 \cdot V_\phi \cdot I_\phi$$

$$P_{3\phi} = S_{3\phi} \cdot \text{PF}$$

$$Q_{3\phi} = \sqrt{S_{3\phi}^2 - P_{3\phi}^2}$$

However, in  $\Delta$  connection:  $V_\phi = \frac{V_{l-l}}{\sqrt{3}}$ ,  $I_\phi = I_l$

$$\therefore S_{3\phi} = \sqrt{3} \cdot V_{l-l} \cdot I_l$$

For all 3 $\phi$  systems

important: Unless otherwise stated, voltages are expressed as line-to-line quantities, currents are expressed as line quantities, and power is expressed as total 3 $\phi$  quantity.

### Delta-connected Source/Load

- Phase voltage = line-to-line voltage


$$V_\phi = V_{l-l}$$

- Phase currents & line currents are related by:

$$\begin{aligned} \bar{I}_a &= \bar{I}_{ab} - \bar{I}_{ca} \quad (\text{KCL}) \\ &= I \angle \beta - I \angle \beta + 120^\circ \\ &= \sqrt{3} I \angle \beta - 30^\circ \end{aligned}$$

i.e.
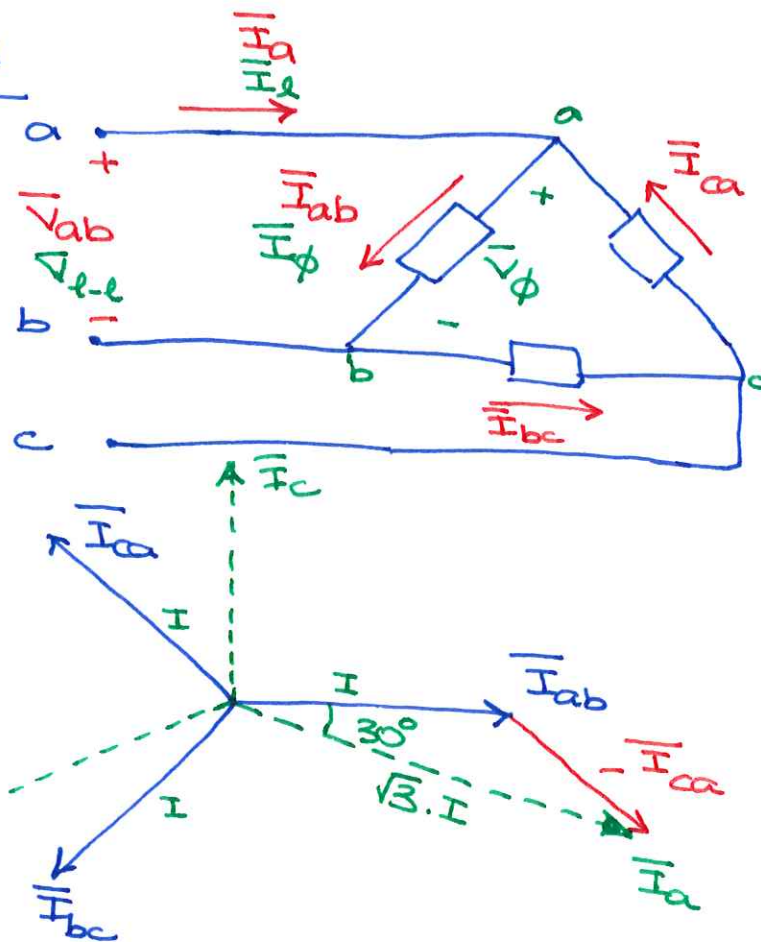
$$\begin{aligned} \text{mag: } I_l &= \sqrt{3} \cdot I_\phi \\ \text{phase: } \theta_{I_l} &= \theta_{I_\phi} - 30^\circ \end{aligned} \quad \text{OR} \quad \bar{I}_l = \bar{I}_\phi \cdot \sqrt{3} \angle -30^\circ$$





• Similar to Y connection,  $S_{3\phi} = 3 \cdot V_{\phi} \cdot I_{\phi}$

but for  $\Delta$  connection:  $V_{\phi} = V_{ll}$  &  $I_{\phi} = \frac{I_l}{\sqrt{3}}$

$$\therefore S_{3\phi} = \sqrt{3} \cdot V_{ll} \cdot I_l$$

identical to Y connection

$\Delta$ -Y Transformation :

• See handout

Per-Phase (Single Phase) Analysis

• A balanced  $3\phi$  system can be completely solved by analyzing one phase.

• Procedure:

- Convert all  $\Delta$  loads & sources to equivalent Y.
- Solve one phase (phase A for example) independent of other phases. This will produce  $\overline{V}_{l-n}$ ,  $\overline{I}_l$ ,  $\overline{S}_{1\phi}$
- Then, we use single phase values to find desired  $3\phi$  values:


e.g.:  $\overline{S}_{3\phi} = 3 \times \overline{S}_{1\phi}$

- Phase B & C voltages & currents are determined by  $\pm 120^\circ$  phase shift
- Line-to-line voltages &  $\overline{I}_{\phi}$  for  $\Delta$  connection can be determined by using relationships between  $\overline{V}_{l-n}$  &  $\overline{V}_{ll}$  and  $\overline{I}_l$  &  $\overline{I}_{\phi}$  for  $\Delta$
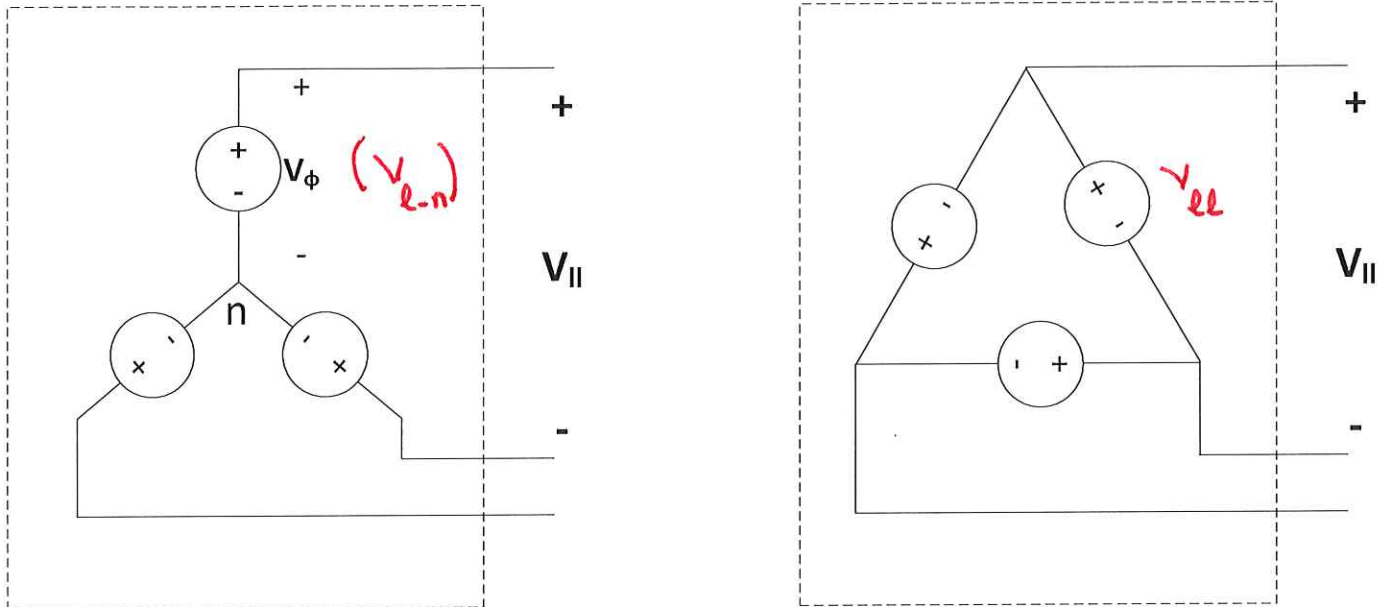
## Delta-Wye transformation

Sources:

For sources to be equivalent, the line-to-line voltage ( $V_{ll}$ ) produced by one configuration should be identical to  $V_{ll}$  produced by the other.



For the Y-connected source to be equivalent to the delta-connected source, the phase (line-to-neutral) voltage in the Y-connected source should be:

phase voltage of Y  $\rightarrow \bar{V}_\phi = \frac{\bar{V}_{ll}}{\sqrt{3} \angle 30^\circ}$  ← phase voltage of equivalent  $\Delta$



For the delta-connected source to be equivalent to the Y-connected source, the phase (line-to-line) voltage in the delta connection should be the same as the line-to-line voltage in the Y connection. We can also express the phase voltage in the delta connection (line-to-line) in terms of the phase voltage in the Y connection (line-to-neutral):

$$\bar{V}_{ll} = \bar{V}_\phi \cdot \sqrt{3} \angle 30^\circ$$

For example, Given a  $\Delta$  source with  $\bar{V}_{ll} = 138 \angle 0^\circ$  kV  
 the equivalent Y source has  $\bar{V}_\phi = \bar{V}_{en} = \frac{138 \angle 0^\circ}{\sqrt{3} \angle 30^\circ}$   
 $= \frac{138}{\sqrt{3}} \angle -30^\circ$  kV
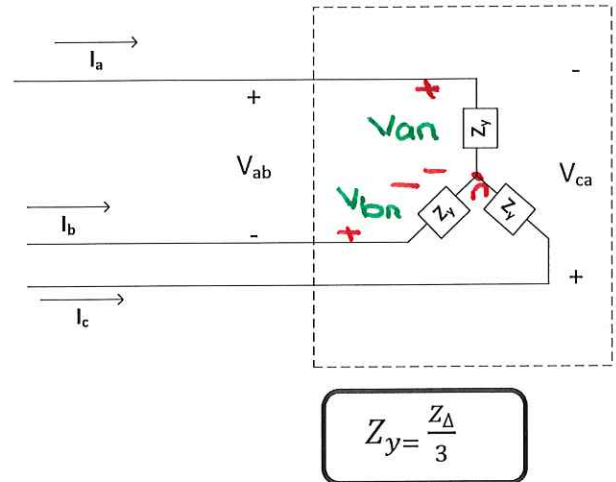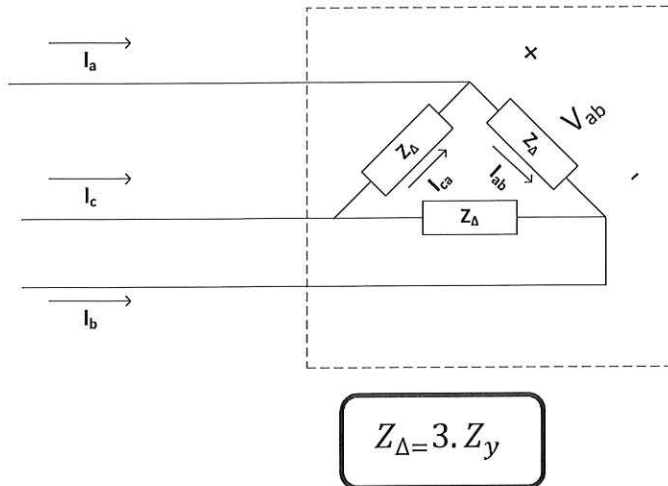
### Loads:

For loads to be equivalent, the line-to-line voltage ( $V_{ll}$ ) at the load terminals and the line current drawn by the load ( $I_l$ ) should be identical. To accomplish this, the equivalent loads should be calculated based on the following equations:



Why?

$$\overline{V_{an}} \quad \overline{V_{bn}}$$

$$\overline{V_{ab}} = Z_Y \cdot \overline{I_a} - Z_Y \cdot \overline{I_b} = Z_Y \cdot (\overline{I_a} - \overline{I_b}) \quad [1]$$

similarly,

$$\overline{V_{ca}} = Z_Y \cdot (\overline{I_c} - \overline{I_a}) \quad [2]$$

For a balanced system,

$$\overline{I_a} + \overline{I_b} + \overline{I_c} = 0 \quad \therefore \quad \overline{I_a} = -\overline{I_b} - \overline{I_c} \quad [3]$$

Subtract [2] from [1], then plug in [3]

$$\begin{aligned} \overline{V_{ab}} - \overline{V_{ca}} &= Z_Y \cdot (\overline{I_a} - \overline{I_b} - \overline{I_c} + \overline{I_a}) \\ &= 3 Z_Y \cdot \overline{I_a} \quad \text{from [3]} \end{aligned}$$

KCL:

$$\overline{I_a} = \overline{I_{ab}} - \overline{I_{ca}} = \frac{\overline{V_{ab}}}{Z_{\Delta}} - \frac{\overline{V_{ca}}}{Z_{\Delta}}$$

$$\therefore Z_{\Delta} = \frac{\overline{V_{ab}} - \overline{V_{ca}}}{\overline{I_a}}$$

← re-arrange


$$\therefore 3 Z_Y = \frac{\overline{V_{ab}} - \overline{V_{ca}}}{\overline{I_a}}$$

$\overline{V_{ab}}, \overline{V_{ca}}, \overline{I_a}$  should be identical for the loads to be equivalent  $\therefore$


$$Z_{\Delta} = 3 \cdot Z_Y \quad \text{or} \quad Z_Y = \frac{Z_{\Delta}}{3}$$



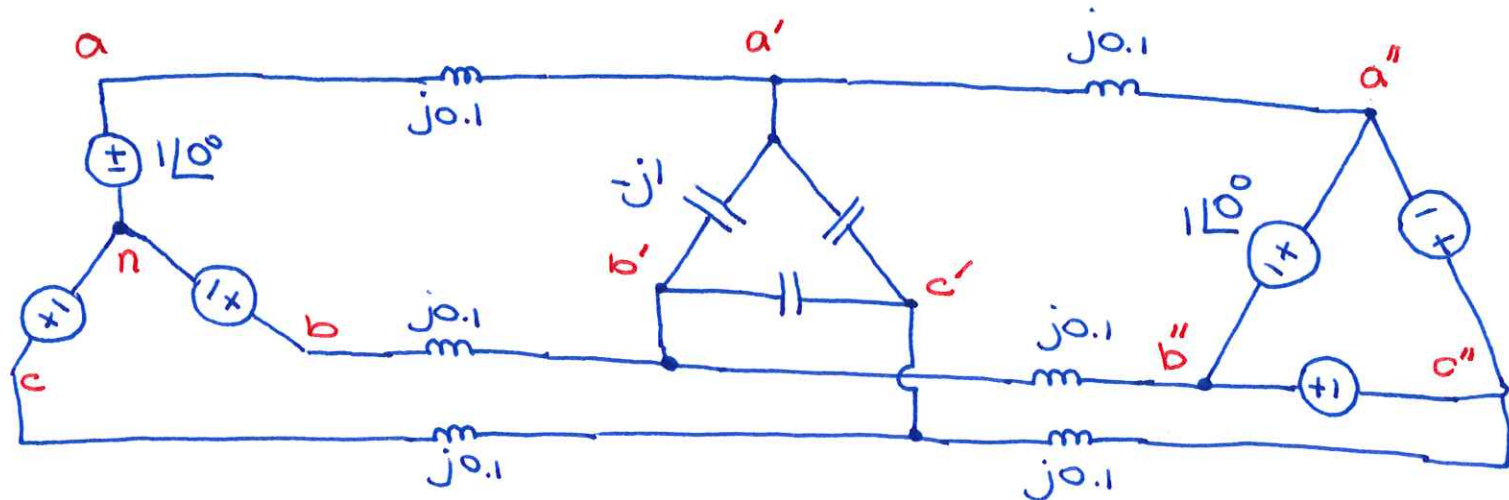Ex: Find : . Load voltage  $\overline{V}_{a'b'}$   
 . Total power supplied by left source




. Convert everything to Y:

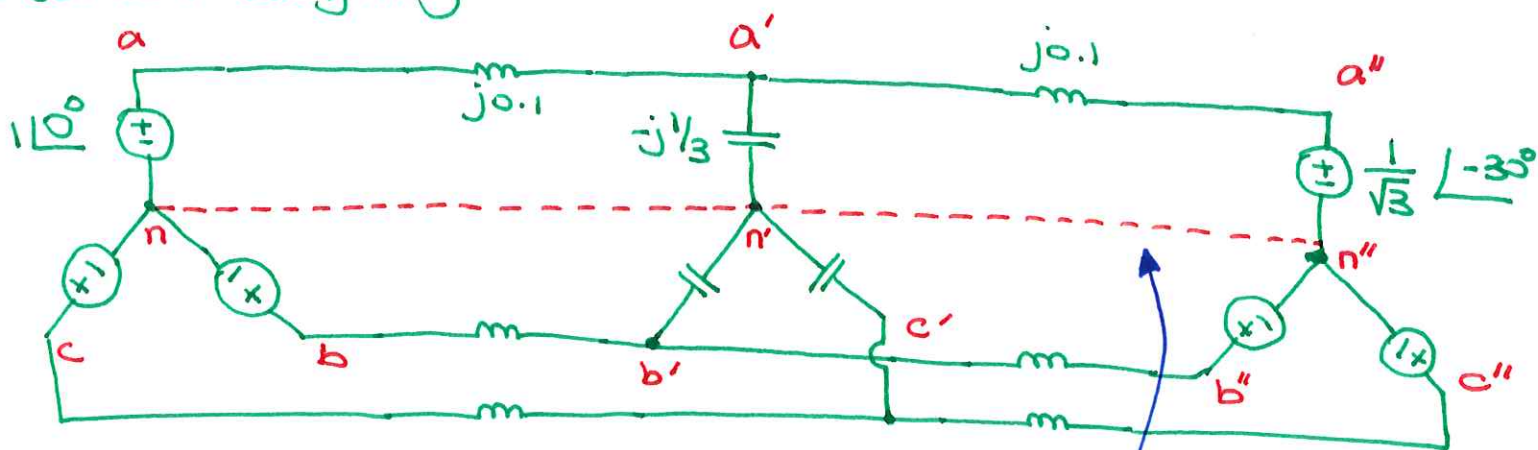

added a  $0\Omega$  neutral wire to complete the circuit

Single phase circuit for phase a:

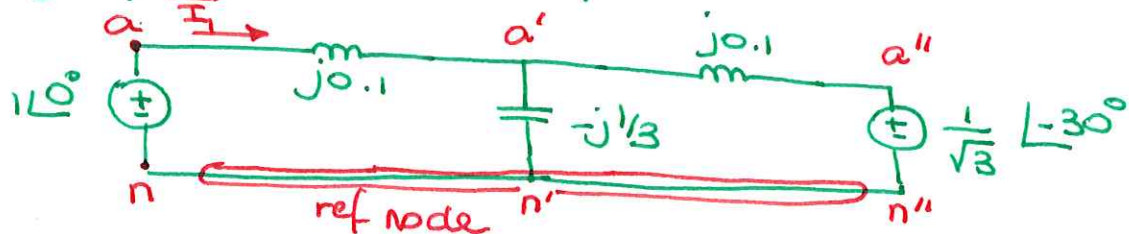

$$\text{KCL (node eq) at } a' : \frac{\overline{V}_{a'} - 1\angle 0^\circ}{j0.1} + \frac{\overline{V}_{a'}}{-j1/3} + \frac{\overline{V}_{a'} - \frac{1}{\sqrt{3}} \angle -30^\circ}{j0.1} = 0$$

$$\therefore (-j10)(\overline{V}_{a'} - 1) + (j3)(\overline{V}_{a'}) + (-j10)(\overline{V}_{a'} - \frac{1}{\sqrt{3}} \angle -30^\circ) = 0$$

$$\therefore \overline{V}_{a'} = 0.9 \angle -10.9^\circ$$

← This is  $\overline{V}_{a'n'}$


i.e. Line-to-neutral voltage for (equivalent) Y-connected capacitor

$$\overline{V_{a'b'}} = \overline{V_{a'n'}} \sqrt{3} \angle 30^\circ = 1.56 \angle 19.1^\circ \text{ V}$$

line-to-line (phase) voltage across capacitor in the orig circuit

aside:  $\overline{V_{b'c'}} = 1.56 \angle 19.1^\circ - 120^\circ$
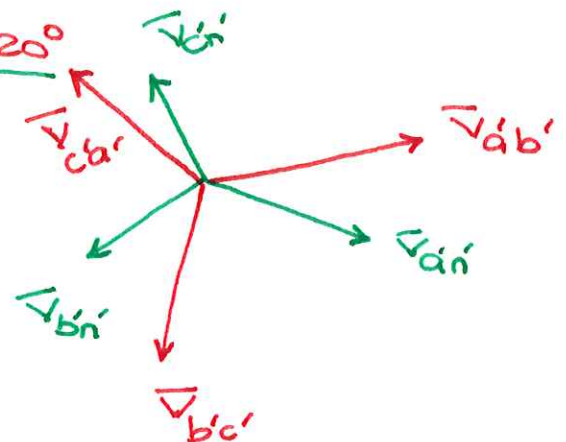
$$\overline{V_{c'a'}} = 1.56 \angle 19.1^\circ + 120^\circ$$



To find power from the left source:

$$\overline{I_1} = \frac{\overline{V_a} - \overline{V_{a'}}}{j0.1} = \frac{1 - 0.9 \angle -10.9^\circ}{j0.1} = 2.06 \angle -34^\circ \text{ A}$$

$$\overline{S}_{\text{left source } 3\phi} = 3 \cdot \underbrace{\overline{V_{an}} \cdot \overline{I_1}^*}_{\overline{S}_{1\phi}} = \underbrace{5.1}_{P_{3\phi}(\text{W})} + j \underbrace{3.5}_{Q_{3\phi}(\text{VAR})}$$




### Topic 3: (Power) Transformers

- Reminder: Power systems operate at **or near** a few pre-defined voltage levels, e.g: 120 V, ..., 500 kV
- Transformers (Txfr) transfer power between different AC voltage levels. We transmit power at higher voltage levels because:  $S = V \cdot I$  ; if  $V \uparrow$  then  $I \downarrow$  which results in:

- 1)  $I^2 R$  losses in lines  $\downarrow$
- 2) voltage drop across the lines  $\downarrow$
- 3) smaller conductors for lines

#### Ideal Transformer

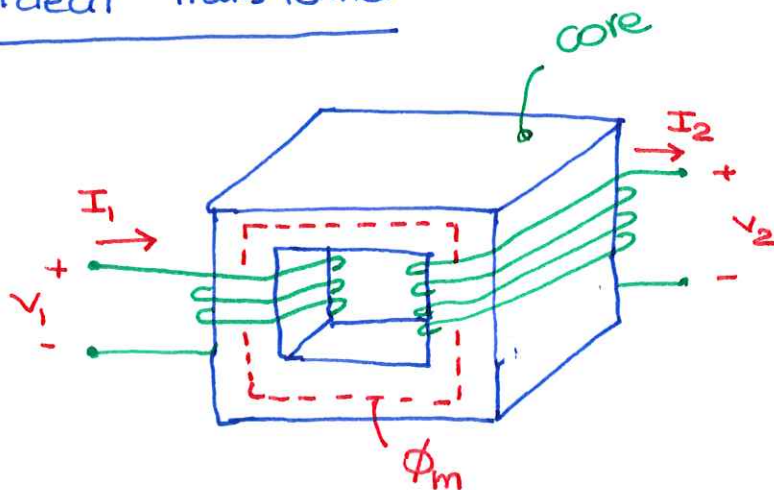

$\Phi_m$ : magnetic flux

$\mu$ : magnetic permeability of the core

winding 1 has  $N_1$  turns  
winding 2 has  $N_2$  turns

assumptions: • No real power losses in the windings ( $R = 0$ )  
                  "                  "                  in the core

•  $\mu$  is infinite

• no leakage flux;  $\Phi_m$  is contained in the core

From Faraday's Law :  $V_1 = N_1 \frac{d\phi_m}{dt}$  ,  $V_2 = N_2 \frac{d\phi_m}{dt}$


$$\therefore \frac{d\phi_m}{dt} = \frac{V_1}{N_1} = \frac{V_2}{N_2} \therefore \boxed{\frac{V_1}{V_2} = \frac{N_1}{N_2} = a}$$

turns ratio

since  $S_1 = V_1 I_1$  &  $S_2 = V_2 I_2$  and  $S_1 = S_2$

$$\therefore \boxed{\frac{I_1}{I_2} = \frac{N_2}{N_1} = \frac{1}{a}}$$

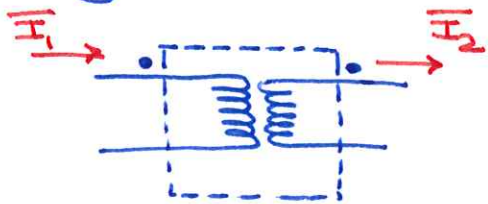• Winding direction is not always visible. Solution: dot convention




when current enters a winding at the dotted terminal, flux is in the direction of the dot

$\therefore$  When current enters dotted terminal from one side & leaves dotted terminal on other side, those currents are in phase

i.e.,  $\vec{I}_1$  &  $\vec{I}_2$  are in phase, just scaled up/down by  $1/a$

### Referring Impedances

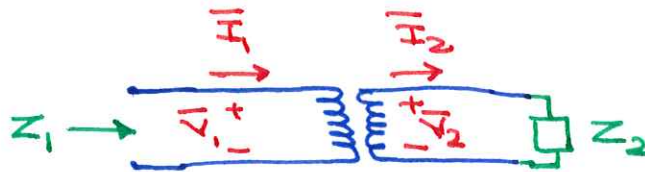

if  $Z_2$  is connected to winding 2,  $Z_1$  (impedance seen from winding 1) is :

$$Z_1 = \frac{V_1}{I_1} = \frac{\frac{N_1}{N_2} V_2}{\frac{N_1}{N_2} I_2} = \left(\frac{N_1}{N_2}\right)^2 \cdot \frac{V_2}{I_2} = \left(\frac{N_1}{N_2}\right)^2 \cdot Z_2$$