

Transmission Line Models Tutorial Questions for Lecture 2

1. The sending-end voltage, current, and power factor of a three-phase transmission line spanning from Red Deer to Calgary are found to be 260 kV, 300 A, and 0.9 lagging, respectively. The $ABCD$ constants are:

$$A = D = 0.8904 \angle 1.34^\circ$$

$$B = 186.82 \angle 79.45^\circ \Omega$$

$$C = 1.131 \times 10^{-3} \angle 90.41^\circ \text{S}$$

Find:

- (i) The corresponding receiving-end phase voltage and current
- (ii) Receiving-end power factor.

In-Class Example Lecture 2 Solution

1. Given:

$$|I_S| = 300 \text{ A}; \cos \theta_S = 0.9 \text{ lag}; ABCD \text{ constants}$$

$$\text{Required: } [V_R, I_R, \cos \theta_R]$$

$$\text{The sending-end phase voltage, } |V_S| = 260/\sqrt{3} = 150.111 \text{ kV}$$

The sending-end current is:

$$I_S = |I_S| \angle -\cos^{-1} 0.9 = 300 \angle -25.84^\circ \text{ A}; \text{ We have used negative sign because the power factor is lagging}$$

Recall,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}^{-1} = \frac{1}{AD-BC} \begin{bmatrix} D & -B \\ -C & A \end{bmatrix}$$

$$\text{But } AD - BC = 1$$

$$\text{Therefore, } \begin{bmatrix} A & B \\ C & D \end{bmatrix}^{-1} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix}$$

This means that:

$$\begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}^{-1} \begin{bmatrix} V_S \\ I_S \end{bmatrix}$$

$$\begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_S \\ I_S \end{bmatrix}$$

$$\begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} 0.8904 \angle 1.34^\circ & -186.82 \angle 79.45^\circ \\ -1.131 \times 10^{-3} \angle 90.41^\circ & 0.8904 \angle 1.34^\circ \end{bmatrix} \begin{bmatrix} 150.111 \times 10^3 \\ 300 \angle -25.84^\circ \end{bmatrix}$$

$$V_R = (0.8904 \angle 1.34^\circ)(150.111 \times 10^3) + (-186.82 \angle 79.45^\circ)(300 \angle -25.84^\circ)$$

$$= (133658.8 \angle 1.34^\circ) + (-56046 \angle 53.61^\circ)$$

$$= (133622.3 + j3125.65) + (-33250.9 - j45116.9)$$

$$= (100371.4 - j41991.25)$$

$$V_R = \mathbf{108.8 \angle -22.7^\circ \text{ kV}}$$

$$I_R = (-1.131 \times 10^{-3} \angle 90.41^\circ)(150.111 \times 10^3) + (0.8904 \angle 1.34^\circ)(300 \angle -25.84^\circ)$$

$$= (-169.77 \angle 90.41^\circ) + (267.12 \angle -24.5^\circ)$$

$$= (1.215 - j169.76) + (243.07 - j110.77)$$

$$= (244.28 - j280.53)$$

$$I_R = \mathbf{372 \angle -48.95^\circ \text{ A}}$$

(ii) The receiving-end power factor is:

$$\cos \theta_R = \cos(\theta_{VR} - \theta_{IR})$$

$$= \cos(-22.7^\circ + 48.9^\circ) = 0.897 \text{ lagging}$$