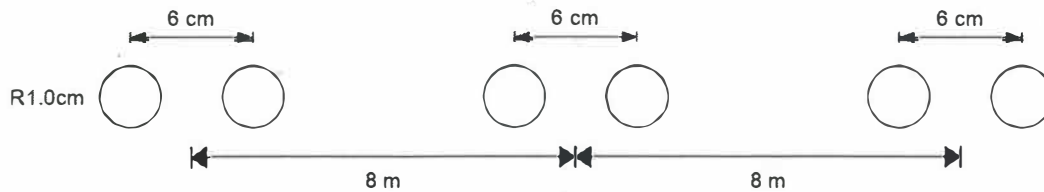


Name: _____

ID: _____

- 1) The figure below shows the conductor configuration of three-phase overhead transmission line with each phase bundle consisting of two solid conductors. All conductors have a radius of 1 cm with 6 cm bundle spacing. The bundles are equally spaced at 8 m from each other. Assume the GMR for one conductor is r'



- a) Find the phase inductance of the line in mH/km. [4 marks]

$$\textcircled{1} D_{eq} = \sqrt[3]{8 \times 8 \times 16} = 10.08 \text{ m}$$

$$\textcircled{1} D_{SL} = \sqrt{(0.7788)(0.01) \times 0.06} = 0.0216 \text{ m}$$

$$\textcircled{1} L = 2 \times 10^{-7} \ln\left(\frac{D_{eq}}{D_{SL}}\right) = 1.23 \text{ mH/km}$$

- b) Find the capacitance to neutral of the line in nF/km. [3 marks]

$$\textcircled{1} D_{eq} = \sqrt[3]{8 \times 8 \times 16} = 10.08 \text{ m}$$

$$\textcircled{1} D_{SC} = \sqrt{0.01 \times 0.06} = 0.0245 \text{ m}$$

$$\textcircled{1} C = \frac{2 \pi \epsilon_0}{\ln\left(\frac{D_{eq}}{D_{SC}}\right)} = 9.24 \text{ nF/km}$$

Name: _____

ID: _____

2) The specification of a three phase high voltage transmission line is provided below:

- Rated voltage: 260 kV
- Phase line resistance: $0.06 \Omega/\text{km}$
- Phase line reactance: $0.5 \Omega/\text{km}$
- Phase to neutral admittance: $j4 \times 10^{-6} \text{ S/km}$

For the following line segments:

- Determine the ABCD parameters
- Sketch the equivalent line circuit and label the line parameters, voltages and currents
(No numerical values needed for the labels)

a) Line segment is 150 km. [8 marks]


$$\textcircled{1} Z = z \cdot l = (0.06 + j0.5)(150) = 9 + j75 = 75.54 \angle 83.16^\circ \Omega$$

$$\textcircled{1} Y = y \cdot l = (j4 \times 10^{-6})(150) = j6 \times 10^{-4} \text{ S}$$

$$\textcircled{1} A = D = 1 + \frac{YZ}{2} = 0.978 + j0.0027 = 0.978 \angle 0.158^\circ$$

$$\textcircled{1} B = Z$$
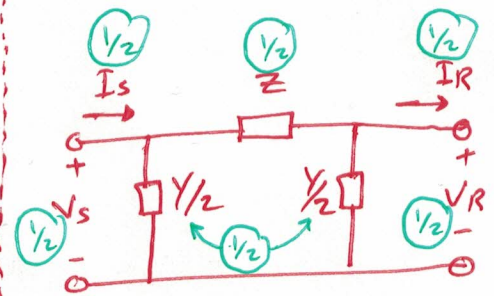
$$\textcircled{1} C = Y \left(1 + \frac{YZ}{4}\right) = -8.1 \times 10^{-7} + j5.93 \times 10^{-4} = 5.93 \angle 90.08^\circ$$



b) Line segment is 50 km [6 marks]


$$\textcircled{1} Z = z \cdot l = (0.06 + j0.5)(50) = 3 + j25 = 25.18 \angle 83.16^\circ \Omega$$

$$\textcircled{1/2} A = 1$$

$$\textcircled{1} B = Z$$

$$\textcircled{1/2} C = 0$$

$$\textcircled{1/2} D = 1$$

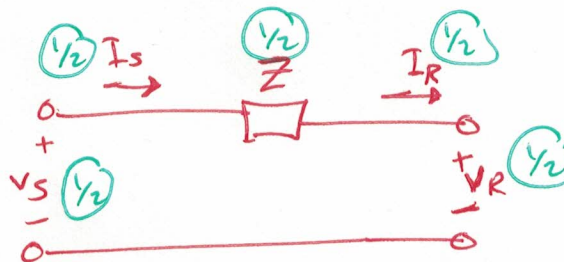

Name: _____

ID: _____

- 3) A 60 km three phase transmission line is rated at 260 kV (Line to line). The sending bus is delivering 100 MW and 40 MVar at the rated voltage. Calculate line-to-line voltage and current at the receiving bus. [5 marks]

Hint: The ABCD parameters for this line are $\begin{bmatrix} 1 & 3.6 + j30 \\ 0 & 1 \end{bmatrix}$

$$\textcircled{1} \quad I_R = I_S = \frac{S}{\sqrt{3} V_{LL}} \angle \theta_I$$

$$\textcircled{1} \quad ; \theta_I = -\tan^{-1} \frac{Q}{P}$$

$$= -21.8$$

$$\rightarrow I_R = \frac{\sqrt{(100 \times 10^6)^2 + (40 \times 10^6)^2}}{\sqrt{3} \times 260 \times 10^3} \angle -21.8$$

$$= 239.16 \angle -21.8^\circ \text{ A}$$

* Alternative method for I_R :-

$$\textcircled{1} \quad I_R = I_S = \frac{S^*}{\sqrt{3} V_{LL}} \quad \textcircled{1}$$

$$= \frac{(100 \times 10^6 - j40 \times 10^6)}{\sqrt{3} \times 260 \times 10^3}$$

$$= 239.16 \angle -21.8^\circ \text{ A}$$

In the online version of this quiz, the current values were provided. For a short line, $I_s = I_r$

* From ABCD matrix $\rightarrow Z = B = 3.6 + j30 = 30.22 \angle 83.15^\circ$

$$\textcircled{1} \quad V_{RLN} = V_{SLN} - I Z$$

$$= \frac{260 \times 10^3}{\sqrt{3}} \angle 0 - (239.16 \angle -21.8^\circ)(30.22 \angle 83.15^\circ)$$

$$\textcircled{1} \rightarrow$$

$$= 146.64 - j6.34 = 146.78 \angle -2.48^\circ \text{ kV}$$

$$\rightarrow V_{RLL} = \sqrt{3} V_{RLN} \quad \textcircled{1/2} \quad \textcircled{1/2}$$

$$= 254.22 \angle -2.52^\circ \text{ kV}$$