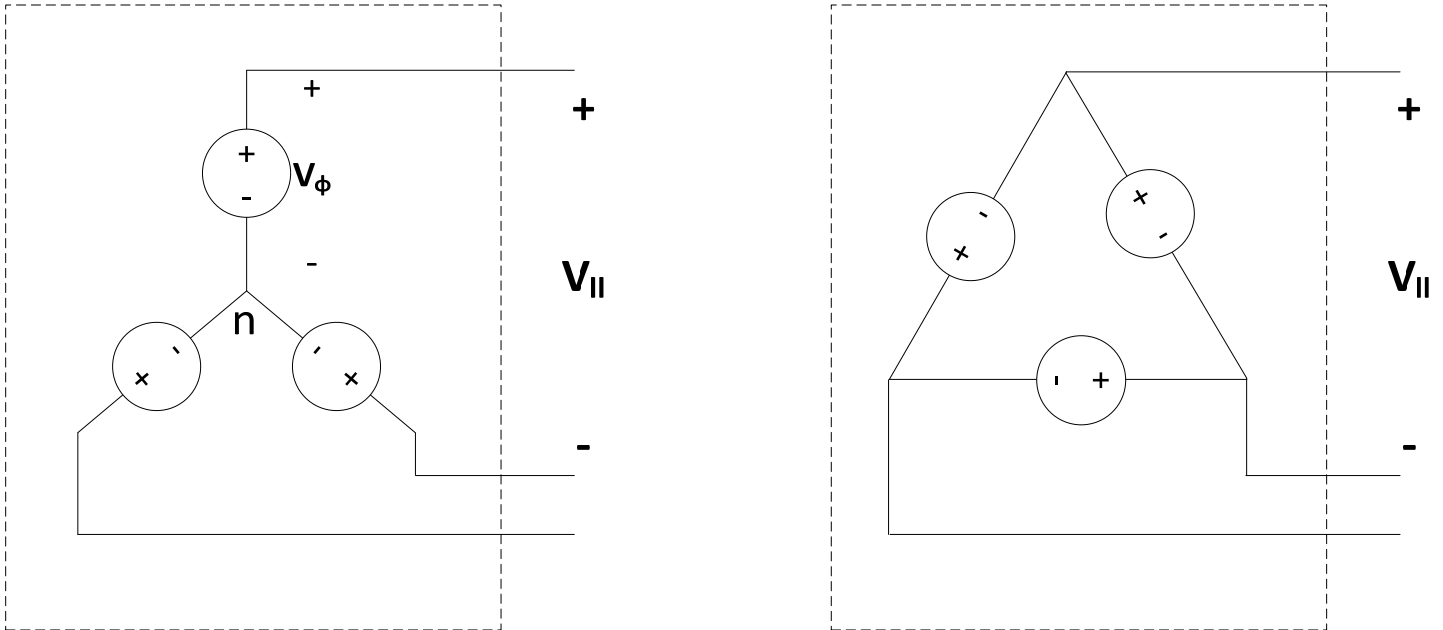


## Delta-Wye transformation

Sources:

For sources to be equivalent, the line-to-line voltage ( $V_{ll}$ ) produced by one configuration should be identical to  $V_{ll}$  produced by the other.



For the Y-connected source to be equivalent to the delta-connected source, the phase (line-to-neutral) voltage in the Y-connected source should be:


$$\overline{V_\phi} = \frac{\overline{V_{ll}}}{\sqrt{3} \angle 30^\circ}$$

For the delta-connected source to be equivalent to the Y-connected source, the phase (line-to-line) voltage in the delta connection should be the same as the line-to-line voltage in the Y connection. We can also express the phase voltage in the delta connection (line-to-line) in terms of the phase voltage in the Y connection (line-to-neutral):


$$\overline{V_{ll}} = \overline{V_\phi} \cdot \sqrt{3} \angle 30^\circ$$
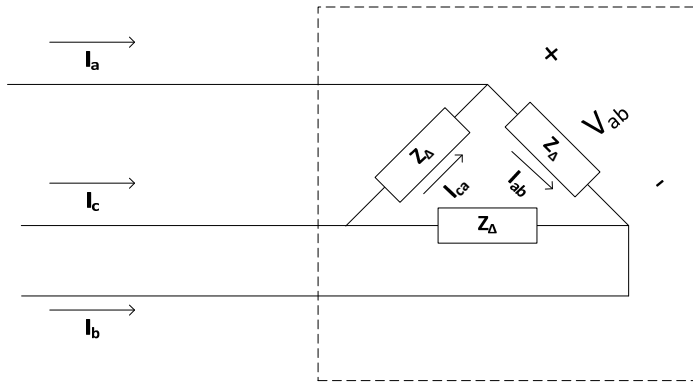
## Loads:

For loads to be equivalent, the line-to-line voltage ( $V_{ll}$ ) at the load terminals and the line current drawn by the load ( $I_l$ ) should be identical. To accomplish this, the equivalent loads should be calculated based on the following equations:



$$Z_{\Delta} = 3 \cdot Z_y$$

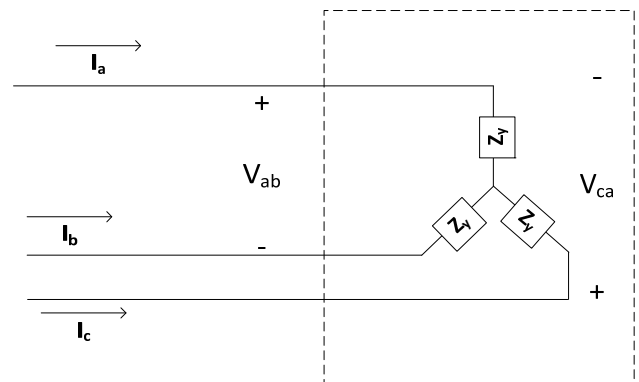

$$Z_y = \frac{Z_{\Delta}}{3}$$

**Why?**

$$\bar{V}_{ab} = Z_y \cdot \bar{I}_a - Z_y \cdot \bar{I}_b = Z_y \cdot (\bar{I}_a - \bar{I}_b) \quad [1]$$

$$\bar{V}_{ca} = Z_y \cdot (\bar{I}_c - \bar{I}_a) \quad [2]$$

For a balanced system,

$$\bar{I}_a + \bar{I}_b + \bar{I}_c = 0 \quad \therefore \bar{I}_a = -\bar{I}_b - \bar{I}_c \quad [3]$$

Subtract [2] from [1], then plug in [3]

$$\begin{aligned} \bar{V}_{ab} - \bar{V}_{ca} &= Z_y \cdot (\bar{I}_a - \bar{I}_b - \bar{I}_c + \bar{I}_a) \\ &= 3 Z_y \cdot \bar{I}_a \end{aligned}$$

$$\therefore 3 Z_y = \frac{\bar{V}_{ab} - \bar{V}_{ca}}{\bar{I}_a}$$

KCL:

$$\bar{I}_a = \bar{I}_{ab} - \bar{I}_{ca} = \frac{\bar{V}_{ab}}{Z_{\Delta}} - \frac{\bar{V}_{ca}}{Z_{\Delta}}$$

$$\therefore Z_{\Delta} = \frac{\bar{V}_{ab} - \bar{V}_{ca}}{\bar{I}_a}$$