


Set 2 Solution

3.9 (a) $a = N_1 / N_2 = 2000 / 500 = 4$

$$R_{eq1} = 2 + 0.125(4)^2 = 4 \Omega; X_{eq1} = 8 + (0.5)4^2 = 16 \Omega$$

$$\bar{Z}'_2 = 12(4)^2 = 192 \Omega$$

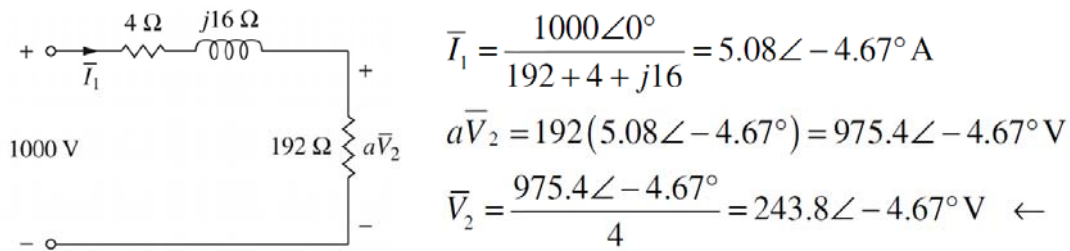The equivalent circuit referred to primary is shown below:



(b) $V_{2,NL} = V_1 / a = 1000 / 4 = 250 \text{ V}$

$$\text{Voltage Regulation} = \frac{250 - 243.8}{243.8} \times 100 = 2.54\% \leftarrow$$

3.10 Rated current magnitude on the 66-kV side is given by

$$I_1 = \frac{15,000}{66} = 227.3 \text{ A}$$

$$I_1^2 R_{eq1} = (227.3)^2 R_{eq1} = 100 \times 10^3$$

$$\therefore R_{eq1} = 1.94 \Omega \leftarrow$$

$$Z_{eq1} = \frac{5.5 \times 10^3}{227.3} = 24.2 \Omega$$

$$\text{Then } X_{eq1} = \sqrt{Z_{eq1}^2 - R_{eq1}^2} = \sqrt{(24.2)^2 - (1.94)^2} = 24.12 \Omega \leftarrow$$

3.11 Turns Ratio = $a = N_1/N_2 = 66/11.5 = 5.74$

With high-voltage side designated as 1, and L-V side as 2,

$$(11.5 \times 10^3)^2 a^2 G_{C1} = 65 \times 10^3, \text{ based on O.C test.}$$

Note: To transfer shunt admittance from H-V side to L-V side, we need to multiply by a^2 .

$$\therefore G_{C1} = \frac{65 \times 10^3}{(11.5 \times 10^3)^2 (5.74)^2} = 14.9 \times 10^{-6} \text{ S} \leftarrow$$

$$Y_1 = \frac{I_2}{V_2} \times \frac{1}{a^2} = \frac{30}{11.5 \times 10^3} \times \frac{1}{(5.74)^2} = 79.2 \times 10^{-6} \text{ S}$$

$$\therefore B_{m1} = \sqrt{Y_1^2 - G_{C1}^2} = 10^{-6} \sqrt{(79.2)^2 - (14.9)^2} \\ = 77.79 \times 10^{-6} \text{ S} \leftarrow$$

Just a long-winded way of saying:

$$G_c = P_{oc} / (V_{\text{rated, HV}})^2$$

$$\text{Identical to: } |Y| = I_{\text{HV,OC}} / V_{\text{rated, HV}}$$

In the given operating conditions (10 MW of load at 0.8 PF and rated voltage):

$$S_{\text{load}} = \frac{P_{\text{load}}}{\text{pf}} = \frac{10}{0.8} = 12.5 \text{ MVA}$$

$$I_{\text{load}}(\text{referred to HV side}) = \frac{S_{\text{load}}}{V_{\text{load, ref to HV}}} = \frac{12.5 \times 10^6}{66 \times 10^3} = 189.4 \text{ A}$$

$$\text{Losses in winding resistance} = I_{\text{load}}(\text{referred to HV side})^2 \times R_{eq,1} = 189.4^2 \times 1.94 = 69.6 \text{ KW}$$

(In the above calculation, we neglected the excitation branch current and assumed that all of I_{load} referred to HV side will go through R_{eq} . You can calculate the excitation branch current = $66\text{kV}/(G_c + jB_m)$ and subtract this from I_{load} referred to HV side to get the exact current through R_{eq} .)

Losses in $G_c = 65\text{kW}$ (from the OC test. Can you see why?)

$$\eta = \frac{10 \text{ MW}}{10 \text{ MW} + 69.6 \text{ KW} + 65 \text{ KW}} = 98.7\%$$

3.23

$$G : X = 0.18 \left(\frac{100}{90} \right) = 0.2; T_1 : X = 0.1 \left(\frac{100}{50} \right) = 0.2$$

$$T_2 : X = 0.06 \left(\frac{100}{40} \right) = 0.15; T_2 : X = 0.06 \left(\frac{100}{40} \right) = 0.15$$

$$T_3 : X = 0.064 \left(\frac{100}{40} \right) = 0.16; T_4 : X = 0.08 \left(\frac{100}{40} \right) = 0.2$$

$$M : X = 0.185 \left(\frac{100}{66.5} \right) \left(\frac{10.45}{11} \right)^2 = 0.25$$

For Line 1, $Z_{BASE} = \frac{(220)^2}{100} = 484 \Omega$ and $X = \frac{48.4}{484} = 0.1$

For Line 2, $Z_{BASE} = \frac{(110)^2}{100} = 121 \Omega$ and $X = \frac{65.43}{121} = 0.54$


The load complex power at 0.6 Lagging pf is $\bar{S}_{L(3\phi)} = 57 \angle 53.13^\circ \text{ MVA}$

\therefore The load impedance in OHMS is $\bar{Z}_L = \frac{(10.45)^2}{57 \angle -53.13^\circ} = \frac{V_{LL}^2}{\bar{S}_{L(3\phi)}^*}$
 $= 1.1495 + j1.53267 \Omega$

The base impedance for the load is $(11)^2 / 100 = 1.21 \Omega$


\therefore Load Impedance in pu $= \frac{1.1495 + j1.53267}{1.21} = 0.95 + j1.2667$

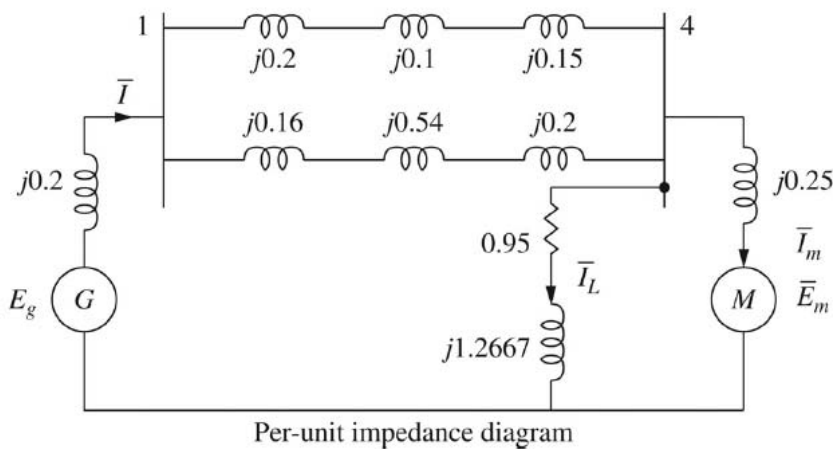The per-unit equivalent circuit is shown below:



You are not required to know how to model motors in 487, yet!
 For (steady-state) circuit analysis, motors are modelled identical to generators, i.e. they are an EMF behind an impedance. The only difference is generators produce power while motors consume it.

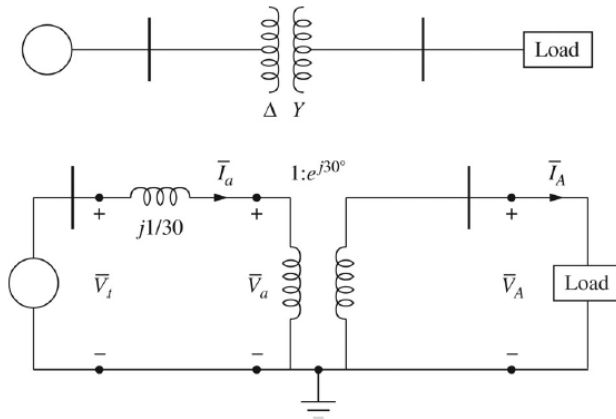- 3.38 (a) The single-line diagram and the per-phase equivalent circuit, with all parameters in per unit, are given below:



Current supplied to the load is $\frac{240 \times 10^3}{\sqrt{3} \times 230} = 602.45 \text{ A}$

Base current at the load is $100,000 / (\sqrt{3} \times 230) = 251.02 \text{ A}$

The power-factor angle of the load current is $\theta = \cos^{-1} 0.9 = 25.84^\circ \text{ Lag}$. With $\bar{V}_A = 1.0 \angle 0^\circ$ as reference, the line currents drawn by the load are

$$\begin{aligned}\bar{I}_A &= \frac{602.45}{251.02} \angle -25.84^\circ = 2.4 \angle -25.84^\circ \text{ per unit} \\ \bar{I}_B &= 2.4 \angle -25.84^\circ - 120^\circ = 2.4 \angle -145.84^\circ \text{ per unit} \\ \bar{I}_C &= 2.4 \angle -25.84^\circ + 120^\circ = 2.4 \angle 94.16^\circ \text{ per unit}\end{aligned}$$

Reminder: $\text{Pf} = \cos(\theta_v - \theta_i)$
Since we're choosing $\theta_v = 0$,
 $\theta_i = -\cos^{-1}(\text{Pf})$

- (b) Low-voltage side currents further lag by 30° because of phase shift

$$\bar{I}_a = 2.4 \angle -55.84^\circ; \bar{I}_b = 2.4 \angle 175.84^\circ; \bar{I}_c = 2.4 \angle 64.16^\circ$$

- (c) The transformer reactance modified for the chosen base is

$$X = 0.11 \times (100/330) = \frac{1}{30} \text{ pu}$$

The terminal voltage of the generator is then given by

$$\begin{aligned}\bar{V}_t &= \bar{V}_A \angle -30^\circ + jX\bar{I}_a \\ &= 1.0 \angle -30^\circ + j(1/30)(2.4 \angle -55.34^\circ) \\ &= 0.9322 - j0.4551 = 1.0374 \angle -26.02^\circ \text{ pu}\end{aligned}$$

Terminal voltage of the generator is $23 \times 1.0374 = 23.86 \text{ kV}$

The real power supplied by the generator is

$$\text{Re}[\bar{V}_t \bar{I}_a^*] = 1.0374 \times 2.4 \cos(-26.02^\circ + 55.84^\circ) = 2.16 \text{ pu}$$

which corresponds to 216 MW absorbed by the load, since there are no I^2R losses.

- (d) By omitting the phase shift of the transformer altogether, recalculating \bar{V}_t with the reactance $j\left(\frac{1}{30}\right)$ on the high-voltage side, the student will find the same value for V_t i.e. $|\bar{V}_t|$.

3.49 Base kV in transmission-line circuit = 132 kV

$$\text{Base kV in the generator } G_1 \text{ circuit} = 132 \times \frac{13.2}{165} = 10.56 \text{ kV}$$

$$\text{Base kV in the generator } G_2 \text{ circuit} = 132 \times \frac{13.8}{165} = 11.04 \text{ kV}$$

On the common base of 100 MVA for the entire system,

$$G_1 : \bar{Z} = j0.15 \times \frac{100}{50} \times \left(\frac{13.2}{10.56}\right)^2 = j0.4688 \text{ pu}$$

$$G_2 : \bar{Z} = j0.15 \times \frac{100}{20} \times \left(\frac{13.8}{11.04}\right)^2 = j1.1719 \text{ pu}$$

$$T_1 : \bar{Z} = j0.1 \times \frac{100}{80} \times \left(\frac{13.2}{10.56}\right)^2 = j0.1953 \text{ pu}$$

$$T_2 : \bar{Z} = j0.1 \times \frac{100}{40} \times \left(\frac{13.8}{11.04}\right)^2 = j0.3906 \text{ pu}$$

Base impedance in transmission-line circuit is

$$\frac{(132)^2}{100} = 174.24 \Omega$$

$$\bar{Z}_{TR.LINE 1} = \frac{50 \times j200}{174.24} = 0.287 + j1.1478 \text{ pu}$$


$$\bar{Z}_{TR.LINE 2} = \frac{25 \times j100}{174.24} = 0.1435 + j0.5739 \text{ pu}$$

$$LOAD : 40(0.8 + j0.6) = (32 + j24) \text{ MVA}$$

$$R_{LOAD} = \frac{(150)^2}{32} = 703.1 \Omega = \frac{703.1}{174.24} \text{ pu} = 4.035 \text{ pu}$$

$$X_{LOAD} = \frac{(150)^2}{24} = 937.5 \Omega = \frac{937.5}{174.24} \text{ pu} = 5.381 \text{ pu}$$
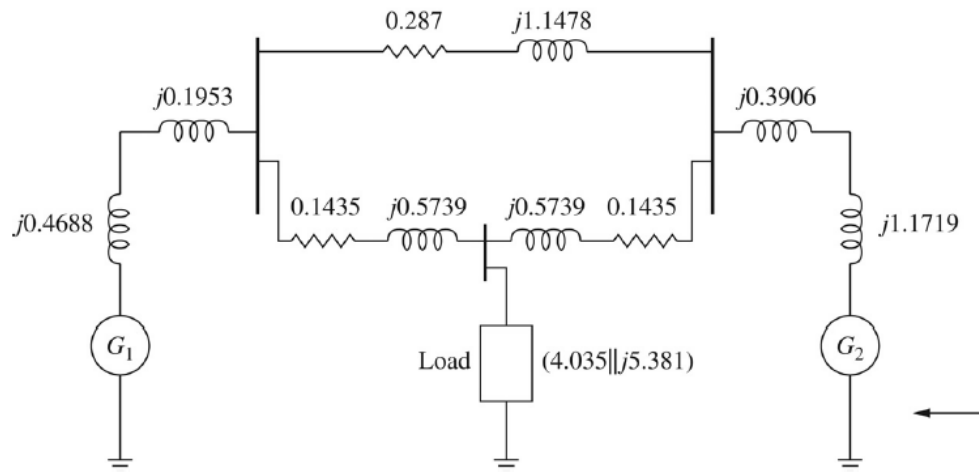
$$\bar{Z}_{LOAD} = (R_{LOAD} \parallel jX_{LOAD})$$



Impedance diagram of the system with pu values