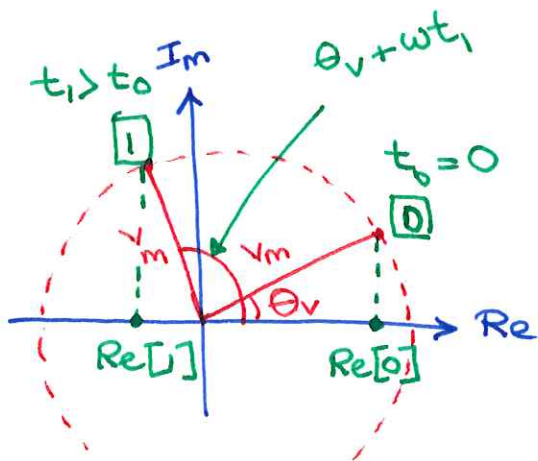


Tutorial 1

Phasors : $V_m \cos(\omega t + \theta_v) = \text{Re} [V_m e^{j(\omega t + \theta_v)}]$


Can we plot $V_m e^{j(\omega t + \theta_v)}$? This is a polar number (vector) with magnitude V_m and time-varying phase $(\omega t + \theta_v)$



$$V_m e^{j(\omega t + \theta_v)}$$


- rotates ccw in complex plane
- $V_m \angle \theta_v$ is a snapshot at $t=0$

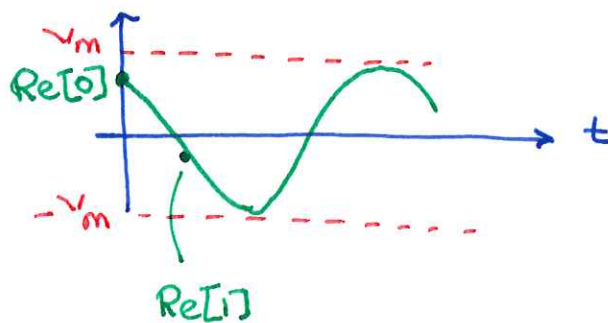$V_m \cos(\omega t + \theta_v)$ is the projection of this rotating vector on the real axis



Leading & Lagging

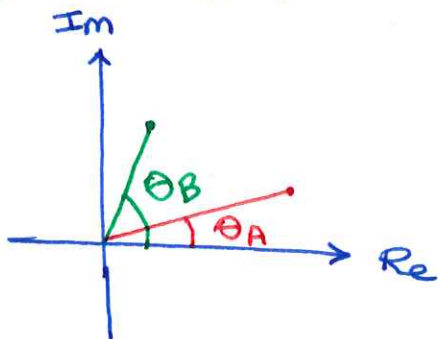- Try to keep phase angles between -180° & 180°




$\theta_B > \theta_A \therefore$ phasor B leads A

. To remember ∇ & Ξ relationship for L & C:

$\begin{matrix} E & L & I \\ \uparrow & & \uparrow \\ \text{voltage leads} & & \text{current} \end{matrix}$



 the
 $\begin{matrix} I & C & E \\ \uparrow & & \uparrow \\ \text{current leads} & & \text{voltage} \end{matrix}$
 man!

. Let's revisit the class example:

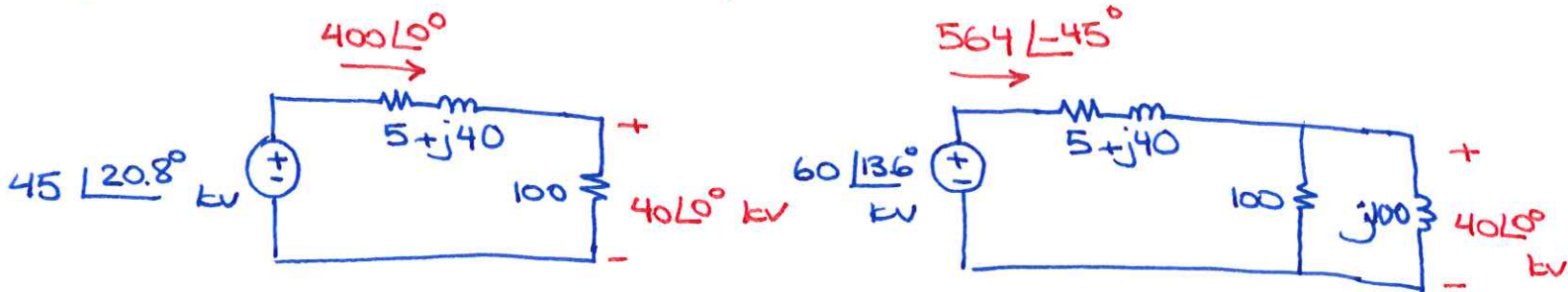

Question 1 :

. Source Power Triangle

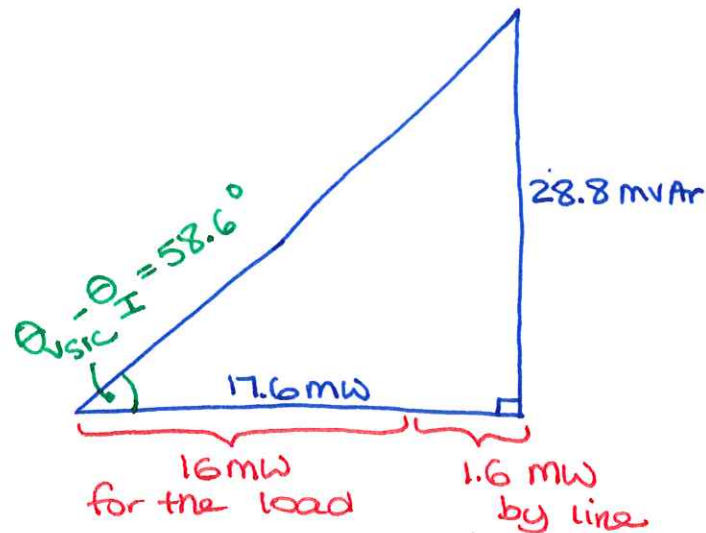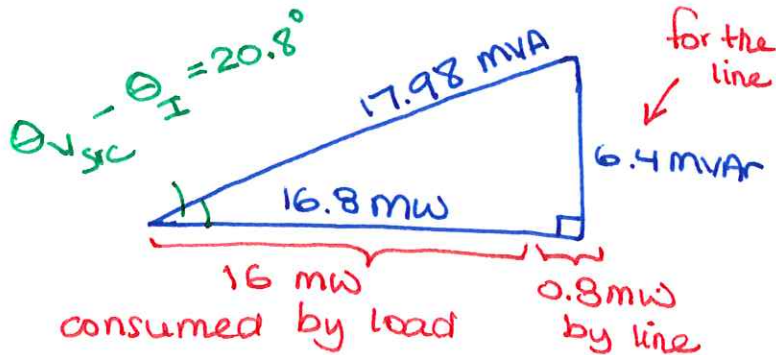


higher line current results in more line losses.

. Load power triangle

16 mW, 16 mVA



Power triangle with $Q=0$
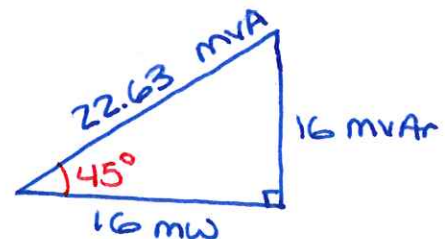
$$PF = \frac{P}{S} = \cos(\theta_{V_{load}} - \theta_I) = 1$$





$$\begin{aligned}
 \bar{S}_{load} &= \bar{V}_{load} \cdot \bar{I}^* \\
 &= (40 \angle 0^\circ \text{ kV}) (564 \angle +45^\circ) \\
 &= \underbrace{16}_{P(\text{mW})} + j \underbrace{16}_{Q(\text{mVAR})}
 \end{aligned}$$

Question 2 :

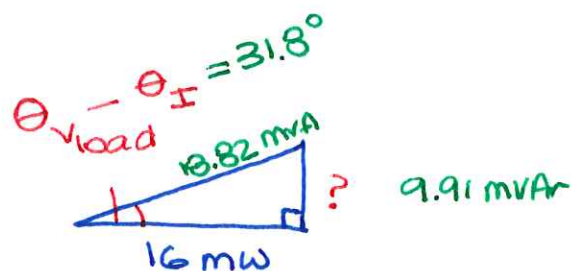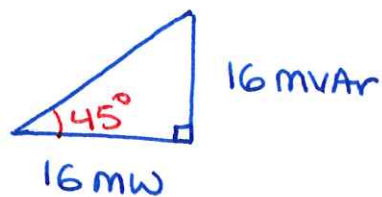

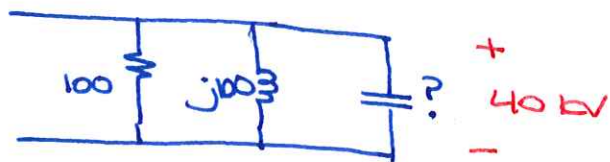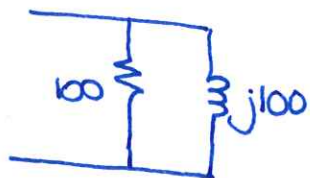usually not allowed to change real power requirement



In the new configuration, $\theta_{V_{load}} - \theta_I = \cos^{-1}(0.85) = \pm 31.8^\circ$

lagging PF $\therefore \theta_I < \theta_V \therefore \theta_V - \theta_I > 0$

$$S_{new} = \frac{P}{PF_{new}} = \frac{16 \text{ mW}}{0.85} = 18.82 \text{ mVA}$$

$$Q_{new} = \sqrt{S_{new}^2 - P_{new}^2} = 9.91 \text{ mVAr}$$

Need to "supply" Q of $16 - 9.91 = 6.083 \text{ mVAr}$ by adding a capacitor.

$$Q_{cap} = \frac{V^2}{X_{cap}} \therefore X_{cap} = \frac{V^2}{Q_{cap}} = \frac{(40 \text{ kV})^2}{-6.083 \text{ mVAr}} = -263 \Omega$$

"supply" Q

$$X_{cap} = \frac{-1}{\omega C} \therefore C = \frac{-1}{\omega \cdot X_{cap}} = \frac{-1}{2\pi \times 60 \times (-263)} = 10.1 \mu\text{F}$$

we can assume North American $f = 60 \text{ Hz}$