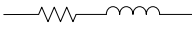


## Transmission line voltage and current equations

Transmission line models used in previous topics looked like: 

$$Z = R + jX = R + j\omega L$$

We ignored the line capacitance in these models.

In part 1 of topic 5, we came up with equations to calculate the distributed inductance (H/m) and distributed capacitance (F/m)

Objective of part 2: Determine how to model (lump) this all together.

Consider a small portion of the line with length  $\Delta x$ :

$z = R + j\omega L$  where:

$R$  is in  $\Omega/\text{m}$  &

$L$  is in  $\text{H}/\text{m}$

$y = j\omega C$  where

$C$  is in  $\text{F}/\text{m}$

From KVL:  $V(x + \Delta x) = V(x) + z \cdot \Delta x \cdot I(x)$       Therefore:  $\frac{V(x+\Delta x) - V(x)}{\Delta x} = z \cdot I(x)$

From KVL:  $I(x + \Delta x) = I(x) + V(x + \Delta x) y \cdot \Delta x$       Therefore:  $\frac{I(x+\Delta x) - I(x)}{\Delta x} = y \cdot V(x + \Delta x)$

Combine (i) and (ii) to get:  $V(x) = K_1 \cdot \cosh(\gamma x) + K_2 \cdot \sinh(\gamma x)$  where  $\gamma = \sqrt{y \cdot z}$  propagation constant (1/m)

If we know  $V$  and  $I$  at one end, e.g. receiving end ( $x=0$ ):  $V_R = V(0)$  and  $I_R = I(0)$ , we can find  $K_1$  and  $K_2$  :

$$V(x) = V_R \cdot \cosh(\gamma x) + I_R Z_c \cdot \sinh(\gamma x) \quad \text{where} \quad Z_c = \sqrt{z/y} \quad \text{characteristic impedance } (\Omega)$$

Similar derivation for  $I(x)$  gives:  $I(x) = I_R \cdot \cosh(\gamma x) + \frac{V_R}{Z_c} \cdot \sinh(\gamma x)$

Eq (1) and (2) give us voltage and current at any point  $x$  along the line ( $x$  is the distance from the receiving end)

Note: voltage and current in above expressions are phasors.