

Tutorial 1

Both questions are based on the class example for Topic 1

- 1)** Draw the power triangles for the source and the load (before and after addition of the inductive element)
- 2)** To reduce line losses, the inductive load in that example has been asked to improve its power factor to 0.85 lagging. What size capacitor is needed to accomplish this?