Solutions to the following problem from the text book are provided here:

**Topic 1:** 2.13, 2.22, 2.24, 2.28,

Topic 2: 2.44, 2.46, 2.52

2.13 
$$\overline{Z} = R - jx_c = 10 - j25 = 26.93 \angle -68.2^{\circ} \Omega$$
  
 $i(t) = (359.3/26.93)\cos(\omega t + 68.2^{\circ})$   
 $= 13.34\cos(\omega t + 68.2^{\circ})A$ 

(a) 
$$p_R(t) = [13.34\cos(\omega t + 68.2^\circ)][133.4\cos(\omega t + 68.2^\circ)]$$
  
=  $889.8 + 889.8\cos[2(\omega t + 68.2^\circ)]W$ 

(b) 
$$p_x(t) = [13.34\cos(\omega t + 68.2^\circ)][333.5\cos(\omega t + 68.2^\circ - 90^\circ)]$$
  
=  $2224\sin[2(\omega t + 68.2^\circ)]W$ 

(c) 
$$P = I^2 R = (13.34/\sqrt{2})^2 10 = 889.8 \text{ W}$$

(d) 
$$Q = I^2 X = (13.34/\sqrt{2})^2 25 = 2224 \text{ VAR S}$$

(e) 
$$pf = \cos\left[\tan^{-1}(Q/P)\right] = \cos\left[\tan^{-1}(2224/889.8)\right]$$
  
=0.3714 Leading

2.22 (a) 
$$\overline{Y}_1 = \frac{1}{\overline{Z}_1} = \frac{1}{(3+j4)} = \frac{1}{5\angle 53.13^{\circ}} = 0.2\angle -53.13^{\circ}$$

$$= (0.12-j0.16) S$$

$$\overline{Y}_2 = \frac{1}{\overline{Z}_2} = \frac{1}{10} = 0.1 S$$

$$P = V^2 (G_1 + G_2) \Rightarrow V = \sqrt{\frac{P}{G_1 + G_2}} = \sqrt{\frac{1100}{(0.12+0.1)}} = 70.71 \text{ V}$$

$$P_1 = V^2 G_1 = (70.71)^2 \ 0.12 = 600 \text{ W}$$

$$P_2 = V^2 G_2 = (70.71)^2 \ 0.1 = 500 \text{ W}$$
(b)  $\overline{Y}_{eq} = \overline{Y}_1 + \overline{Y}_2 = (0.12 - j0.16) + 0.1 = 0.22 - j0.16$ 

$$= 0.272 \angle -36.03^{\circ} S$$

 $I_s = V Y_{eq} = 70.71(0.272) = 19.23 A$ 

2.24 
$$\overline{S}_1 = P_1 + jQ_1 = 10 + j0$$
;  $\overline{S}_2 = 10\angle\cos^{-1}0.9 = 9 + j4.359$   
 $\overline{S}_3 = \frac{10\times0.746}{0.85\times0.95} \angle -\cos^{-1}0.95 = 9.238\angle -18.19^\circ = 8.776 - j2.885$   
 $\overline{S}_S = \overline{S}_1 + \overline{S}_2 + \overline{S}_3 = 27.78 + j1.474 = 27.82\angle3.04^\circ$   
 $P_S = \text{Re}(\overline{S}_S) = 27.78 \,\text{kW}$   
 $Q_S = \text{Im}(\overline{S}_S) = 1.474 \,\text{kVAR}$   
 $S_S = |\overline{S}_S| = 27.82 \,\text{kVA}$   
 $Q_S = 1.474 \,\text{kVAR}$ 

2.28 
$$\overline{S}_1 = 12 + j6.667$$
  
 $\overline{S}_2 = 4(0.96) - j4 \left[ \sin(\cos^{-1} 0.96) \right] = 3.84 - j1.12$   
 $\overline{S}_3 = 15 + j0$   
 $\overline{S}_{TOTAL} = \overline{S}_1 + \overline{S}_2 + \overline{S}_3 = (30.84 + j5.547) \text{kVA}$ 


(i) Let  $\overline{Z}$  be the impedance of a series combination of R and X

Since 
$$\overline{S} = \overline{V} \, \overline{I}^* = \overline{V} \left( \frac{\overline{V}}{\overline{Z}} \right)^* = \frac{V^2}{\overline{Z}^*}$$
, it follows that 
$$\overline{Z}^* = \frac{V^2}{\overline{S}} = \frac{(240)^2}{(30.84 + j5.547)10^3} = (1.809 - j0.3254) \, \Omega$$
$$\therefore \overline{Z} = (1.809 + j0.3254) \, \Omega \quad \leftarrow$$

(ii) Let  $\overline{Z}$  be the impedance of a parallel combination of R and X

Then 
$$R = \frac{(240)^2}{(30.84)10^3} = 1.8677 \,\Omega$$
$$X = \frac{(240)^2}{(5.547)10^3} = 10.3838 \,\Omega$$
$$\therefore \overline{Z} = (1.8677 || j10.3838) \,\Omega \quad \leftarrow$$

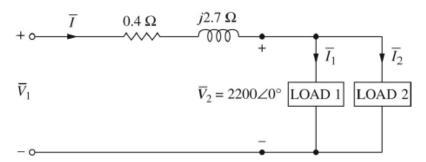2.44 (a) The per-phase equivalent circuit for the problem is shown below:



Phase voltage at the load terminals is  $V_2 = \frac{2200\sqrt{3}}{\sqrt{3}} = 2200 \,\text{V}$  taken as Ref.

Total complex power at the load end or receiving end is

$$\overline{S}_{R(3\phi)} = 560.1(0.707 + j0.707) + 132 = 528 + j396 = 660 \angle 36.87^{\circ} \text{kVA}$$

With phase voltage  $\overline{V}_2$  as reference,

$$\overline{I} = \frac{\overline{S}_{R(3\phi)}^*}{3\overline{V}_2^*} = \frac{660,000\angle - 36.87^\circ}{3(2200\angle 0^\circ)} = 100\angle - 36.87^\circ A$$

Phase voltage at sending end is given by

$$\overline{V_1} = 2200 \angle 0^\circ + (0.4 + j2.7)(100 \angle -36.87^\circ) = 2401.7 \angle 4.58^\circ \text{V}$$

The magnitude of the line to line voltage at the sending end of the line is

$$(V_1)_{L=L} = \sqrt{3}V_1 = \sqrt{3}(2401.7) = 4160 \text{ V}$$


(b) The three-phase complex-power loss in the line is given by

$$\overline{S}_{L(3\phi)} = 3RI^2 + j3 \times I^2 = 3(0.4)(100^2) + j3(2.7)(100)^2$$
  
= 12 kW+ j81 kVAR

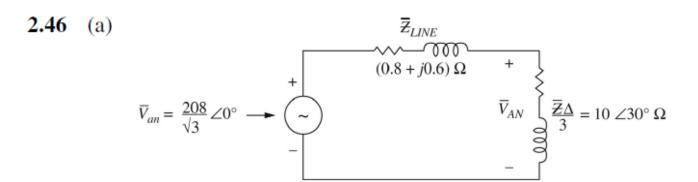(c) The three-phase sending power is

$$\overline{S}_{S(3\phi)} = 3\overline{V}_1 \overline{I}^* = 3(2401.7 \angle 4.58^\circ)(100 \angle 36.87^\circ)$$
  
= 540 kW+ j477 kVAR

Note that  $\overline{S}_{S(3\phi)} = \overline{S}_{R(3\phi)} + \overline{S}_{L(3\phi)}$ 



Using voltage division: 
$$\overline{V}_{AN} = \overline{V}_{an} \frac{\overline{Z}_{\Delta}/3}{(\overline{Z}_{\Delta}/3) + \overline{Z}_{LINE}}$$

$$= \frac{208}{\sqrt{3}} \angle 0^{\circ} \frac{10 \angle 30^{\circ}}{10 \angle 30^{\circ} + (0.8 + j0.6)}$$

$$= \frac{(120.09)(10 \angle 30^{\circ})}{9.46 + j5.6} = \frac{1200.9 \angle 30^{\circ}}{10.99 \angle 30.62^{\circ}}$$

$$= 109.3 \angle -0.62^{\circ} \text{ V}$$

Load voltage =  $V_{AB} = \sqrt{3} (109.3) = 189.3 \text{ V Line-to-Line}$ 

(b) 
$$\overline{V}_{an} = \frac{208}{\sqrt{3}} \text{ V}$$

$$\frac{\overline{Z}_{eq}}{=10 \angle 30^{\circ} || (-j20)}$$
$$=11.547 \angle 0^{\circ} \Omega$$

$$\overline{V}_{AN} = \overline{V}_{an} \frac{\overline{Z}_{eq}}{\overline{Z}_{eq} + \overline{Z}_{LINE}}$$

$$= \left(208/\sqrt{3}\right) \frac{11.547}{\left(11.547 + 0.8 + j0.6\right)}$$

$$= \frac{1386.7}{12.362/2.78^{\circ}} = 112.2\angle - 2.78^{\circ} \text{ V}$$

Load voltage Line-to-Line  $V_{AB} = \sqrt{3} (112.2) = 194.3 \text{ V}$ 

2.52 (a) Let 
$$\overline{V}_{AN}$$
 be the reference:  $\overline{V}_{AN} = \frac{2160}{\sqrt{3}} \angle 0^{\circ} \simeq 2400 \angle 0^{\circ} \text{ V}$   
Total impedance per phase  $\overline{Z} = (4.7 + j9) + (0.3 + j1) = (5 + j10) \Omega$ 

:. Line Current = 
$$\frac{2400\angle 0^{\circ}}{5+j10}$$
 = 214.7\(\neq -63.4\(^{\chi}\)A =  $\overline{I}_A$  \(\infty\)

With positive A-B-C phase sequence,

$$\overline{I}_B = 214.7 \angle -183.4^{\circ} \text{ A}; \overline{I}_C = 214.7 \angle -303.4^{\circ} = 214.7 \angle 56.6^{\circ} \text{ A} \leftarrow$$

(b) 
$$(\overline{V}_{A'N})_{LOAD} = 2400\angle 0^{\circ} - [(214.7\angle -63.4^{\circ})(0.3 + j1)]$$
  
 $= 2400\angle 0^{\circ} - 224.15\angle 9.9^{\circ} = 2179.2 - j38.54$   
 $= 2179.5\angle -1.01^{\circ}V \leftarrow$   
 $(\overline{V}_{B'N})_{LOAD} = 2179.5\angle -121.01^{\circ}V^{\Box}; (V_{C'N})_{LOAD} = 2179.5\angle -241.01^{\circ}V^{\Box}$ 

(c) S/Phase =  $(V_{A'N})_{LOAD} I_A = (2179.5)(214.7) = 467.94 \text{ kVA} \leftarrow$ Total apparent power dissipated in all three phases in the load

$$[S_{3\phi}]_{LOAD} = 3(467.94) = 1403.82 \text{ kVA} \leftarrow$$

Active power dissipated per phase in load =  $\left(P_{1\phi}\right)_{LOAD}$ 

$$= (2179.5)(214.7)\cos(62.39^{\circ}) = 216.87 \,\text{kW} \leftarrow$$
$$\therefore \left[ P_{3\phi} \right]_{LOAD} = 3(216.87) = 650.61 \,\text{kW} \leftarrow$$

Reactive power dissipated per phase in load =  $\left(Q_{1\phi}\right)_{LOAD}$ 

$$=(2179.5)(214.7)\sin(62.39^{\circ}) = 414.65 \text{ kVAR} \leftarrow$$

$$: [Q_{3\phi}]_{LOAD} = 3(414.65) = 1243.95 \text{ kVAR} \leftarrow$$

(d) Line losses per phase  $(P_{1\phi})_{LOSS} = (214.7)^2 \ 0.3 = 13.83 \text{ kW} \leftarrow$ Total line loss  $(P_{3\phi})_{LOSS} = 13.83 \times 3 = 41.49 \text{ kW} \leftarrow$