

$$= \underbrace{-16.8 \text{ mW}}_P - j \underbrace{6.4 \text{ mVAR}}_Q$$


supplies 16.8 mW

$Q = -6.4 \text{ mVAR}$
"supplies" reactive power

• Load power factor = 1 (unity PF)

$Q_{\text{load}} = 0$ since no reactive element.

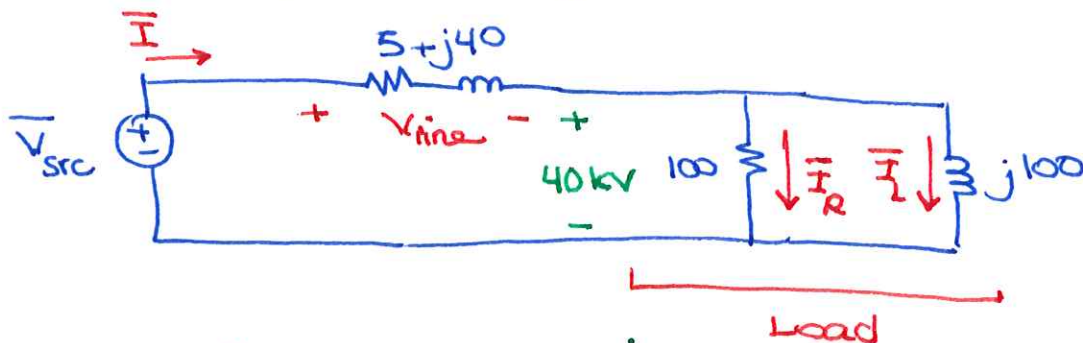• Repeat last example with an inductance added to the load
(to model txfrs, motors, etc.)



$$Z_{\text{load}} = 100 \parallel j100 = \frac{100 \times j100}{100 + j100} = 70.7 \angle 45^\circ \Omega$$

$$\theta_Z = 45^\circ$$

$\therefore \theta_V - \theta_I = 45^\circ$ for combined load

$$\text{Load PF} = \cos(\theta_V - \theta_I) = \cos(\theta_Z) = \cos(45^\circ) = 0.707 \text{ lagging}$$

$$\bar{I} = \frac{40 \text{ kV}}{Z_{\text{load}}} = \frac{40000 \angle 0^\circ}{70.7 \angle 45^\circ} = 564 \angle -45^\circ \text{ A}$$

$$\begin{aligned} \bar{V}_{\text{src}} &= \bar{V}_{\text{line}} + 40 \text{ kV} = (564 \angle -45^\circ)(5 + j40) + 40000 \\ &= 59.7 \angle 13.6^\circ \text{ kV} \end{aligned}$$

$$\bar{S}_{\text{src}} = - \bar{V}_{\text{src}} \cdot \bar{I}^* = - (59.7 \angle 13.6^\circ) (564 \angle 45^\circ) \text{ mVA}$$

$$= \underbrace{-17.6 \text{ mW}}_P - j \underbrace{28.8 \text{ mVAR}}_Q$$

- Reactive power required by the load resulted in higher current which resulted in higher real power losses in the line.

Solution: Adding power factor correction capacitors on the load side. This will bring θ_Z closer to 0° thereby reducing I in the line. i.e. Q required by inductive elements of the load now supplied by local capacitor instead of the source.

- Alternative solution: we can find P_{load} using $\frac{V_{load}^2}{R}$ $\leftarrow 40kV$
 $\leftarrow 100\Omega$
 or $I_R^2 \cdot R$, Q_{load} using $\frac{V_{load}^2}{X}$ $\leftarrow 40kV$
 $\leftarrow 100\Omega$ or $I_L^2 \cdot X$

$$P_{line} = I^2 \cdot R_{line} \quad , \quad Q_{line} = I^2 \cdot X_{line}$$

\uparrow \uparrow \uparrow \uparrow
 564 5 100 40

then: $P_{src} = P_{load} + P_{line}$, $Q_{src} = Q_{load} + Q_{line}$

- When calculating P_{line} , can we use $\frac{V_{line}^2}{R_{line}}$?

No, V_{line} is the voltage across the complex impedance

$5 + j40$. we need the voltage across the 5Ω resistor only

to use in $\frac{V^2}{R}$ equation.

- Important : Elements in a power system operate at or near distinct, pre-defined voltage levels called rated or nominal voltage.

Example : 120 V , 240 V , 600 V , 13.8 kV , 25 kV , ...

Gen & distributed rated or nominal voltages

and 69 kV , 138 kV , 240 kV , 500 kV

transmission rated or nominal voltage

- Nominal voltage of the outlets in your house is 120 V (always).

Operating voltage of the outlet changes based on operating conditions (but it should be close to the nominal voltage under normal conditions).


e.g. ^{op.} voltage of the outlet could be 118 V , 125 V , etc.

- When solving a circuit , we must use the operating voltage
- Can't assume op. voltage = nominal (or rated) voltage unless explicitly stated.

Motor Nameplate example

shows rated values for this motor

rated
output
mech
power,
 P_{mech}

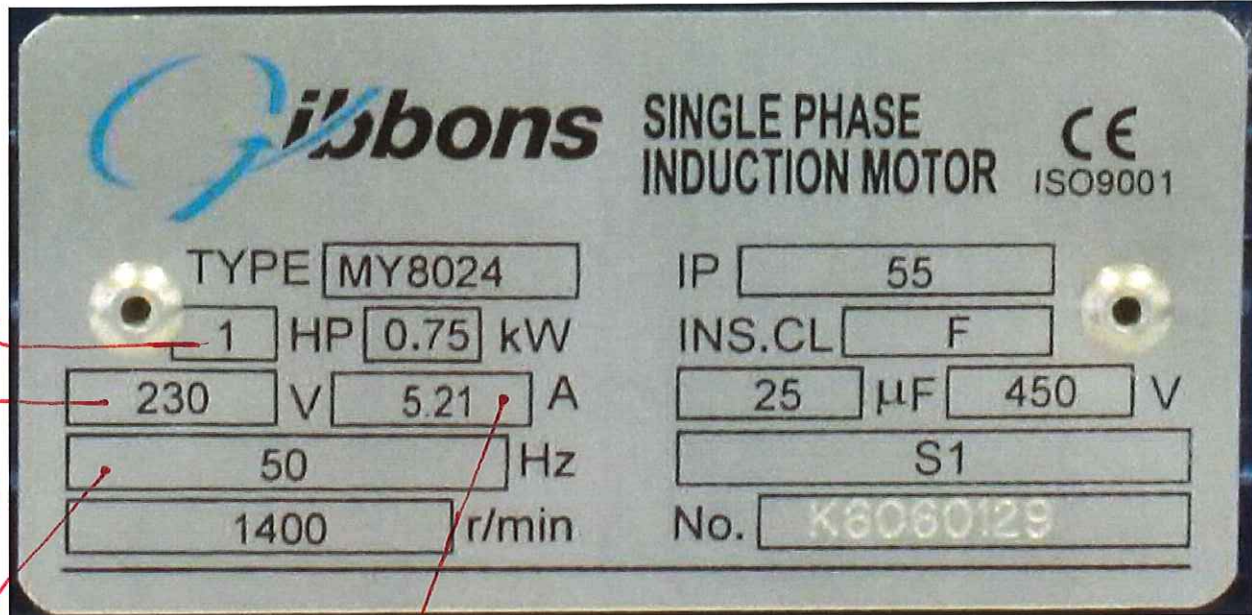

rated
(nominal)
voltage


European!

$$1 \text{ HP} = 746 \text{ W}$$

rated (full load) current

Draws 5.21 A when operating at rated conditions
(delivering 1 HP with an operating voltage of 230V)
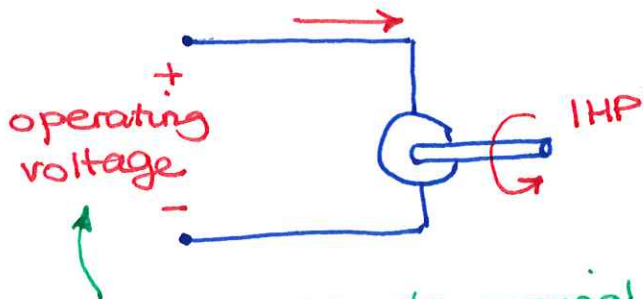
$$I = 5.21 \text{ A if op voltage} = 230 \text{ V}$$




should be close to nominal voltage of 230V

. if op voltage is 220 V (for example), the motor will draw

$$5.21 \times \frac{230}{220} \text{ to maintain the same output power.}$$

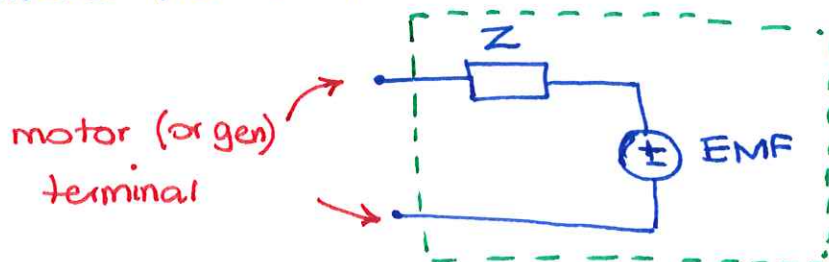. We will model motors (and generator) as:




$$S_{\text{rated}} = V_{\text{rated}} \times I_{\text{rated}} = 230 \text{ V} \times 5.21 \text{ A} = 1.2 \text{ kVA}$$

Assuming 100% efficient motor i.e. $P_{\text{elec input}} = P_{\text{mech}} = 0.75 \text{ kW}$,

then we can calculate Q :


positive
power
angle
Motor is
inductive

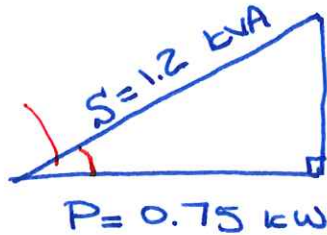


$$Q = \sqrt{1.2^2 - 0.75^2} = 0.94 \text{ kVAr}$$

Topic 2: Three Phase Systems


- So far, all AC circuits looked like:

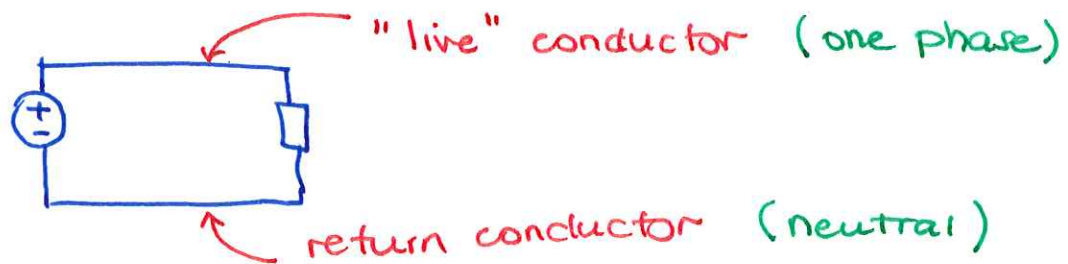

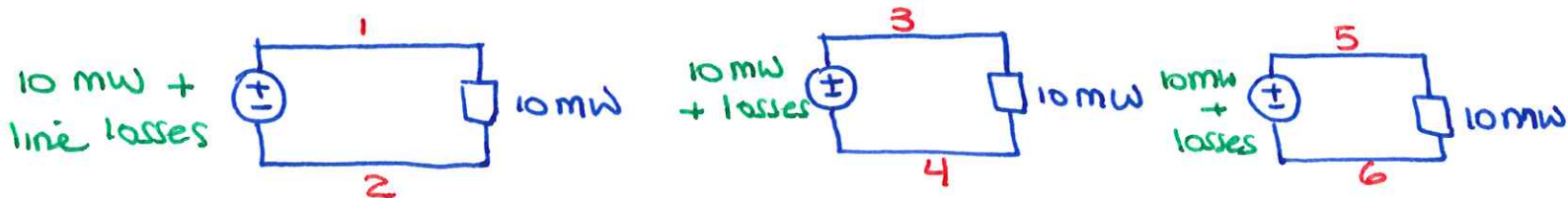- Suppose we have 3 identical loads at 10 MW (for example). We can create 3 single phase systems:



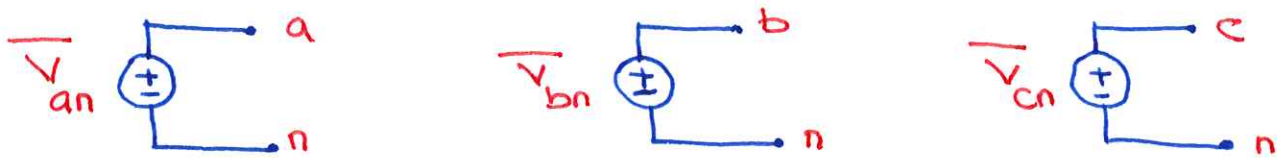- Total of 6 conductors from gen to load. These can be 100's of km long.
- In each gen, instantaneous elec power ($p(t)$ from eq (i) in Topic 1) is time-varying but the input mech power is constant. This results in vibration & noise.
- Consider 3 single phase sources:




- if :
- voltage magnitudes are the same $V_{an} = V_{bn} = V_{cn}$
 - voltage phases are 120° apart


then, by connecting these 3 we will create a balanced three phase source. (See handout on AC generation)

Yani's cheap plastic AC generation handout

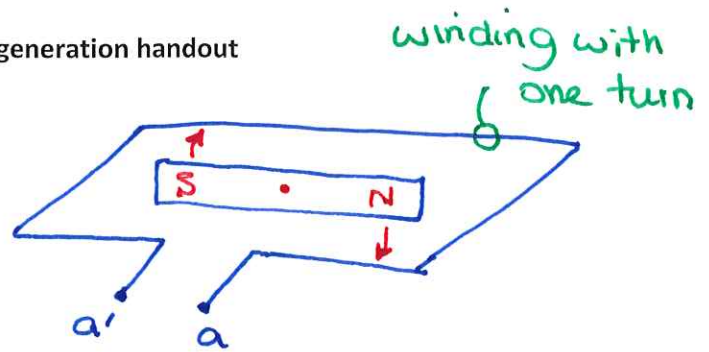
Consider this very simplified representation of an AC generator:



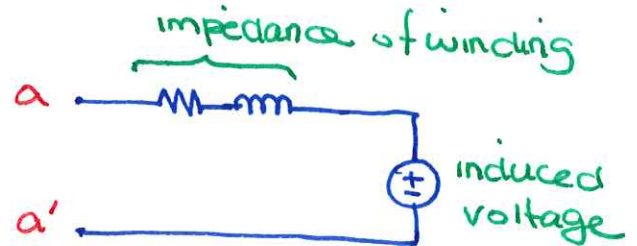The rotating magnetic field induces a voltage across the aa' winding. The electrical representation of that is:




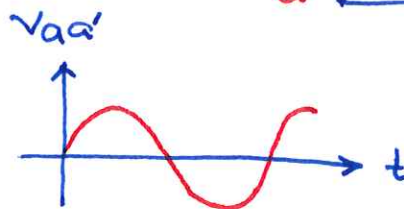This produces sinusoidal voltage/current:




Consider the cross-sectional view of this generator:

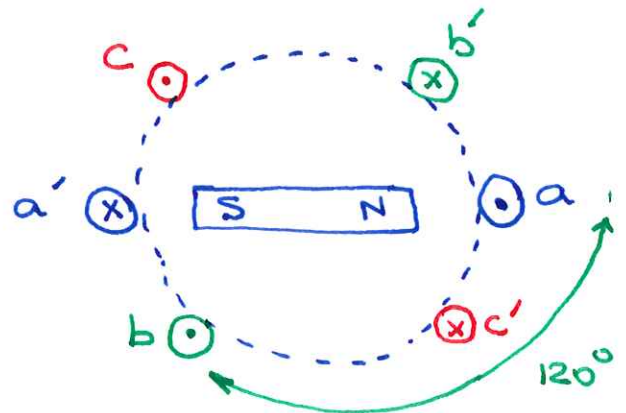Let's add two other windings bb' and cc', all separated at 120°





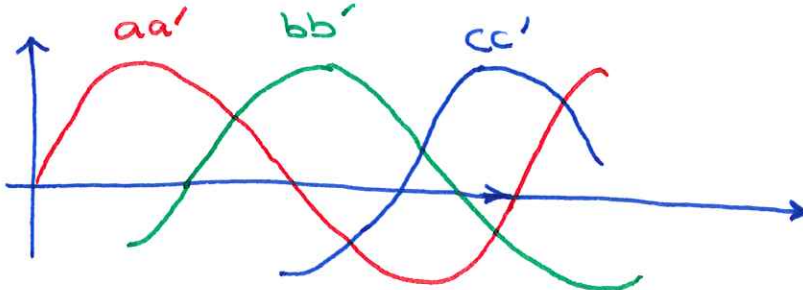The voltages induced on these windings will be 120° apart:




Two ways to connect the three windings:

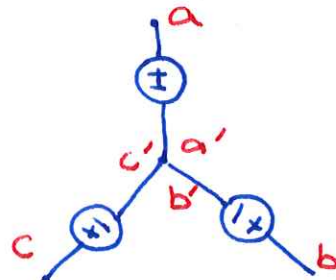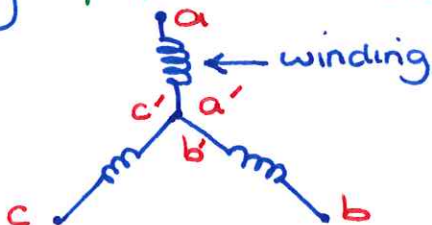① physical connection \rightarrow elec equivalent




• ignored winding Z here!


② physical:

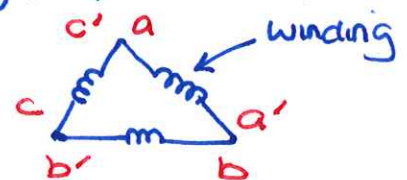

electrical equivalent:

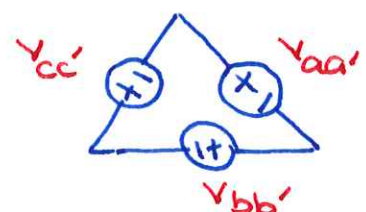

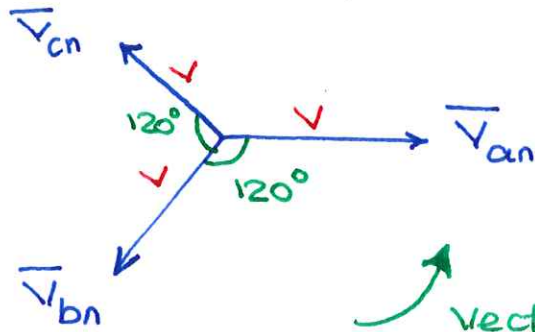For example, \overline{V}_{an} , \overline{V}_{bn} , and \overline{V}_{cn} for a balanced three phase source can look like:



$$\overline{V}_{an} = V \angle 0^\circ$$

$$\overline{V}_{bn} = V \angle -120^\circ$$

$$\overline{V}_{cn} = V \angle +120^\circ$$

→ vectors rotate ccw

this is an abc (positive) rotation; phase a followed by phase b followed by phase c.

$$\overline{V}_{an} + \overline{V}_{bn} + \overline{V}_{cn} = 0$$


• Two ways to connect three-phase (3ϕ) sources & loads:

Wye/star (Y) or Delta (Δ)

* this does not apply to lines

Wye - Connected Source

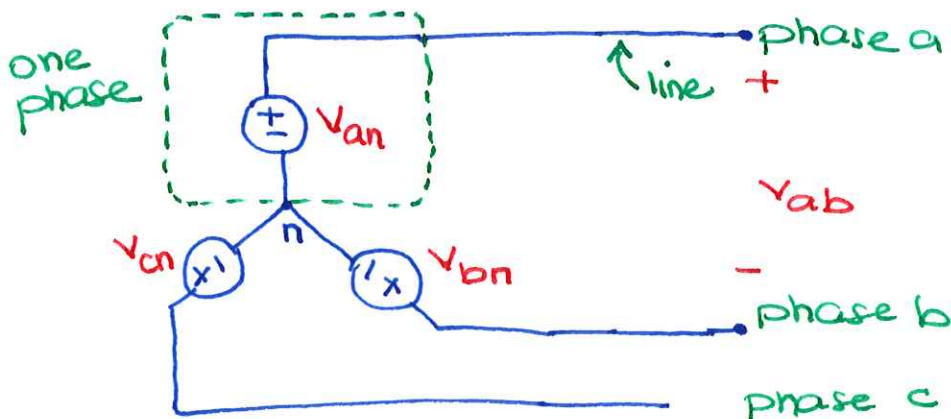
• Same terminology applies to Y-connected loads.



V_{an} , V_{bn} , V_{cn} : line-to-neutral (phase-to-neutral) voltages


V_{ab} , V_{bc} , V_{ca} : line-to-line (phase-to-phase) voltages

Δ -connected Source

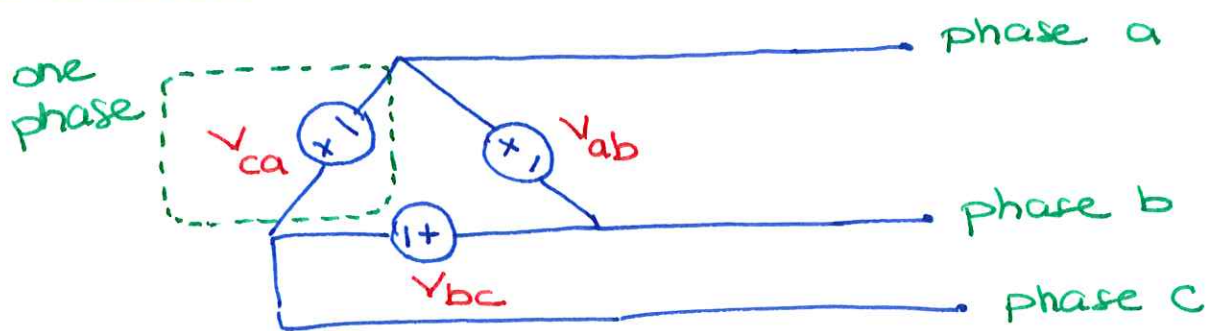

V_{ab} , V_{bc} , V_{ca} : line-to-line voltage

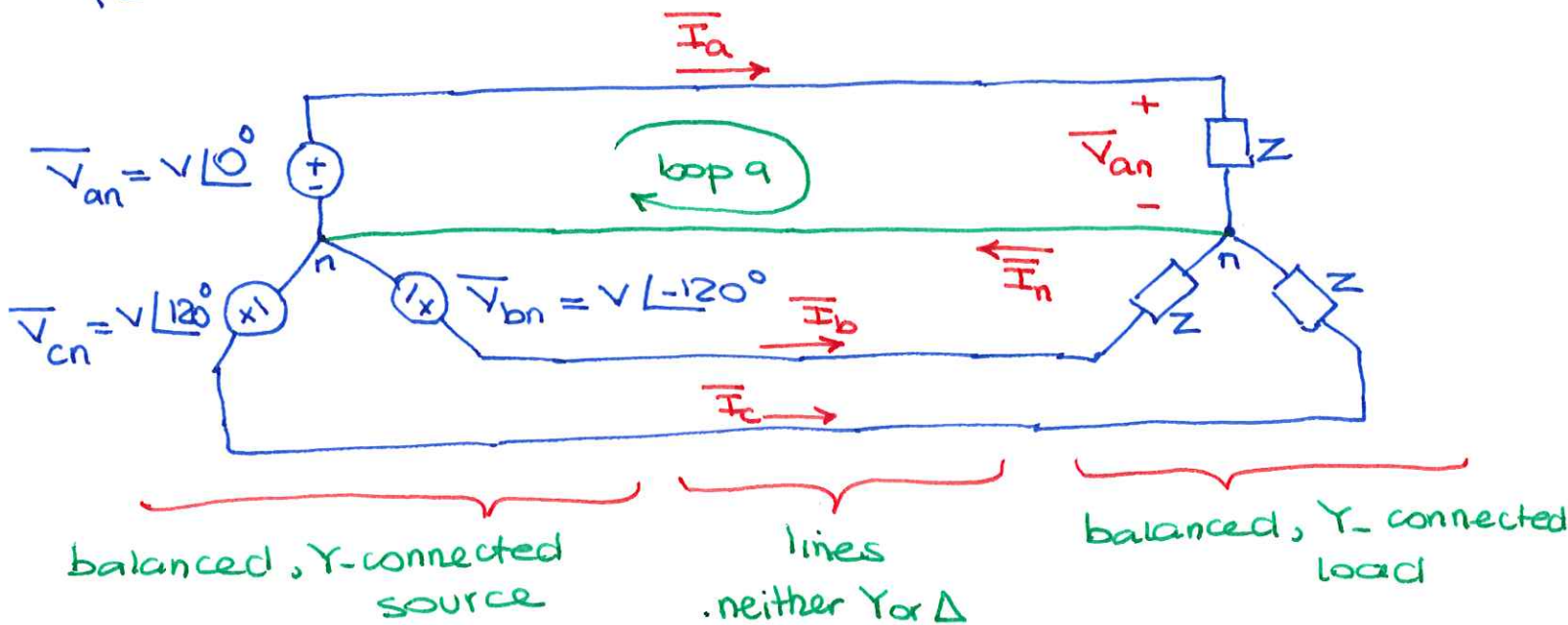we can show that the 3 ϕ system delivers the same power as 3 single phase systems with $\frac{1}{2}$ the conductors (3 instead of 6):



$$\text{KVL around loop a: } V \angle 0^\circ - \bar{I}_a \cdot Z = 0 \quad \therefore \bar{I}_a = \frac{V}{Z}$$

$$\text{Similarly, } \bar{I}_b = \frac{V \angle -120^\circ}{Z}, \quad \bar{I}_c = \frac{V \angle +120^\circ}{Z}$$

$$\begin{aligned} \text{KCL at neutral point } n: \quad \bar{I}_n &= \bar{I}_a + \bar{I}_b + \bar{I}_c \\ &= \frac{V}{Z} \left(1 \angle 0^\circ + 1 \angle -120^\circ + 1 \angle +120^\circ \right) \\ &= 0 \end{aligned}$$


i.e. Neutral (return) conductor is not needed.

Power delivered to the 3 ϕ load:


$$\begin{aligned}\overline{S}_{3\phi} &= \underbrace{\overline{V}_{an} \cdot \overline{I}_a^*}_{V \angle 0^\circ \cdot \left(\frac{V}{Z} \angle 0^\circ\right)^*} + \underbrace{\overline{V}_{bn} \cdot \overline{I}_b^*}_{\left(V \angle -120^\circ\right) \left(\frac{V}{Z} \angle -120^\circ\right)^*} + \underbrace{\overline{V}_{cn} \cdot \overline{I}_c^*}_{= \frac{V^2}{Z^*}} \\ &= \frac{V^2}{Z^*} \qquad \qquad \qquad = \frac{V^2}{Z^*}\end{aligned}$$

$$\therefore \overline{S}_{3\phi} = 3 \cdot \frac{V^2}{Z^*} = 3 \underbrace{\overline{V}_{an} \cdot \overline{I}_a^*}_{\text{power in } 1\phi \text{ system}} = 3 \cdot \overline{S}_{1\phi}$$

power in 1 ϕ system

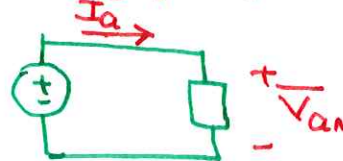

Back to the original problem:

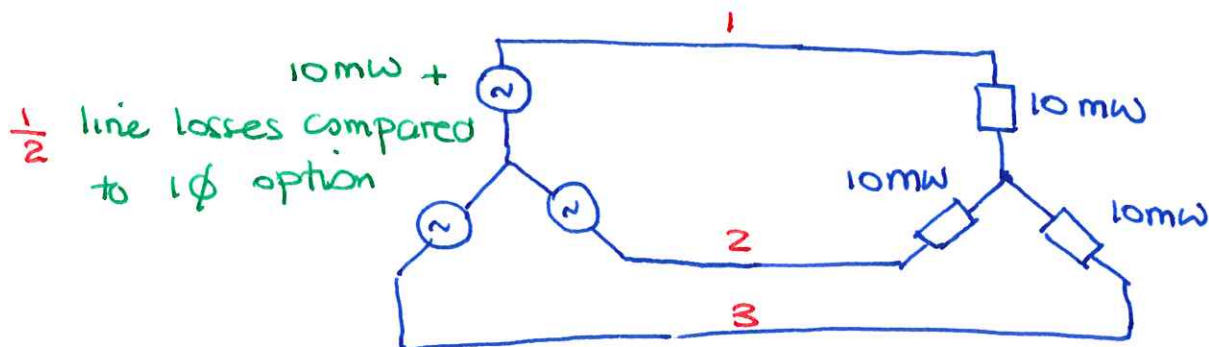

Not shown in the notes, but also very important:

total $p(t)$ in 3 ϕ gen is constant \therefore reduced vibration & noise compared to 1 ϕ gen

Important: Voltages & Currents in 3ϕ Systems

- Voltage in each phase of a device (gen, load) is phase voltage
- Current in each phase of a device (gen, load) is phase current