

Name: SOLUTION

ID: 2015487

B
RW

SCHULICH
School of Engineering



ENEL 487 Final Examination

Wednesday, April 29, 2015

Time: 12:00 – 3:00 pm

Location: Auxiliary Gym

Instructor: Pouyan (Yani) Jazayeri

- Please note that the official University of Calgary examination regulations are printed on page 2 of this paper.
- Exam consists of 7 problems and 16 pages.
- Write answers in the space provided below each question.
- Show your work neatly in the work area. Otherwise, marks for partially correct answers cannot be given.
- Total marks for the exam is 100.
- Closed book exam. You may not refer to books or notes during the test.
- No wireless devices or earphones allowed during exam.
- Only scientific calculators without formulae storage and text display are allowed.

| Question | 1 | 2 | 3 | 4 | 5 | 6 | 7 | Total |
|----------|-----|-----|-----|-----|-----|-----|-----|-------|
| Mark | /15 | /15 | /15 | /15 | /15 | /15 | /10 | /100 |

Problem 1:

Answer the following questions on the scantron sheet provided to you. Correct answers are rewarded 1 point.

1) For a purely capacitive element under sinusoidal steady-state excitation, the voltage and current phasors are:

- a) in phase
- b) perpendicular to each other with V leading I
- ☒ c) perpendicular to each other with I leading V
- d) None of the above

$$\bar{V} = Z \bar{I}$$

$$= (j\omega C)^{-1} \bar{I}$$

$$\bar{V} = \left(\frac{1}{\omega C} \angle -90^\circ \right) \cdot \bar{I}$$

$$\therefore \theta_v = \theta_i - 90^\circ$$

2) The average power in a single-phase ac circuit with a purely inductive load, for sinusoidal steady-state excitation is:

- a) $(I_{rms})^2 X_L$
- b) $(V_{max})^2 / X_L$
- ☒ c) Zero
- d) None of the above

$$P_{avg} = 0$$

3) The admittance of a $-j 1/2 \Omega$ impedance is:

- a) $-j2 \text{ S}$
- ☒ b) $j2 \text{ S}$
- c) $-j4 \text{ S}$
- d) None of the above

$$Y = \frac{1}{Z} = \frac{1}{-j\frac{1}{2}} = j2$$

4) For a balanced Δ load supplied by a balanced source, the line currents into the load are $\sqrt{3}$ times the load currents and lag by 30 degrees.

- ☒ a) True
- b) False

5) Transmission line conductance is usually neglected in power system studies.

- ☒ a) True
- b) False

6) Bundling reduces the series reactance of the line?

- ☒ a) Yes
- b) No

7) In the Newton Raphson method, the Jacobian Matrix $J(x)$ consists of

- ☒ a) Partial derivatives
- b) Inverses
- c) P_{branch} and Q_{branch} expressions
- d) None of the above

8) Which of the following variables is known for a load bus?

- ☒ a) Real Power consumed by the load
- b) Voltage angle
- c) Jacobian matrix
- d) Voltage magnitude

9) The Ybus of a 14 bus systems is a _____ matrix

- a) 14×1
- b) $(14 - 1) \times 14$
- ☒ c) 14×14
- d) Not enough information given

10) The bus selected as the slack bus must have a source of both real and reactive power.

- ☒ a) True
- b) False

11) Per Unit quantity has the same unit/dimension as that of the actual quantity.

- a) True
- ☒ b) False

12) The Alberta market has a demand of 5000MW at the moment. The offers received from the generators are as follows: generator A offers 1000MW at \$15, generator B offers 1000MW at \$25, generator C offers 4000MW at \$0, generator D offers 2000MW at \$20, and generator E offers 2000MW at \$10. What is the market clearing price?

- a) \$20
- b) \$0
- c) \$15
- ☒ d) None of the above

13) Which of the following is not a common heat dissipation technique for transformers?

- a) Forced air
- b) Forced oil
- c) Natural air flow
- ☒ d) None of the above (i.e. They are all acceptable)

14) Select the material with the best conductivity.


- a) Gold
- b) Aluminum
- c) Copper
- ☒ d) Silver

15) In design of ACSR conductors, more aluminum results in lower resistance while more steel results in higher strength.



- ☒ a) True
- b) False

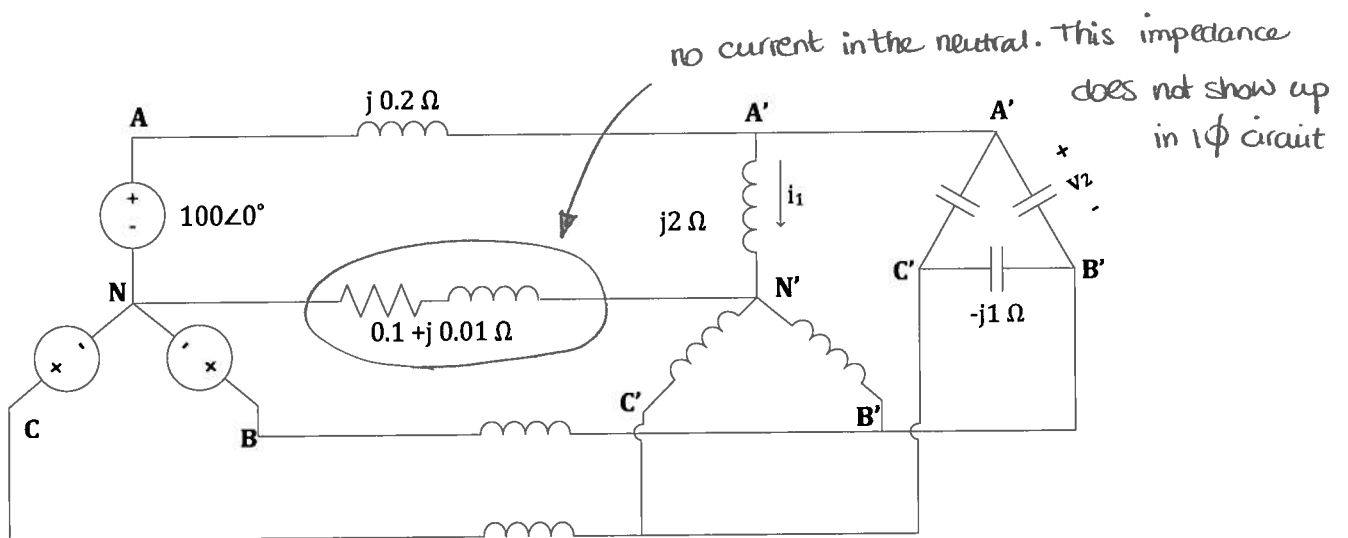Problem 2:

Consider the balanced three-phase system shown below. Determine $v_2(t)$ and $i_1(t)$. [15 marks]



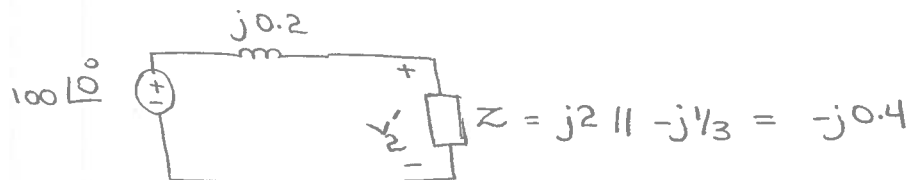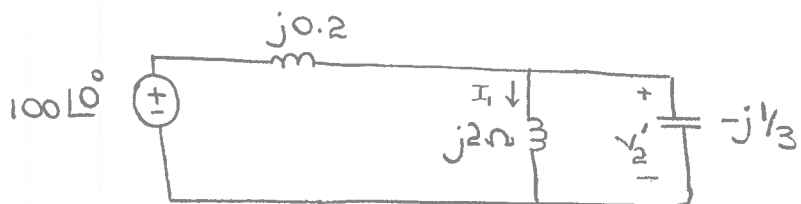• convert Δ -connected load to Y & perform 1 ϕ analysis :



$$\bar{v}_2' = 100 \frac{-j0.4}{-j0.4 + j0.2} = 200 \angle 0^\circ$$

$$\bar{v}_2 = \sqrt{3} \angle 30^\circ \cdot \bar{v}_2' = 200\sqrt{3} \angle 30^\circ \quad \text{or} \quad 346.4 \angle 30^\circ$$

$$v_2(t) = \sqrt{2} \cdot 200\sqrt{3} \cos(\omega t + 30^\circ) \quad \text{or} \quad 489.9 \cos(\omega t + 30^\circ)$$


$$\bar{I}_1 = \frac{\bar{v}_2'}{j2} = \frac{200}{j2} = -j100 \quad \text{or} \quad 100 \angle -90^\circ$$

$$i_1(t) = 100\sqrt{2} \cos(\omega t - 90^\circ) \quad \text{or} \quad 141.4 \cos(\omega t - 90^\circ)$$

Problem 3:

The three phase system shown below has the following ratings:

| | | | |
|------------|---|------------------------|-----------------------------------|
| Generator: | 60 MVA, | 13.8kV (line-to-line), | $X_{\text{gen}} = 0.2 \text{ pu}$ |
| T1: | 50 MVA, | 13.2 kV/132 kV, | $X_{T1} = 0.091 \text{ pu}$ |
| T2: | 50 MVA, | 138 kV/13.8 kV, | $X_{T2} = 0.083 \text{ pu}$ |
| Line: | 15.87 + j79.35 Ω per phase | | |
| Load: | Z Ω per phase (i.e. unknown impedance) | | |

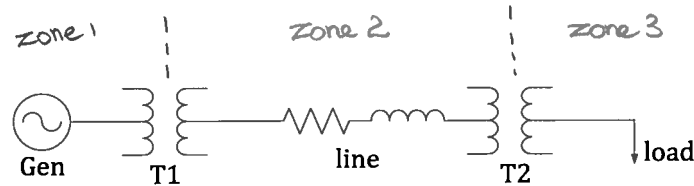

Select a power base of 60 MVA for the system and a base voltage of 13.8kV for the generator zone. Under these base values, the system was analyzed. It was calculated that the load is drawing a current of $0.7\angle -40^\circ \text{ pu}$, and its terminal voltage is $1\angle 0^\circ \text{ pu}$.

- Draw the impedance diagram of the system in per unit. The load impedance can be labeled as Z_{pu} . You will need numerical values for all other impedances. [8 marks]
- Find the load's active and reactive power in per unit. Hint: You can use $S_{\text{pu}} = V_{\text{pu}} I_{\text{pu}}^*$ [3 marks]
- Find the actual quantity of the load's three phase active and reactive power in MW and MVar. [1 marks]
- What is the line current at the load terminals in Amps? [1 mark]
- Find the total active power losses in the line in per unit and MW. [2 marks]

a) $V_{\text{base}_1} = 13.8 \text{ kV}$ (given)

$$V_{\text{base}_2} = V_{\text{base}_1} \times \frac{132}{13.8} = 138 \text{ kV}$$

$$V_{\text{base}_3} = V_{\text{base}_2} \times \frac{13.8}{138} = 13.8 \text{ kV}$$

$$X_{\text{gen}} = 0.2 \text{ pu} \quad (\text{does not change})$$

$$X_{T1} = 0.091 \times \left(\frac{13.2 \text{ kV}}{13.8 \text{ kV}} \right)^2 \frac{60 \text{ MVA}}{50 \text{ MVA}} \approx 0.1 \text{ pu}$$

$$X_{T2} = 0.083 \times \left(\frac{13.8 \text{ kV}}{13.8 \text{ kV}} \right)^2 \frac{60 \text{ MVA}}{50 \text{ MVA}} \approx 0.1 \text{ pu}$$

$$Z_{\text{line}} = \frac{Z_{\text{actual}}}{Z_{\text{base}_2}} = \frac{15.87 + j79.35}{317.4} = 0.05 + j0.25$$

$$\begin{aligned}
 \text{b) } S_{pu} &= V_{pu} \cdot I_{pu}^* = 1 \angle 0^\circ \times (0.7 \angle -40^\circ)^* = 0.7 \angle 40^\circ \text{ pu} \\
 &= \underbrace{0.54}_{P_{pu}} + j \underbrace{0.45}_{Q_{pu}} \text{ pu}
 \end{aligned}$$

$$\text{c) } P_{3\phi} = P_{pu} \times S_{base} = 0.54 \times 60 \text{ MW} = 32.17 \text{ MW}$$

$$Q_{3\phi} = Q_{pu} \times S_{base} = 0.45 \times 60 \text{ MVAR} = 27 \text{ MVAR}$$

$$\text{d) } I_{base3} = \frac{S_{base}}{\sqrt{3} V_{base3}} = \frac{60 \text{ MVA}}{\sqrt{3} \times 13.8 \text{ kV}} = 2510 \text{ A}$$

$$I_{load} = 0.7 \angle -40^\circ \times I_{base3} = 1757 \angle -40^\circ \text{ A}$$

$$\text{e) } P_{loss,pu} = I_{pu}^2 \times R = (0.7)^2 \times 0.05 = 0.0245 \text{ pu}$$

$$P_{loss} = P_{loss,pu} \times S_{base} = 1.47 \text{ MW}$$

Problem 4:

A 60-Hz, 200-km, three-phase overhead transmission line, constructed of ACSR conductors, has a series impedance of $(0.2 + j0.8) \Omega/\text{km}$ per phase and admittance of $j10 \times 10^{-6} \text{ S/km}$ per phase. Using the nominal π circuit, compute ABCD parameters and the voltage and current at the sending end if the load at the receiving end draws 200 MVA at 0.9 lagging and at a line-to-line voltage of 230 kV. [15 marks]

$$Z = z \cdot l = (0.2 + j0.8) \times 200 = 40 + j160 = 164.9 \angle 75.6^\circ \Omega$$

$$Y = y \cdot l = (j10 \times 10^{-6}) \times 200 = j2 \times 10^{-3}$$

$$A = D = 1 + \frac{YZ}{2} = 0.84 + j0.04 = 0.841 \angle 2.73^\circ$$

$$B = Z = 164.9 \angle 75.6^\circ \Omega$$

$$C = Y \left(1 + \frac{ZY}{4} \right) = 0.0018 \angle 91.25^\circ \text{ S}$$

$$V_r = \frac{230 \text{ kV}}{\sqrt{3}} = 132.8 \text{ kV} \quad (\text{line to neutral})$$

$$|I_r| = \frac{S}{\sqrt{3} V_{r, \text{L-L}}} = \frac{200 \times 10^6}{\sqrt{3} \times 230 \times 10^3} = 502.04$$

$$\cos(\theta_{V_r} - \theta_{I_r}) = \text{pf} \quad \therefore \quad \theta_{I_r} = -\cos^{-1}(0.9) = -25.84^\circ$$

\uparrow
 0°

$$\therefore \quad \overline{I_r} = 502.04 \angle -25.84^\circ$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$


$$\therefore \quad V_s = A \cdot V_r + B \cdot I_r = 178.7 \angle 22.5^\circ \text{ kV}$$

$$|V_{s, \text{L-L}}| = \sqrt{3} \times 183.5 = 309.5 \text{ kV}$$

$$I_s = C \cdot V_r + D \cdot I_r = 390.1 \angle 10.82^\circ \text{ A}$$

Problem 5:

Figure below shows the conductor configuration of a completely transposed, three-phase overhead transmission line with bundled phase conductors. All conductors have a radius of 0.7 cm.

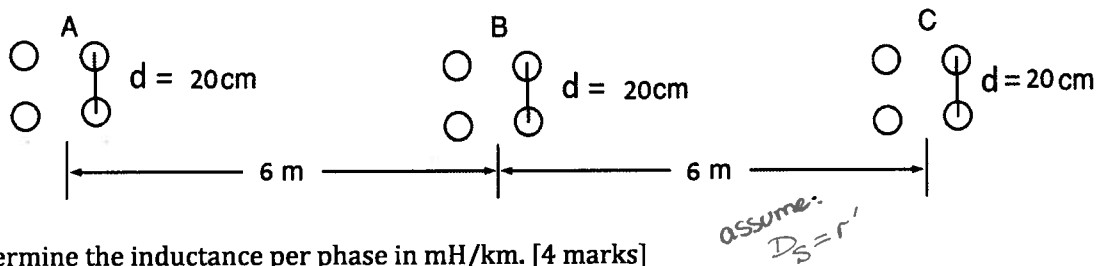

- Determine the inductance per phase in mH/km. [4 marks]
- Determine the inductive line reactance per phase in Ω/km at 60 Hz. Also, calculate the reactive power absorbed by the inductance if a 100 km transmission line with this configuration is operating at 1000A. [4 marks]
- Determine the line-to-neutral capacitance in nF/km per phase. [3 marks]
- Determine the capacitive reactance in Ω/km per phase. Also, calculate the reactive power supplied by the reactance if a 100 km transmission line with this configuration is operating at 200kV. [4 marks]

$$\begin{aligned}
 \text{a) } L &= 2 \times 10^{-7} \ln \frac{D_{eq}}{D_{SL}} \\
 D_{SL} &= 1.091 \sqrt[4]{D_s \cdot d^3} = 1.091 \sqrt[4]{r' \cdot d^3} = 1.091 \sqrt[4]{(0.7788 \times 0.007)(0.2)^3} \\
 &= 0.0887 \text{ m} \\
 D_{eq} &= \sqrt[3]{6 \times 6 \times 12} = 7.56 \text{ m} \\
 \therefore L &= 2 \times 10^{-7} \ln \frac{7.56 \text{ m}}{0.0887 \text{ m}} = 0.889 \text{ mH/km}
 \end{aligned}$$


$$\begin{aligned}
 \text{b) } X_L &= \omega L = 2\pi f \times L = 2\pi 60 \times 0.889 \text{ mH/km} = 0.335 \Omega/\text{km} \\
 Q_L &= 3 \times (I^2 \cdot X_L) = 3 (1000 \text{ A})^2 (100 \text{ km} \times 0.335 \Omega/\text{km}) = 100.5 \text{ mVAR}
 \end{aligned}$$

$$\begin{aligned}
 \text{c) } C_{an} &= \frac{2\pi\epsilon}{\ln \frac{D_{eq}}{D_{sc}}} \quad D_{eq} \text{ same as before; } D_{eq} = 7.56 \text{ m} \\
 D_{sc} &= 1.091 \sqrt[4]{r \cdot d^3} = 1.091 \sqrt[4]{(0.007)(0.2)^3} = 0.0944 \text{ m} \\
 C_{an} &= \frac{2\pi(8.85 \times 10^{-12})}{\ln \frac{7.56 \text{ m}}{0.0944 \text{ m}}} = 12.7 \text{ nF/km}
 \end{aligned}$$

$$\begin{aligned}
 \text{d) } X_C &= \frac{1}{\omega C} = \frac{1}{2\pi \times 60 \times 12.7 \text{ nF/km}} = 2.09 \times 10^5 \Omega/\text{km} \\
 Q_C &= 3 \times -\frac{V_{LN}^2}{X_C} = 3 \times \frac{\left(\frac{V_{LL}}{\sqrt{3}}\right)^2}{X_C} = -\frac{V_{LL}^2}{X_C} = \frac{-(200 \text{ kV})^2}{2.09 \times 10^5 \Omega/\text{km} \times 100 \text{ km}} \\
 &= -1.91 \text{ kVAR}
 \end{aligned}$$

Problem 6:

Considering the system below:

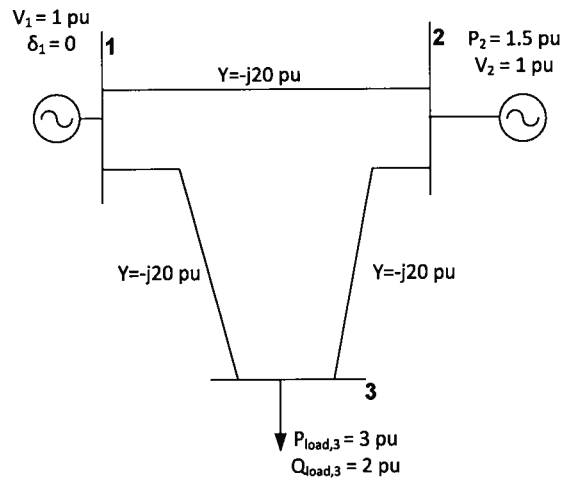a) Complete the following table. Do not include P_{load} and Q_{load} in this table. [3 marks]

| Bus number | Bus type | Known variables | Unknown variables |
|------------|----------|--------------------|--------------------|
| 1 | Slack | V, δ | P_{gen}, Q_{gen} |
| 2 | PV | V, P_{gen} | δ, Q_{gen} |
| 3 | load | P_{gen}, Q_{gen} | V, δ |

b) Create the Y_{bus} matrix for this system [2 marks]

$$b) \quad Y_{bus} = \begin{bmatrix} -j40 & j20 & j20 \\ j20 & -j40 & j20 \\ j20 & j20 & -j40 \end{bmatrix}$$

$$\begin{aligned}
 c) \quad f_1 &= P_{gen,1} - P_{load,1} - V_1 V_1 G[1,1] \cos(\delta_1 - \delta_1) - V_1 V_1 B[1,1] \sin(\delta_1 - \delta_1) \\
 &\quad - V_1 V_2 G[1,2] \cos(\delta_1 - \delta_2) - V_1 V_2 B[1,2] \sin(\delta_1 - \delta_2) \\
 &\quad - V_1 V_3 G[1,3] \cos(\delta_1 - \delta_3) - V_1 V_3 B[1,3] \sin(\delta_1 - \delta_3) \\
 &= P_{gen,1} - (1)(1)(20) \sin(-\delta_2) - V_3 (20) \sin(-\delta_3) \\
 &= P_{gen,1} + 20 \sin \delta_2 + 20 V_3 \sin(\delta_3)
 \end{aligned}$$

$$\begin{aligned}
 f_2 &= P_{gen,2} - P_{load,2} - V_2 V_1 B[2,1] \sin(\delta_2 - \delta_1) - V_2 V_3 B[2,3] \sin(\delta_2 - \delta_3) \\
 &= 1.5 - (1)(1)(20) \sin(\delta_2) - (1) V_3 (20) \sin(\delta_2 - \delta_3) \\
 &= 1.5 - 20 \sin(\delta_2) - 20 V_3 \sin(\delta_2 - \delta_3)
 \end{aligned}$$

$$\begin{aligned}
 f_4 &= Q_{gen,1} - Q_{load,1} + V_1 V_2 B[1,2] \cos(\delta_1 - \delta_2) + (V_1)^2 B[1,1] \cos(\delta_1 - \delta_1) \\
 &\quad + V_1 V_3 B[1,3] \cos(\delta_1 - \delta_3) \\
 &= Q_{gen,1} + 20 \cos(-\delta_2) - 40 + 20 V_3 \cos(-\delta_3)
 \end{aligned}$$

$$d) \quad J_{11}[3,3] = \frac{\partial f_3}{\partial x_3} = \frac{\partial f_3}{\partial \delta_3}$$

$$\begin{aligned} f_3 &= P_{gen,3} - P_{load,3} - V_3 V_1 B[3,1] \sin(\delta_3 - \delta_1) - V_3 V_2 B[3,2] \sin(\delta_3 - \delta_2) \\ &= 0 - 3 - 20 V_3 \sin(\delta_3) - 20 V_3 \sin(\delta_3 - \delta_2) \end{aligned}$$

$$\frac{\partial f_3}{\partial \delta_3} = -20 V_3 \cos(\delta_3) - 20 V_3 \cos(\delta_3 - \delta_2)$$

$$J_{12}[1,2] = \frac{\partial f_1}{\partial x_5} = \frac{\partial f_1}{\partial Q_{gen,2}} = 0$$

$$J_{12}[1,1] = \partial f_1 / \partial x_4 = \partial P_{eq,1} / \partial Q_{gen,1} = 0$$

Problem 7:

The following table shows the branch data of a 4 bus system:

| Line number | Bus to bus | Branch resistance, R (p.u) | Branch Reactance, X (p.u) |
|-------------|------------|----------------------------|---------------------------|
| 1 | 1-2 | 0.564 | 0.981 |
| 2 | 2-3 | 0.873 | 0.765 |
| 3 | 2-4 | 1.092 | 0.45 |
| 4 | 3-4 | 0.5 | 1 |
| 5 | 4-1 | 0.199 | 0.203 |

- a) Calculate the elements in $Y_{bus}[1,1]$ and $Y_{bus}[1,4]$? [4 marks]
- b) A capacitor bank of $j0.2$ pu is connected to bus 1. Will the Y_{bus} matrix change? If yes, calculate the modified elements in the Y_{bus} . If not, explain why. Also, state one reason for adding a capacitor bank to a bus in the power system. [6 marks]

$$a) \quad y_{12} = \frac{1}{Z_{12}} = \frac{1}{0.564 + j0.981} = 0.44 - j0.77 \quad pu$$

$$y_{14} = \frac{1}{Z_{14}} = \frac{1}{0.199 + j0.203} = 2.46 - j2.51 \quad pu$$

$$Y_{Bus}[1,1] = \sum \text{all } y \text{ connected to } 1 = y_{12} + y_{14} = 2.9 - j3.28 \quad pu$$

$$Y_{Bus}[1,4] = -y_{14} = -2.46 + j2.51 \quad pu$$

- b) yes, only $Y_{Bus}[1,1]$ will change. It now includes the admittance of cap bank.

$$\begin{aligned} Y_{Bus}[1,1]_{new} &= Y_{Bus}[1,1]_{old} + Y_{cap} = (2.9 - j3.28) + \frac{1}{-j0.2} \\ &= (2.9 - j3.28) + (j5) \\ &= 2.9 + j1.72 \end{aligned}$$

cap bank added for power factor correction (less losses in line)
or improving the voltage