

From Faraday's Law :  $V_1 = N_1 \frac{d\phi_m}{dt}$  ,  $V_2 = N_2 \frac{d\phi_m}{dt}$


$$\therefore \frac{d\phi_m}{dt} = \frac{V_1}{N_1} = \frac{V_2}{N_2} \therefore \boxed{\frac{V_1}{V_2} = \frac{N_1}{N_2} = a}$$

turns ratio

since  $S_1 = V_1 I_1$  &  $S_2 = V_2 I_2$  and  $S_1 = S_2$

$$\therefore \boxed{\frac{I_1}{I_2} = \frac{N_2}{N_1} = \frac{1}{a}}$$

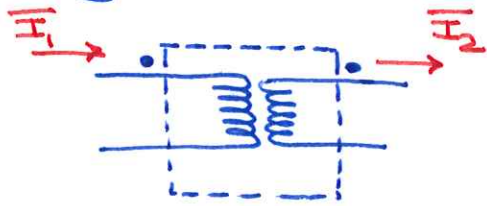• Winding direction is not always visible. Solution: dot convention




when current enters a winding at the dotted terminal, flux is in the direction of the dot

$\therefore$  When current enters dotted terminal from one side & leaves dotted terminal on other side, those currents are in phase

i.e...  $\vec{I}_1$  &  $\vec{I}_2$  are in phase, just scaled up/down by  $1/a$


### Referring Impedances

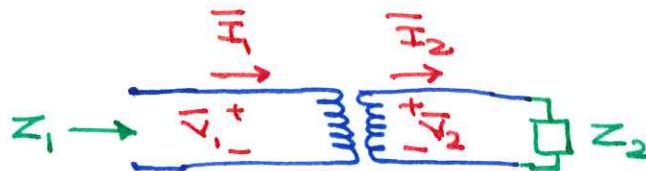

if  $Z_2$  is connected to winding 2,  $Z_1$  (impedance seen from winding 1) is :

$$Z_1 = \frac{V_1}{I_1} = \frac{\frac{N_1}{N_2} \cdot V_2}{\frac{N_2}{N_1} \cdot I_2} = \left(\frac{N_1}{N_2}\right)^2 \cdot \frac{V_2}{I_2} = \left(\frac{N_1}{N_2}\right)^2 \cdot Z_2$$

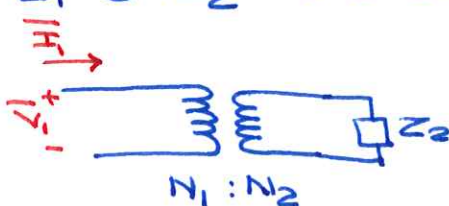$Z_1$  is  $Z_2$  referred to winding 1 :




$$\rightarrow Z_1 = \left(\frac{N_1}{N_2}\right)^2 \cdot Z_2$$

## Real (Non-ideal) Transformers

- Have losses (winding resistance & core losses)
- Have leakage flux
- Have finite  $\mu$

Model:

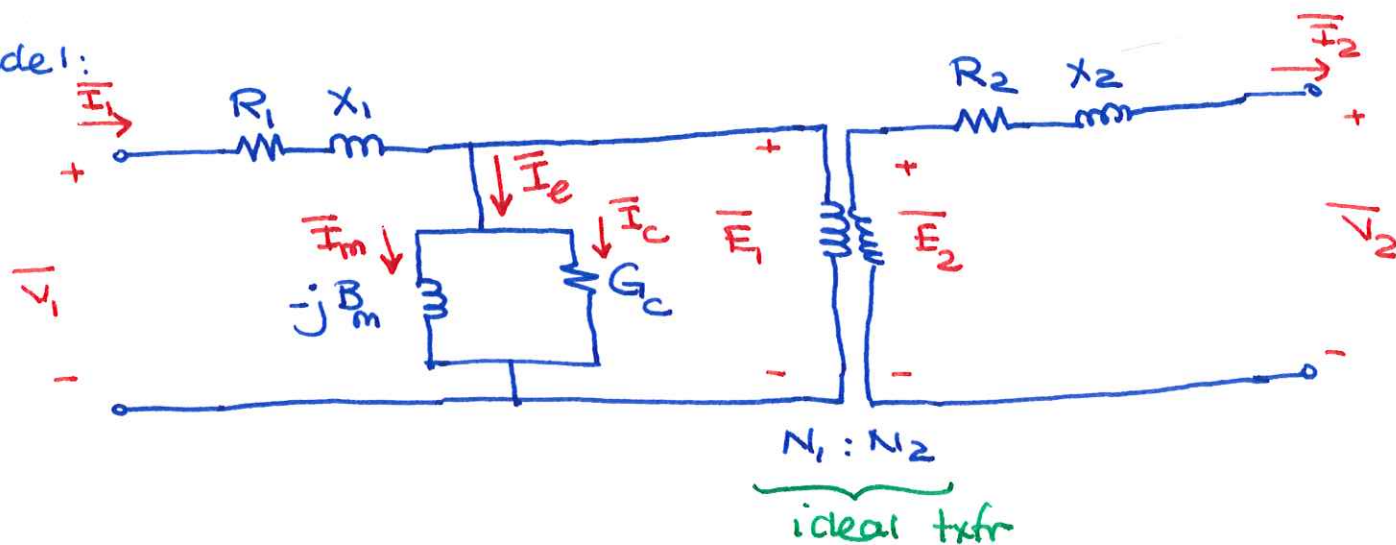

- $R_1$  &  $R_2$  to model winding resistance
- $X_1$  &  $X_2$  to model leakage flux ( $\phi$  from one winding that doesn't link with the other)
- $G_c$  (and  $I_c$ ) to model core losses (hysteresis & eddy current losses)
- $B_m$  (and  $I_m$ ) to model magnetizing current
- Excitation current  $I_e = I_m + I_c$

Reminder: Impedance, Admittance, etc.

$$\underbrace{Y}_{\text{admittance}} \triangleq \frac{1}{Z} = \frac{1}{R + jX} = \underbrace{G}_{\text{conductance}} + j \underbrace{B}_{\text{susceptance}}$$

$$\text{if } R=0, Y = \frac{1}{jX} = -j \frac{1}{X} = -jB$$


$$\text{if } X=0, Y = \frac{1}{R} = G$$

Admittances in parallel add

$$\therefore G_c \parallel -jB_m = \underbrace{G_c - jB_m}_{\text{equivalent admittance of exc'n branch}}$$

equivalent admittance of exc'n branch

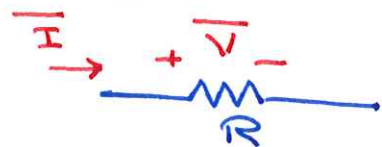To represent a resistor in a circuit, we can use:



$$\bar{V} = \bar{I} \cdot R$$

or



$$\bar{I} = \bar{V} \cdot G$$


$$Y = G = \frac{1}{R}$$

for an inductor



$$\bar{V} = Z \cdot \bar{I} = (jX) \bar{I}$$

or

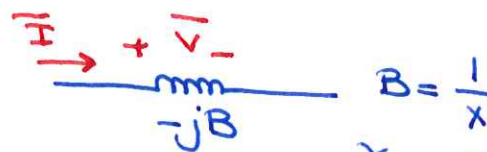


$$\bar{I} = Y \cdot \bar{V} = (-jB) \cdot \bar{V}$$

$$B = \frac{1}{X}$$


$$Y = -jB$$

for a complex impedance

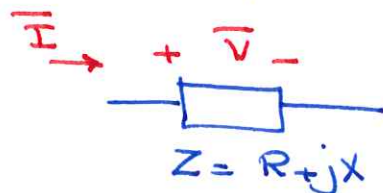

$$\bar{V} = Z \cdot \bar{I}$$

or

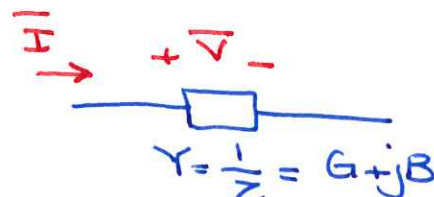

$$\bar{I} = Y \cdot \bar{V}$$

Please note that:

$$Y \triangleq \frac{1}{Z} = \frac{1}{R+jX} \cdot \frac{R-jX}{R-jX} = \frac{R-jX}{R^2 - \cancel{j^2} X^2}$$


$$= \frac{R-jX}{R^2 + X^2} = \underbrace{\frac{R}{R^2 + X^2}}_G + j \underbrace{\frac{-X}{R^2 + X^2}}_B$$

can't use  $G = \frac{1}{R}$  or  $B = \frac{-1}{X}$  for complex  $Z$



Back to the non-ideal transformer model:

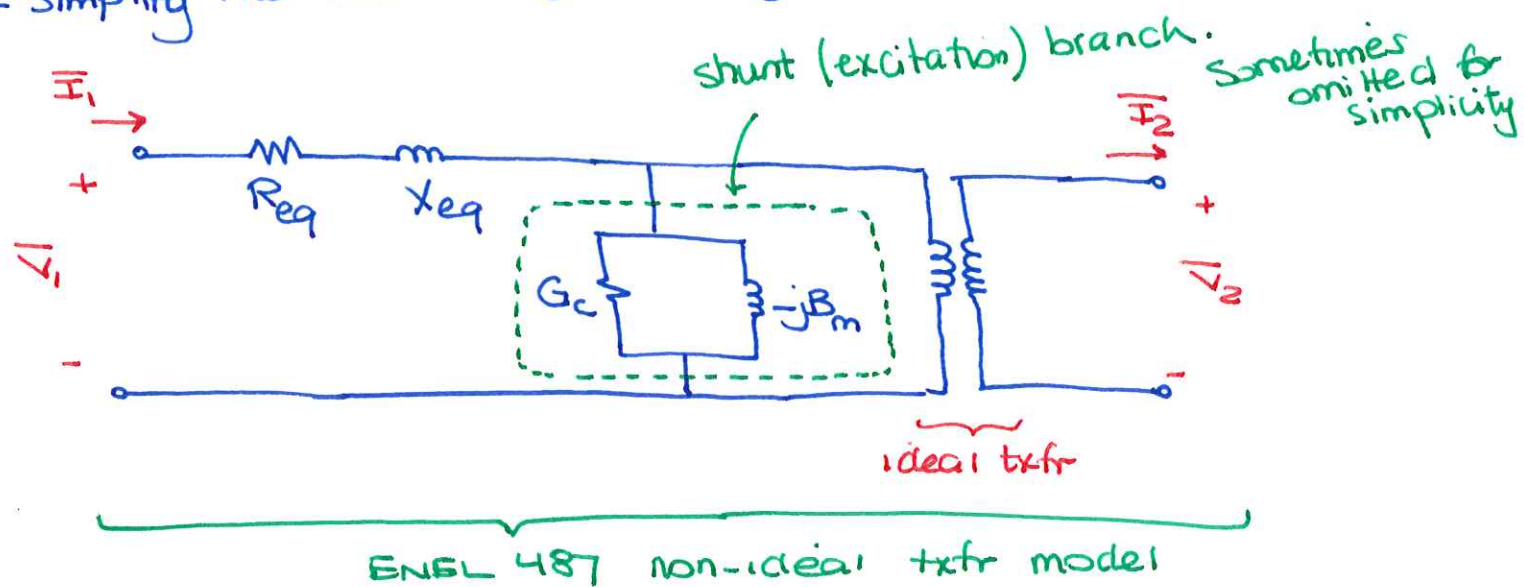
- Simplify the model by referring all impedances to one side:



$$R_{eq} \approx R_1 + \left(\frac{N_1}{N_2}\right)^2 \cdot R_2$$

$$X_{eq} \approx X_1 + \left(\frac{N_1}{N_2}\right)^2 \cdot X_2$$

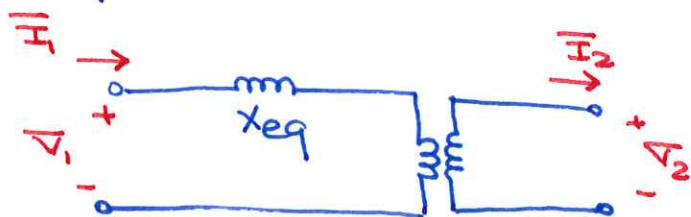- In the simplest non-ideal txfr model,  $R_{eq}$  is also omitted.



## Transformer Rated Values

- Each txfr has:
  - rated voltage for HV & LV side
  - rated current for HV & LV sides
  - rated power

• For 1 $\phi$  txfr: 
$$I_{rated} = \frac{S_{rated}}{V_{rated}}$$

• For 3 $\phi$  txfr: 
$$I_{rated} = \frac{S_{rated}}{\sqrt{3} V_{rated}}$$

↑  
line current
↑  
line-to-line voltage

3 $\phi$  power


Ex : Txfr at Enmax Substation #34 (feeds Campus & adj 'hood)

$$3\phi, \underbrace{69}_{V_{rated\ HV}} : \underbrace{13.2\text{ kV}}_{V_{rated\ LV}}, \underbrace{25\text{ mVA}}_{S_{rated}}$$

$V_{rated}$  : . voltage that a winding & its insulation is designed to handle  
 . Typically, same as system nominal / rated voltage

$$I_{rated\ HV} = \frac{25\text{ mVA}}{\sqrt{3} \times 69\text{ kV}} = 209\text{ A} \quad \leftarrow \text{max current that line HV side can handle}$$
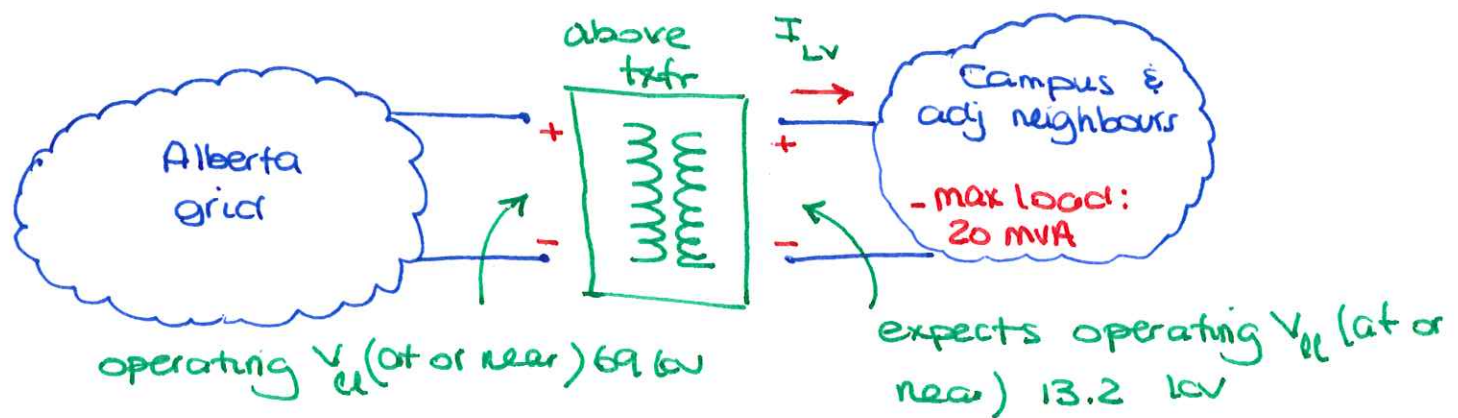
$$I_{rated\ LV} = \frac{25\text{ mVA}}{\sqrt{3} \times 13.2\text{ kV}} = 1093\text{ A}$$



. For a load of 20 mVA, operating LV voltage = 13.2 kV,

$$\text{then } I_{LV} = \frac{20\text{ mVA}}{\sqrt{3} \times 13.2\text{ kV}} = 879\text{ A} < I_{LV\text{ rated}} \quad \text{OK!}$$

. Could we have used a 3 $\phi$ , 138 : 26.4 kV, 25 mVA txfr instead?  
 provides the same voltage transformation

$$\text{if } V_{HV\text{ operating}} = 69\text{ kV}$$

$$\text{then } V_{LV\text{ operating}} = 69 \times \frac{26.4}{138} = 13.2\text{ kV}$$


we still get the same voltage.

. while the voltages are OK, we will exceed  $I_{rated}$  if load > 12.5 mVA

## Measuring Txfr Model Parameters: $R_{eq}$ , $X_{eq}$ , $G_c$ , $B_m$
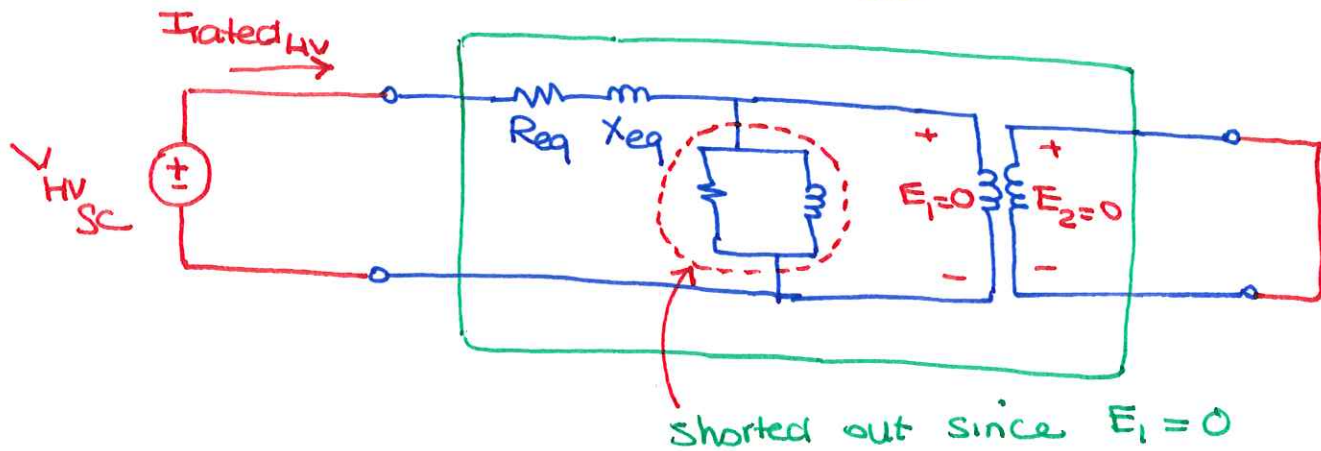
### 1) Short Circuit Test (Load Loss Test)

- Short LV side
- Apply voltage to HV side until  $I_{rated\_HV}$  flows on that side
- Measure applied voltage ( $V_{HV\_sc}$ ) & real power consumed ( $P_{sc}$ )



$$P_{sc} = I_{rated\_HV}^2 \cdot R_{eq} \quad \therefore \boxed{R_{eq} = \frac{P_{sc}}{I_{rated\_HV}^2}}$$

From KVL & Ohm's Law:  $V_{HV\_sc} = I_{rated\_HV} \cdot \underbrace{Z_{eq}}_{R_{eq} + jX_{eq}}$

in magnitudes only:  $V_{HV\_sc} = I_{rated\_HV} \cdot |Z_{eq}|$


we can solve for  $|Z_{eq}| = \frac{V_{HV\_sc}}{I_{rated\_HV}}$

Finally,  $\boxed{X_{eq} = \sqrt{|Z_{eq}|^2 - R_{eq}^2}}$


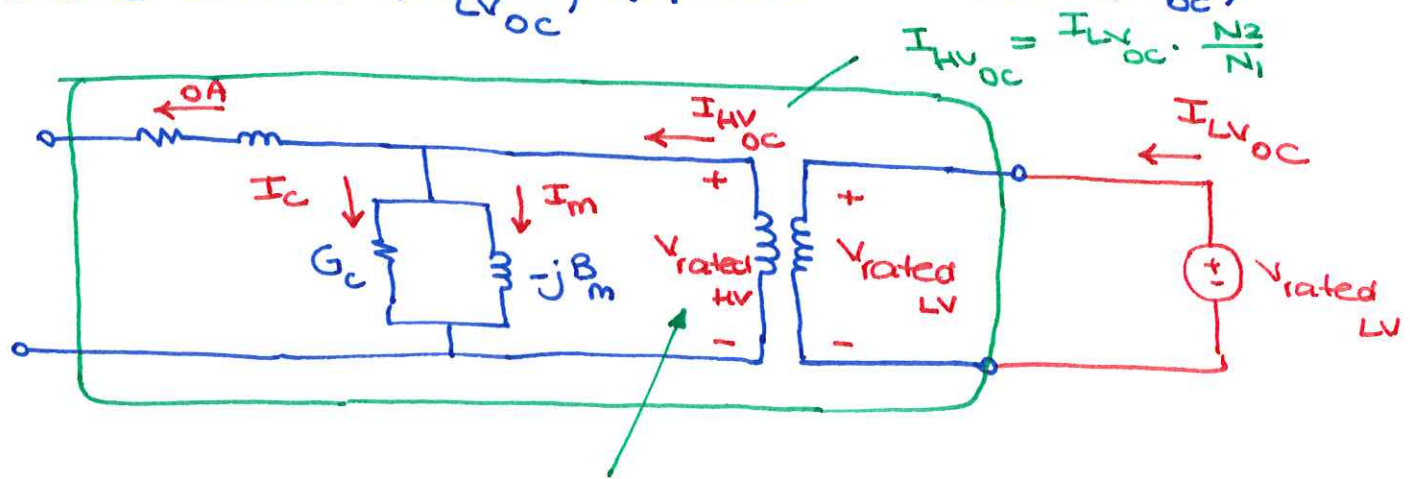
## 2) Open Circuit Test (Core Loss Test, No Load Loss Test)

- Open HV side
- Apply rated voltage to LV terminals
- Measure current ( $I_{LV_{oc}}$ ) & power consumed ( $P_{oc}$ )



$$V_{rated_{HV}} = V_{rated_{LV}} \cdot \frac{N_1}{N_2}$$

• we can calculate  $V_{rated_{HV}}$  &  $I_{HV_{oc}}$  in this test

$$P_{oc} = (V_{rated_{HV}})^2 \cdot G_c \quad \therefore$$

$$G_c = \frac{P_{oc}}{(V_{rated_{HV}})^2}$$

$$\begin{aligned} \overline{I}_{HV_{oc}} &= \overline{I}_c + \overline{I}_m = (\overline{V}_{rated_{HV}} \cdot G_c) + (\overline{V}_{rated_{HV}} \cdot -jB_m) \\ &= \overline{V}_{rated_{HV}} (G_c - jB_m) \end{aligned}$$


total admittance ( $Y_{eq}$ ) of exc'n branch

in magnitudes only,  $I_{HV_{oc}} = V_{rated_{HV}} \cdot |Y_{eq}|$

$$\therefore |Y_{eq}| = \frac{I_{HV_{oc}}}{V_{rated_{HV}}}$$


finally,  $B_m = \sqrt{|Y_{eq}|^2 - G_c^2}$

# Residential Distribution Transformer

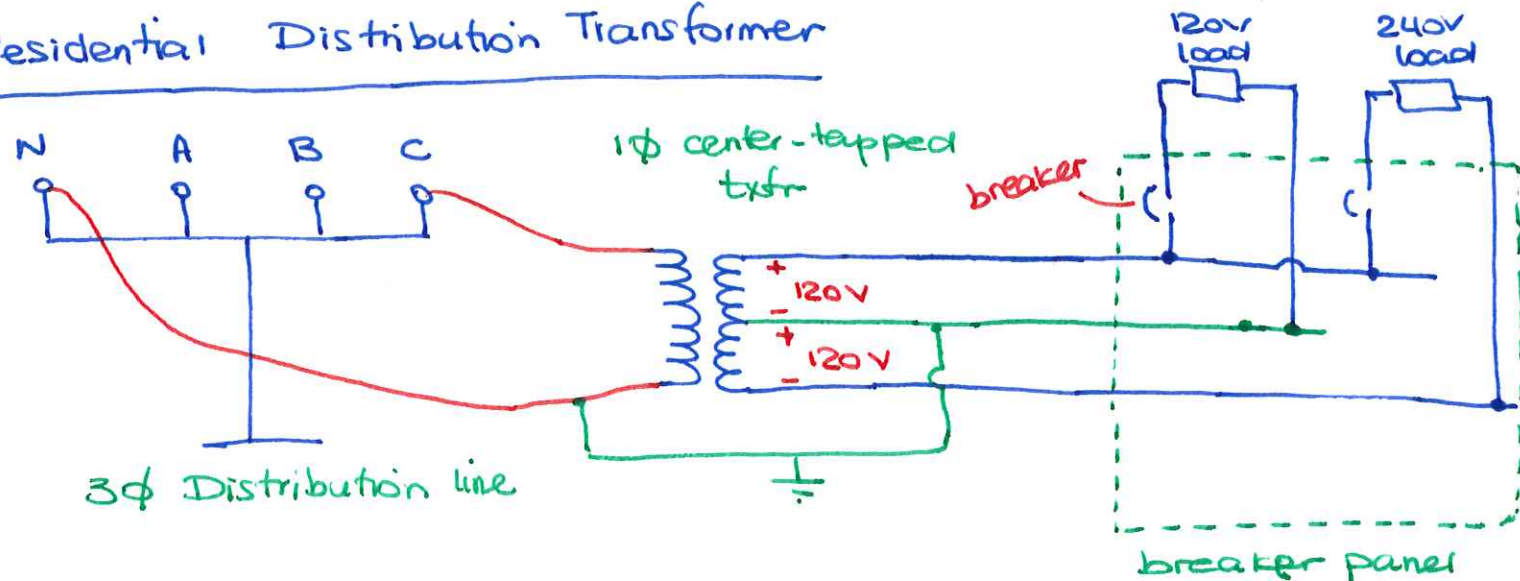

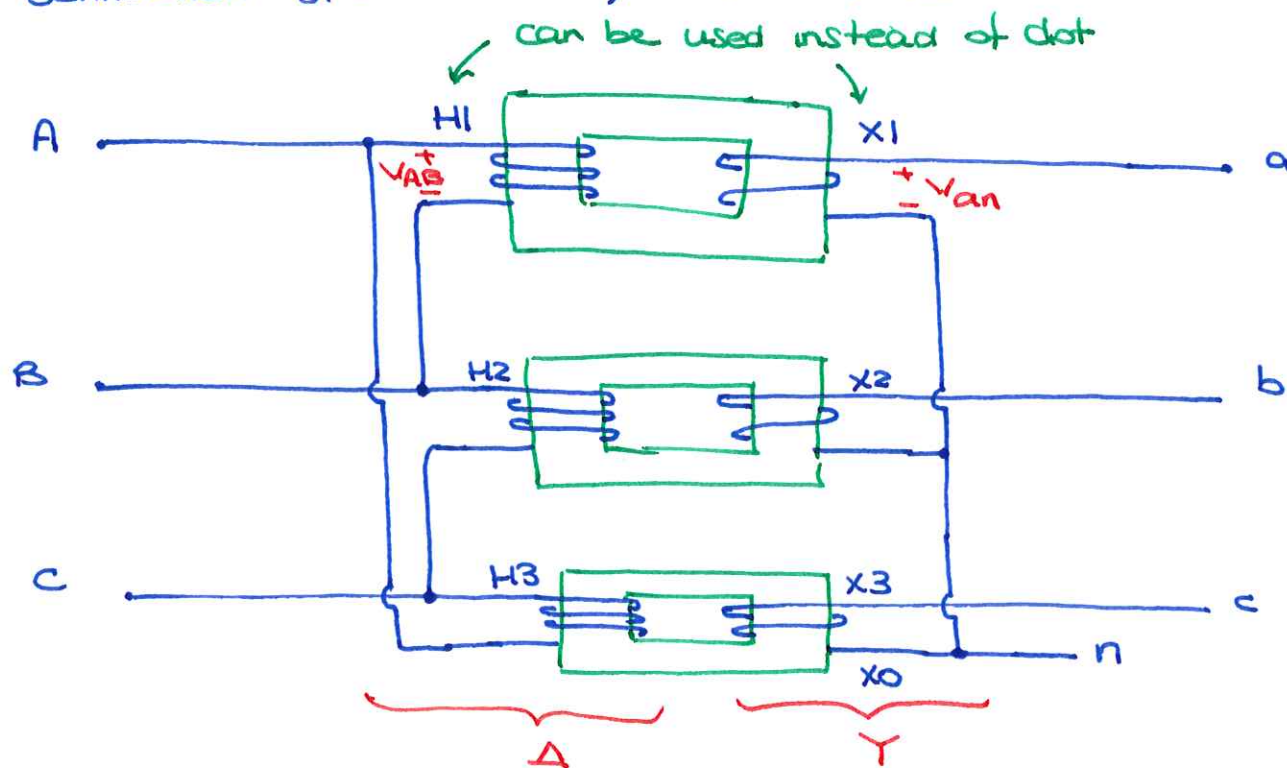
## Three Phase Transformers

- 3 windings on each side: 3 on HV side, 3 on LV side.
- Each side can be connected as Y or  $\Delta$   $\therefore$  4 possible connection types: YY,  $\Delta\Delta$ ,  $\Delta Y$ ,  $Y\Delta$





This is the same as:

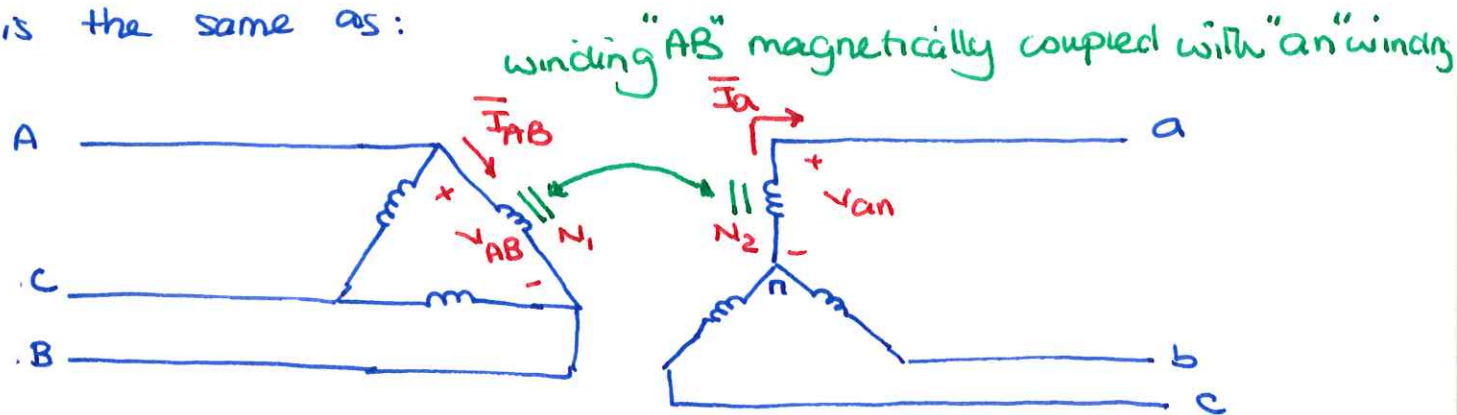

because of the magnetic coupling,

$$\overline{V}_{an} = \frac{N_2}{N_1} \cdot \overline{V}_{AB} : \overline{V}_{an} \text{ in phase with } \overline{V}_{AB}, \text{ scaled down by } \frac{N_2}{N_1}$$

$$\overline{I}_a = \frac{N_1}{N_2} \cdot \overline{I}_{AB} : \overline{I}_a \text{ in phase with } \overline{I}_{AB}, \text{ scaled up by } \frac{N_1}{N_2}$$

- Reminder : we are often interested in line-to-line voltages & line currents on either side of the txfr.

Relationships between  $\overline{V}_{ll}$  &  $\overline{I}_l$  on either side depends on the connection types.